

SEMESTER – III
16PHP312 ADVANCED ELECTRONICS PRACTICALS

L T P C
- - 4 2

ANY TEN EXPERIMENTS

1. Microprocessor – Stepper motor interfacing
2. Microprocessor –Traffic control simulation
3. Microprocessor –Hex Key board interfacing
4. Multiplexer and de-multiplexer
5. Half adder and Half subtractor
6. Full adder and full subtractor
7. BCD to excess – 3 code convertor.
8. A/D Converters any one method, D/A converter .

REFERENCES

1. Ouseph C.C., U.J. Rao and V.Vijayendran, 2007, Practical Physics and Electronics, S. Viswanathan (Printers & Publishers), Pvt. Ltd., Chennai.

Half adder and Half subtractor

AIM

1. To design and set up half adder and half subtractor using a. EXOR gates and AND gates
b. NAND gates

COMPONENTS REQUIRED

IC Trainer kit, IC 7400, IC 7486



PROCEDURE

The simplest binary adder is called half adder. Half adder has two input bits and two output bits. One output bit is the sum and the other is the carry. They are represented by 'S' and 'C' respectively in logic symbol.


The simplest binary subtractor is called half Subtractor. It has two input bits and two output bits. One output bit is the Difference and the other is borrowed. They are represented by 'D' and 'B' respectively in logic symbol

Truth table of Half Adder and Half Subtractor

| Truth table of Half Adder | | | | Truth table of Half Subtractor | | | |
|---------------------------|---|--------|---|--------------------------------|---|--------|-----|
| Inputs | | Output | | Inputs | | Output | |
| A | B | S | C | A | B | D | BOR |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 |

  

 Logic Gate circuits of Half adder for NAND gate



Logic Gate circuits of Half subtractor for NAND gate

RESULT

Half adder and Half subtractor are constructed and their truth tables are verified.

Full adder and Full subtractor

AIM

1. To design and set up full adder and full subtractor using
 - a. EXOR gates and AND gates
 - b. NAND gates

COMPONENTS REQUIRED

IC Trainer kit, ICS 7400, IC 7486


PRINCIPLE

A half adder has no provision to add a carry from the lower order bits when binary numbers are added. When two input bits and a carry are to be added the number of input bits becomes three and the input combination increases to eight. For this full adder is used. Like half adder it also has a sum bit and a carry bit. The new carry generated is represented by 'Cout' and the carry generated from the previous addition is represented by 'Cin'


When two input bits and a borrow have to be subtracted the number of input bits equal to three and the input combinations increases to eight, for this a full subtractor is used.

Truth table of Full Adder and Full Subtractor

| Truth table of Full Adder | | | | | Truth table of Full Subtractor | | | | |
|---------------------------|---|-----|--------|------|--------------------------------|---|---|--------|---|
| Inputs | | | Output | | Inputs | | | Output | |
| A | B | Cin | S | Cout | A | B | | D | |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

 

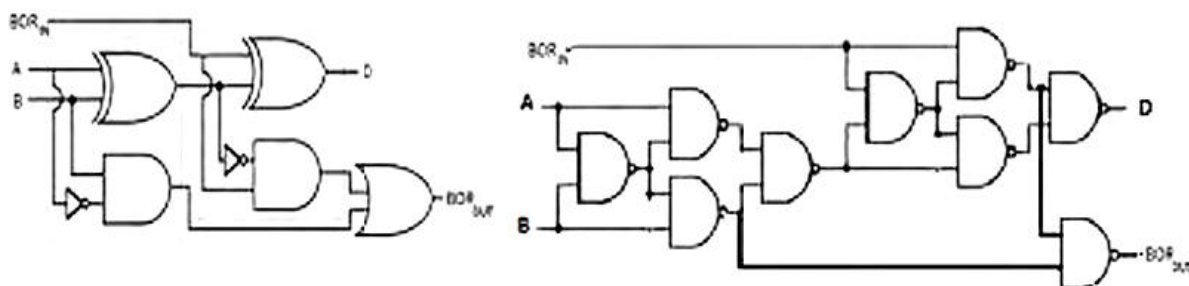Logic Gate circuits of Full adder for NAND gate



Logic Gate circuits of Full subtractor for NAND gate

PROCEDURE

1. Verify whether all the wires and components are in good condition
2. Set up full adder circuit and feed all the input combinations
3. Observe the output corresponding to input combinations and enter it in the Truth table
4. Repeat the above steps for Full subtractor circuits

RESULT

Full adder and Full subtractor circuit was constructed and the truth table was verified

Digital Comparator

AIM

To design and setup single bit comparator using logic gates and verify the truth table.

PRINCIPLE

Digital or Binary Comparators compares the digital signals present at their input terminals and produce an output depending upon the condition of those inputs.

The digital comparator accomplishes this using several logic gates that operate on the principles of Boolean algebra. The purpose of a Digital Comparator is to compare a set of variables or unknown numbers, for example A ($A_1, A_2, A_3, \dots A_n$, etc) against that of a constant or unknown value such as B ($B_1, B_2, B_3, \dots B_n$, etc) and produce an output condition or flag depending upon the result of the comparison. There are two main types of Digital Comparator available and these are.

Identity Comparator - an *Identity Comparator* is a digital comparator that has only one output terminal for when the inputs $A = B$


Magnitude Comparator - a *Magnitude Comparator* is a type of digital comparator that has three output terminals, one each for equality ($A = B$), greater than ($A > B$) and less than ($A < B$)

This is useful if we want to compare two variables and want to produce an output when any of the above three conditions are achieved. For example, produce an output from a counter when a certain count number is reached. Consider the truth table of simple 1-bit comparator.

Truth table of digital- comparator

| INPUT | | OUTPUT | | |
|-------|---|--------|-----|-----|
| B | A | A>B | A=B | A<B |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| | | | | |

 Digital comparators actually use Exclusive-NOR gates within their design for comparing their respective pairs of bits. When we are comparing two binary or BCD values or variables against each other, we are comparing the "magnitude" of these values, logic "0" against a logic "1" which is where the term Magnitude Comparator comes from.



RESULT

Designed and setup single bit comparator using logic gates and verified the truth table.

BCD to Excess – 3 code convertor

AIM


To design and set up the circuit of BCD to Excess-3 converter

COMPONENTS REQUIRED

IC Trainer kit, IC 7486, IC 7408, IC 7404, IC 7432

PRINCIPLE

 The Excess-3 code for a decimal digit is the binary combination corresponding to the decimal digit plus 3. For example, the excess-3 code for decimal digit 5 is the binary combination for $5+3=8$, which is 1000. Each BCD digit four bits with the bits with the bits, from most significant to least significant, labelled A,B,C,D. As the same for excess-3 labeled W,X,Y,Z.



BCD Logic circuit

Truth Table of BCD Logic circuit

| Input (BCD) | | | | Output (Excess-3) | | | |
|-------------|---|---|---|-------------------|---|---|---|
| A | B | C | D | W | X | Y | Z |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |

| | | | | | | | |
|---|---|---|---|---|---|---|---|
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |

PROCEDURE

1. Test all the components using multi meter and digital IC tester
2. Verify the truth table of the circuit by feeding input bit combinations

RESULT

The circuit of BCD to Excess-3 converter has set up and verified the result.

Multiplexer and de Multiplexer

AIM

To design Multiplexer and Demultiplexer and verify their truth tables.

COMPONENTS REQUIRED: -


Digital IC trainer kit, IC

PRINCIPLE


In electronics, a multiplexer (or mux) is a device that selects one of several analog or digital input signals and forwards the selected input into a single line. A multiplexer of 2^n inputs has n select lines, which are used to select which input line to send to the output. An electronic multiplexer can be considered as a multiple-input, single-output switch. Multiplexers are mainly used to increase the amount of data that can be sent over the network

within a certain amount of time and bandwidth. A multiplexer is also called a data selector.

 Conversely, a demultiplexer (or demux) is a device taking a single input signal and selecting one of many data-output-lines, which is connected to the single input. An electronic demultiplexer can be considered as a single-input, multiple-output switch. A multiplexer is often used with a complementary demultiplexer on the receiving end.



| TRUTH TABLE | | |
|-------------|----|------|
| S1 | S0 | DATA |
| 0 | 0 | Y0 |
| 0 | 1 | Y1 |
| 1 | 0 | Y2 |
| 1 | 1 | Y3 |

 

| TRUTH TABLE | | | | | | |
|-------------|----|----|---------|----|----|----|
| INPUTS | | | OUTPUTS | | | |
| DATA | S1 | S0 | Y3 | Y2 | Y1 | Y0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 |

PROCEDURE:

1. Connections are made as per the circuit diagram
2. Switch on the power supply
3. Apply different combinations of inputs and observe the outputs; compare the outputs with the truth tables.

RESULT:


Multiplexer and Demultiplexer are constructed and verified the truth tables.

MICROPROCESSOR – TRAFFIC CONTROL STIMULATION

Aim :

To interfaces traffic light controller with microprocessor 8085.

Flow chart :

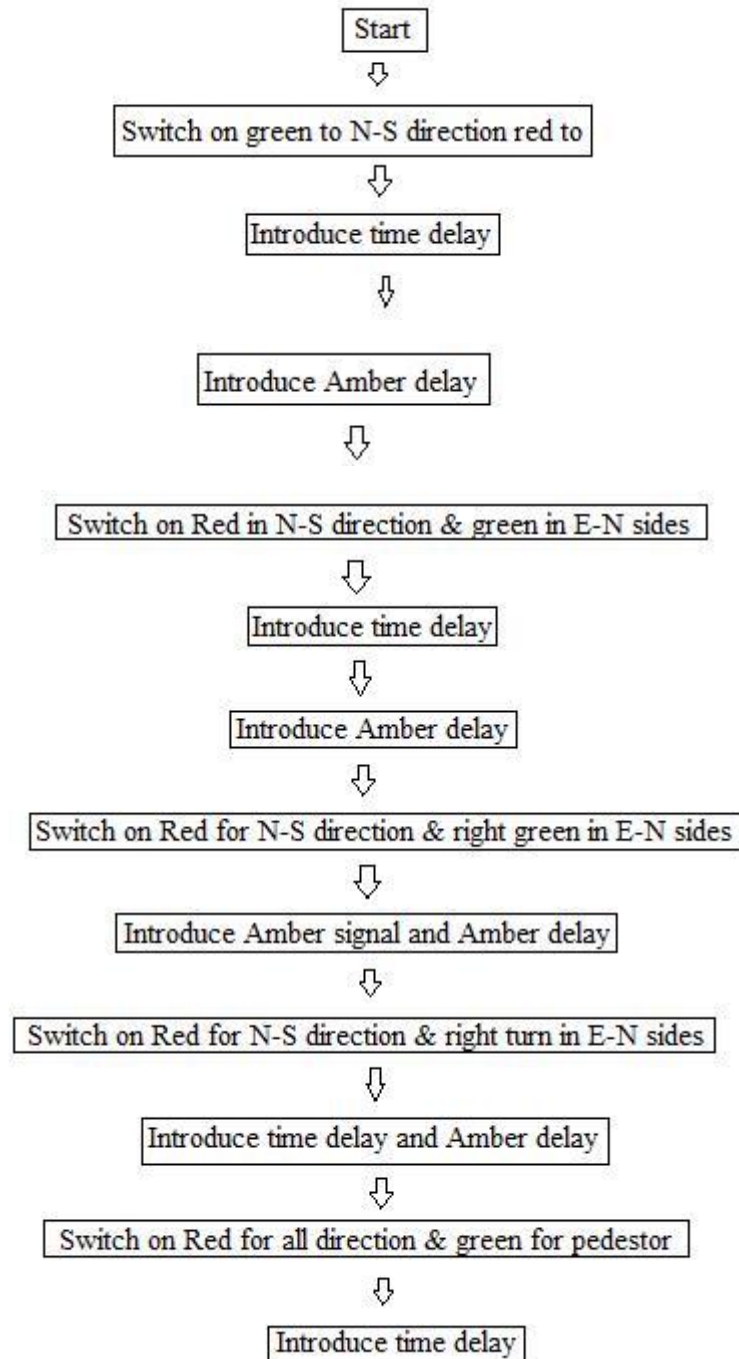

| MEMORY ADDRESS | MNEMONICS | | COMMENTS |
|-------------------|-----------|--------|---|
| | OPCODE | OPERAN | |
| 8500 | MVI | A, 30 | All ports as o/p |
| 8502 | OUT | 25 | |
| 8504 | MVI | A, 0F | For prides for program |
| 8506 | OUT | 21 | |
| 8508 | MVI | A, 8D | For green |
| 850A | CAL | 20 | |
| 850C | L | 8569 | Sequence delay |
| 850F | CAL | 885F | Amber delay |
| 8512 | L | A, | For stopping N – |
| 8514 | MVI | UD | |
| 8516 | OUT | 20 | side Sequence |
| 8519 | CAL | 8569 | delay Amber |
| | L | 855F | delay |
| 851C | CAL | | For free left in all sides and stopping |
| 851E | L | A, 49 | F-W sides for right turn in N sides |
| 8520 | CAL | 20 | |
| 8522 | L | A, 01 | |
| 8524 | | 20 | |
| 8527 | MVI | 8569 | |
| 8529 | OUT | A, 00 | |
| 852B | MVI | 22 | |
| 852E | OUT | 855 | For amber delay |
| 8530 | CAL | F | For stopping vehicle in N-S direction |
| 8532 | L | A, | |
| 8534 | MVI | 89 | For right turn in t-w sides |
| 8536 | OUT | 20 | |
| 8539 | CAL | A, 02 | Sequence delay |
| 853B | L | 22 | |
| 853D | MVI | 8569 | |

| | | | |
|------|------|-------|---|
| 854E | MVI | C, 10 | For amber signal all sides Delay count |
| 8550 | CALL | 856F | |
| 8553 | MVI | A, 30 | |
| 8555 | OUT | 20 | |
| 8557 | MVI | C, 08 | |
| 8559 | CALL | 856F | |
| 855C | JMP | 850 A | |
| 855F | MVI | A, 39 | |
| 8561 | OUT | 20 | |
| 8563 | MVI | C, 08 | |
| 8565 | CALL | 856F | |
| 8568 | RET | | |

Delay program :

| MEMORY ADDRESS | MNEMONICS | |
|----------------|-----------|---------|
| | OPCODE | OPERAND |
| 8569 | MVI | B, 40 |
| 856B | CALL | 856F |
| 856E | RET | |
| 856F | MVI | C, FF |
| 8571 | MVI | A, FF |
| 8573 | NOP | |
| 857A | DCR | A |
| 8575 | JNZ | 8573 |
| 8578 | DCR | C |
| 8579 | MOV | A,B |
| 857C | JNZ | 8571 |
| 857D | ORA | B |
| 857E | JZ | 8583 |
| 8581 | DCR | B |
| 8582 | JZ | 856F |
| 8585 | RET | |

Result:

The traffic control system is stimulated using microprocessor 8085.