

SYLLABUS

B.E Electronics and Communication Engineering

2018-2019

Semester-III

18BEEEC302

ELECTRONIC DEVICES

3H-

3C

Instruction Hours/week: L:3 T:1 P:0

Marks: Internal:40 External:60

Total:100

End Semester Exam:3 Hours

Course Objectives

To expose the students about the construction working and applications of basic electronic devices essential for subsequent courses on

- Analog electronics
- Analog & digital communication and
- CMOS design.

Course outcomes

At the end of this course students will demonstrate the ability to

- Understand the principle of semiconductor physics
- Understand and utilize the mathematical models of semiconductor junctions and MOS transistors for circuits and systems.
- Understand the fabrication process of integrated circuits.

UNIT I INTRODUCTION TO SEMICONDUCTOR PHYSICS

Review of Quantum Mechanics, Electrons in periodic Lattices, E-k diagrams. Energy bands in intrinsic and extrinsic silicon; Carrier transport: diffusion current, drift current, mobility and resistivity; sheet resistance, design of resistors

UNIT II SEMICONDUCTOR DIODES

Generation and recombination of carriers; Poisson and continuity equation P-N junction characteristics, I-V characteristics, and small signal switching models; Avalanche breakdown, Zener diode, Schottky diode, LED, photodiode and solar cell

UNIT III BIPOLAR TRANSISTORS

Bipolar Junction Transistor- Construction – working, I-V characteristics, transistor configurations and input- output characteristics, Early effect (base width modulation) – Ebers-Moll Model, transistor as an amplifier –Transistor as a switch.

UNIT IV FIELD EFFECT TRANSISTORS

Field-Effect Transistors: construction, working and VI characteristics of JFET, MOSFET – enhancement MOSFET, depletion MOSFET, their working principle and VI characteristics, MOS capacitor, C-V characteristics, and small signal models of MOS transistor.

UNIT V IC FABRICATION

Integrated circuit fabrication process: oxidation, diffusion, ion implantation, photolithography, etching, chemical vapor deposition, sputtering, twin-tub CMOS process.

Suggested Readings

1. G. Streetman, and S. K. Banerjee, "Solid State Electronic Devices," 7th edition, Pearson, 2014.
2. D. Neamen, D. Biswas "Semiconductor Physics and Devices," McGraw-Hill Education 2003.
3. S. M. Sze and K. N. Kwok, "Physics of Semiconductor Devices," 3rd edition, John Wiley & Sons, 2006.
4. C.T. Sah, "Fundamentals of solid state electronics," World Scientific Publishing Co. Inc, 1991.
5. Y. Tsividis and M. Colin, "Operation and Modeling of the MOS Transistor," Oxford Univ. Press, 2010.
6. Salivahanan Electronic Devices and circuits Tata McGraw-Hill publishing company 2007

FACULTY IN-CHARGE

HOD / ECE

LECTURE PLAN

NAME OF THE STAFF: G.R. MAHENDRA BABU

DESIGNATION : ASSISTANT PROFESSOR

CLASS : B.E-II YEAR ECE

SUBJECT : ELECTRONIC DEVICES

SUBJECT CODE : 18BEEEC302

S.No.	TOPICS TO BE COVERED	TIME DURATION	TEACHING AIDS
UNIT-I SEMICONDUCTOR DIODES AND SPECIAL PURPOSE DIODES			
1	Introduction	3	
2	Formation of PN junction – working principle	1	T1-Pg.No: 42-46, 56, 85
3	VI characteristics – PN diode currents	1	T1-Pg.No:93,60-65
4	diode current equation	1	T1-Pg.No: 86-87, 100-101
5	Diode resistance – transition and diffusion capacitance	1	T1-Pg.No:102-104
6	Tutorial	1	
7	diode models – voltage breakdown in diodes.	1	T1-Pg.No: 113-117,120-128
8	Special purpose diodes : Zener diode-point-contact diode	1	T1-Pg.No:130-141,143-146
9	backward diode- varactor diode	1	T1-Pg.No:143-146,163-164
10	step- recover y diode- schottky diode,	1	T1-Pg.No:137, R3-Pg.No:105
11	PNPN diode – RF diode	1	T1-Pg.No:164-170
12	Tutorial	1	
	Total (Theory + Tutorial)	14 Hrs (12+2)	
UNIT II BIPOLAR TRANSISTORS			
1	Bipolar Transistors: Construction – working	1	T1-Pg.No:255-256,259-261
2	transistor currents	1	T1-Pg.No:257-259,261-262
3	transistor configurations and input- output characteristics	2	T1-Pg.No:264-268,274
4	Early effect (base width modulation)	1	T1-Pg.No:265
5	Tutorial	1	
6	Ebers Moll model	1	T1-Pg.No:262,277
7	transistor as an amplifier	1	T1-Pg.No:259
8	Transistor as a switch.	1	T1-Pg.No:293-298

9	Transistor applications	1	
10	Tutorial	1	
	Total (Theory + Tutorial)	11 Hrs (9+2)	
UNIT III FIELD EFFECT TRANSISTORS			
1	Field-Effect Transistors: construction, working and VI characteristics of JFET	2	T1-Pg.No:462-469
2	comparison of BJT and JFET	1	W1,W2
3	MOSFET – enhancement MOSFET, depletion MOSFET, their working principle and VI characteristics,	2	T1-Pg.No:472-475
4	Tutorial	1	
5	comparison of MOSFET with JFET	1	W3,W4
6	Comparison of D-MOSFET with E MOSFET	1	W5
7	CMOS, MESFET	1	W6,W7
8	CCD.	1	w8
9	Tutorial	1	
	Total (Theory + Tutorial)	11 Hrs (9+2)	
UNIT IV DC POWER SUPPLIES			
1	Rectifiers and Filters: Block schematic of a typical DC power supply	1	S.Salivahanan, N Suresh Kumar, “Electronic Devices and Circuits”
2	Single phase HWR, FWR, full- wave bridge rectifier	1	
3	Power supply filters (ripple factor and efficiency analysis)	1	
4	Bleeder resistor, voltage dividers	1	
5	Voltage regulators: voltage regulation,	1	
6	Tutorial	1	
7	Zener diode shunt regulator, transistor series regulator	1	
8	Transistor shunt regulator	1	
9	Switching regulators	1	
10	Design of complete DC power supply circuit	1	
11	Tutorial	1	
	Total (Theory + Tutorial)	11 Hrs (9+2)	
UNIT V INTEGRATED CIRCUIT FABRICATION			
1	Integrated circuit – advantages and drawback of ICs	1	R7-Pg.No:1
2	Scale of integration –classification of ICs	1	R7-Pg.No:2-3
3	Definition of linear IC and digital IC with examples	2	R7-Pg.No:1-2
4	manufacturing process of monolithic ICs	2	T1-Pg.No:500-508
5	Tutorial	1	
6	Fabrication of components (diode, capacitor, bipolar transistor and resistor) on monolithic IC	2	T1-Pg.No:509-517
7	Comparison of MOS ICs and bipolar ICs.	1	

8	Tutorial	1	
	Total (Theory + Tutorial)	11 Hrs (9+2)	

Total Lecture: 58 Hours (48+10)

TEXT BOOKS:

S.NO	Author(s) Name	Title of the book	Publisher	Year of publication
1	Millman and Halkias	Electronic devices and Circuits	Tata McGraw Hill International	2010
2	David A.Bell	Fundamental of electronic devices and circuits	Oxford press	2009

REFERENCES:

S.NO.	Author(s) Name	Title of the book	Publisher	Year of publication
1	Street Man	Solid State Electronic Devices'	Prentice Hall Of India,6th edition	2005
2	Mathur Kulshrestha and Chadha	Electron devices and Applications and Integrated circuits'	Umesh Publications	2005
3	Thomas L. Floyd	Electron Devices	Charles and Messil Publications	2012
4	G.K.Mithal	Electronic Devices and Circuits	Khanna Publishers	2013
5	Robert L. Boylestad and Louis Nashelsky	Electronic Devices and Circuit Theory	Pearson Education, 9th Edition,	2009.
6	B. Somanathan Nair	Electronic Devices and Applications	PHI,	2006

ADDITIONAL REFERENCES:

7.	D.roy Choudhury, Shail B.jain	Linear Integrated Circuits	New Age International Limited	2010
8.	S.Salivahanan N Suresh Kumar	Electronic Devices and Circuits	Tata McGraw Hill Education Private Limited	2012

Websites:

1. <http://www.rfwireless-world.com/Terminology/BJT-vs-FET.html>
2. <http://swissen.in/JFETvsBJT.php>
3. <http://www.circuitstoday.com/jfet-and-mosfet-comparison>
4. <http://www.electricalbasicprojects.com/mosfet-vs-jfet-comparison/>
5. <http://www.rfwireless-world.com/Terminology/Depletion-MOSFET-vs-Enhancement-MOSFET.html>.
6. <https://en.wikipedia.org/wiki/CMOS>
7. <http://www.radio-electronics.com/info/data/semicond/fet-field-effect-transistor/gaasfet-mesfet-basics.php>
8. <https://www.elprocus.com/know-about-the-working-principle-of-charge-coupled-device/>

FACULTY IN-CHARGE

HOD/ECE

Introduction – Biasing

The analysis or design of a transistor amplifier requires knowledge of both the dc and ac response of the system. In fact, the amplifier increases the strength of a weak signal by transferring the energy from the applied DC source to the weak input ac signal. The analysis or design of any electronic amplifier therefore has two components:

- The dc portion

and

- The ac

portion

During the design stage, the choice of parameters for the required dc levels will affect the ac response.

What is biasing circuit?

Biasing: Application of dc voltages to establish a fixed level of current and voltage.

Purpose of the DC biasing circuit

- To turn the device “ON”
- To place it in operation in the region of its characteristic where the device operates most linearly.
- Proper biasing circuit which it operate in linear region and circuit have centered Q-point or midpoint biased
- Improper biasing cause Improper biasing cause
 - Distortion in the output signal
 - Produce limited or clipped at output signal


Important basic relationship


$$I_E = I_C + I_B$$
$$\beta = \frac{I_C}{I_B}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$V_{CB} = V_{CE} - V^{BE}$$

Operating Point

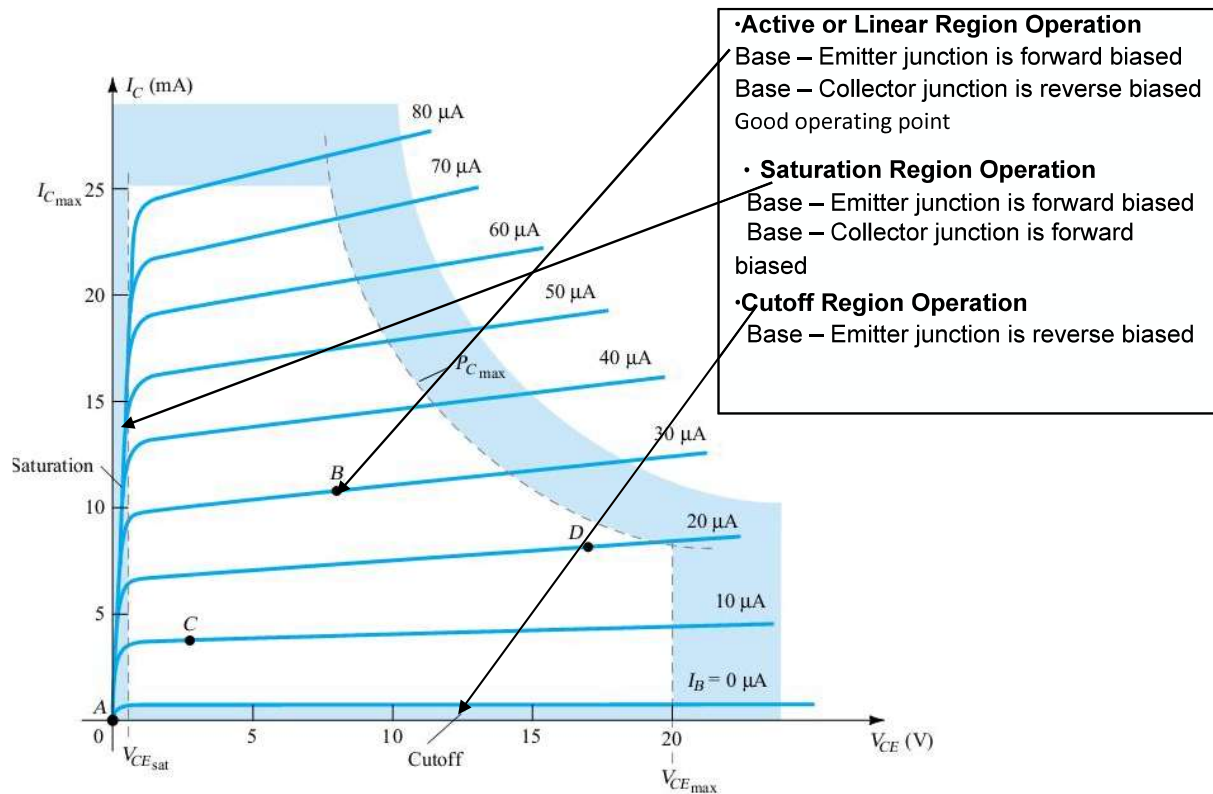


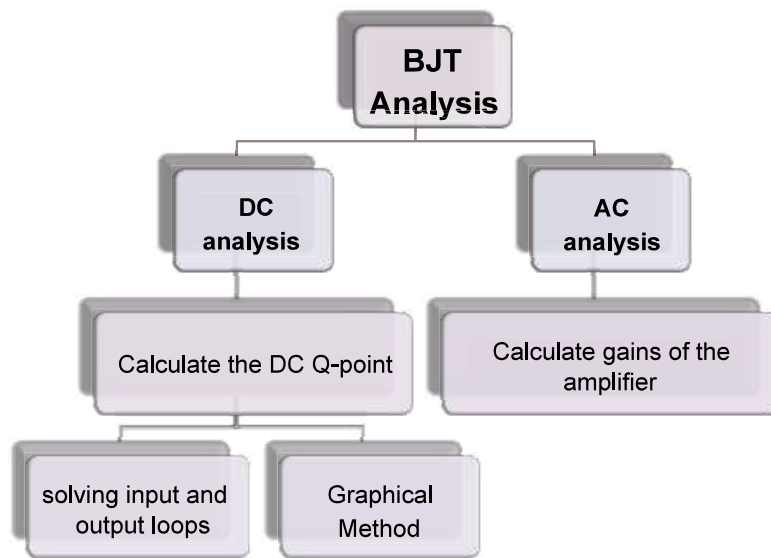

DC Biasing Circuits

- Fixed-bias circuit
- Emitter-stabilized bias circuit
- Collector-emitter loop
- Voltage divider bias circuit
- DC bias with voltage feedback


FIXED BIAS CIRCUIT

 

- This is common emitter (CE) configuration
- 1st step: Locate capacitors and replace them with an open circuit
- 2nd step: Locate 2 main loops which,
 - BE loop (input loop)
 - CE loop (output loop)


FIXED BIAS CIRCUIT

 - 1st step: Locate capacitors and replace them with an open circuit




FIXED BIAS CIRCUIT

- 2_{nd} step: Locate 2 main loops.

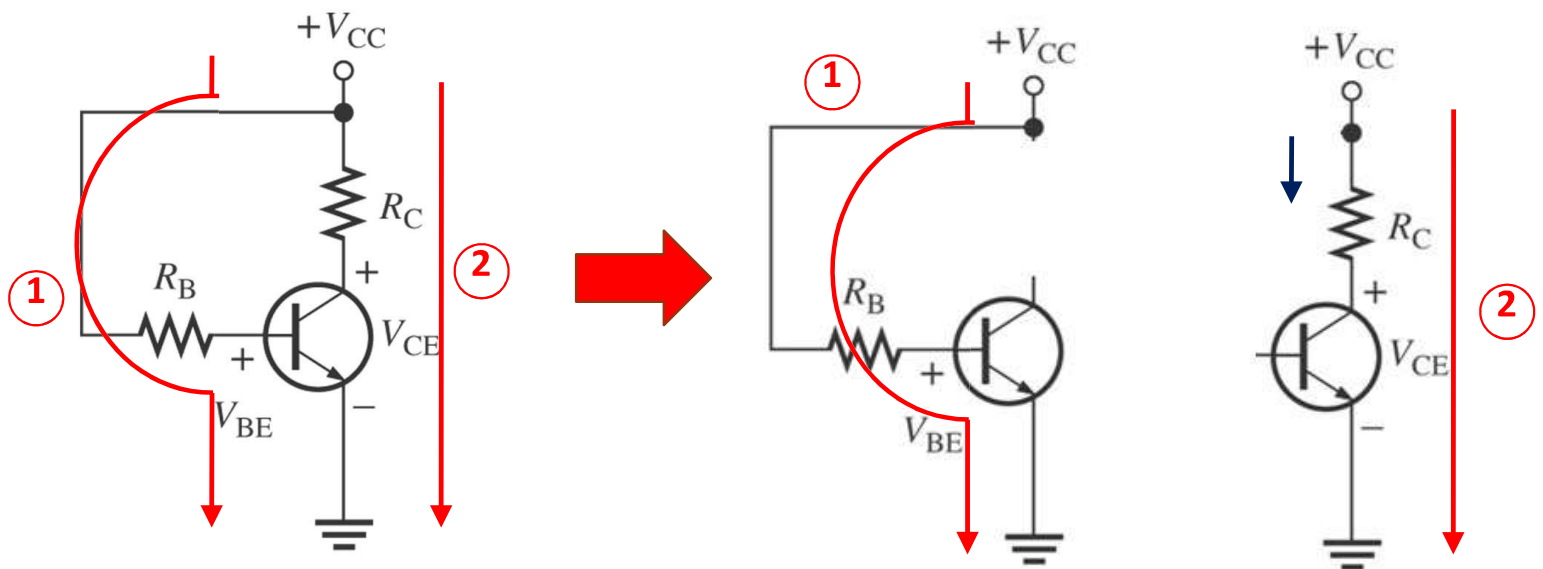

FIXED BIAS CIRCUIT

● BE Loop Analysis

 


■ From KVL;

$$\begin{aligned} -V_{CC} + I_B R_B + V_{BE} &= 0 \\ \therefore I_B &= \frac{V_{CC} - V_{BE}}{R_B} \quad \text{A} \end{aligned}$$

FIXED BIAS CIRCUIT

● CE Loop

Analysis

 

■ From KVL;

$$-V_{CC} + I_C R_C + V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

As we know;

$$I_C = \beta I_B$$

■ Substituting (A) with (B)

$$I_C = \beta_{DC} \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$

Note that R_C does not affect the value of I_C

FIXED BIAS CIRCUIT

● DISADVANTAGE


- Unstable – because it is too dependent on β and produce
- For improved bias stability, add emitter resistor to dc bias.



Load line analysis

A fixed bias circuit with given values of V_{CC} , R_C and R_B can be analyzed (means, determining the values of I_{BQ} , I_{CQ} and V_{CEQ}) using the concept of load line also.

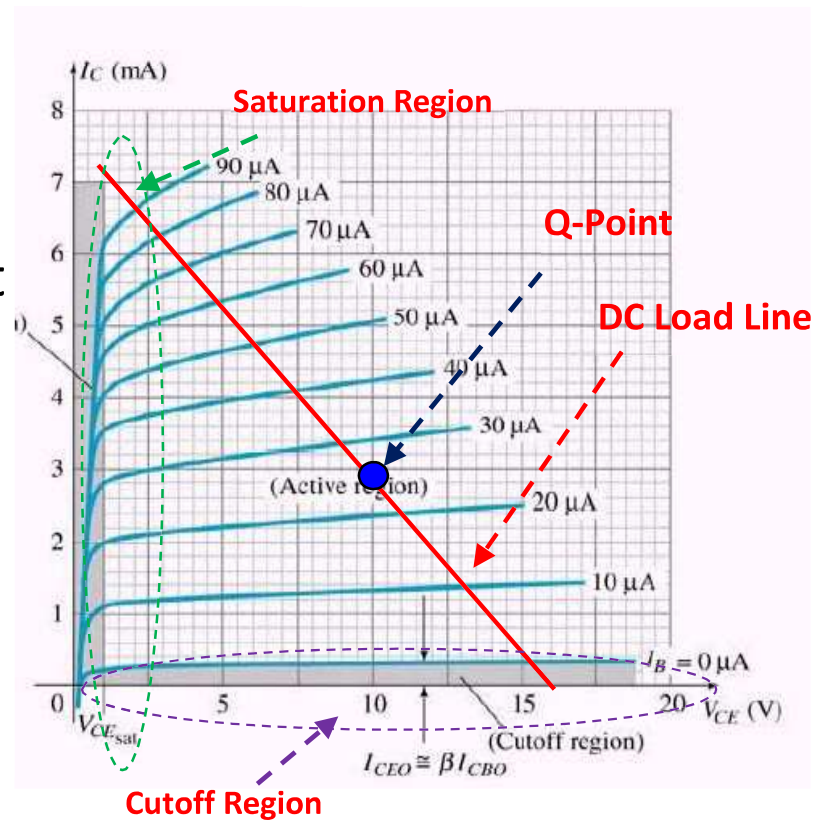Here the input loop KVL equation is not used for the purpose of analysis, instead, the output characteristics of the transistor used in the given circuit and output loop KVL equation are made use of.



□ Plot load line equation


$$V_{CE} = V_{CC} - I_C R_C$$

□ $I_{C(sat)}$ occurs when transistor operating in *saturation region*



$$I_{C(sat)} = \frac{V_{CC}}{R_C} \bigg|_{V_{CE} = 0}$$

□ $V_{CE(off)}$ occurs when transistor operating in *cut-off region*


$$V_{CE(off)} = V_{CC} - I_C R_C \bigg|_{I_C = 0}$$

 

Circuit Values Affect the Q-Point

  


Decreasing V_{CC}

 

Increasing R_C

Varying I_B


EMITTER-STABILIZED BIAS CIRCUIT

 

- An emitter resistor, R is added to improve stability
- 1st step: Locate capacitors, replace them with an open and circuit
- 2nd step: Locate 2 main loops which,
 - BE loop
 - CE loop


EMITTER-STABILIZED BIAS CIRCUIT

 - 1st step: Locate capacitors and replace them with an open circuit



EMITTER-STABILIZED BIAS CIRCUIT


- 2_{nd} step: Locate 2 main loops.

 

EMITTER-STABILIZED BIAS CIRCUIT

● BE Loop

Analysis

 

■ From kvl;

$$-V_{CC} + I_B R_B + V_{BE} + I_E R_E = 0$$

Recall; $I_E = (\beta + 1)I_B$

Substitute for I_E


$$-V_{CC} + I_B R_B + V_{BE} + (\beta + 1)I_B R_E = 0$$

$$\therefore I_B = \frac{-V_{CC} + V_{BE}}{R_B + (\beta + 1)R_E}$$

EMITTER-STABILIZED BIAS CIRCUIT

● CE Loop

Analysis

 

■ From KVL;

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

■ Assume;

■ $I_E \approx I_C$

■ Therefore;

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Improved Bias Stability

The addition of the emitter resistor to the dc bias of the BJT provides improved stability, that is, the dc bias currents and voltages remain closer to where they were set by the circuit when outside conditions, such as temperature, and transistor beta, change.

Without Re

$$I_c = \left(\frac{V_{CC} - V_{BE}}{R_B} \right) \beta$$


With Re

$$I_c = \left(\frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \right) \beta$$

Note : it seems that beta in numerator canceled with beta in denominator

VOLTAGE DIVIDER BIAS CIRCUIT

- Provides good Q-point stability with a single polarity supply voltage
- This is the biasing circuit wherein, I_{CQ} and V_{CEQ} are almost independent of β .
- The level of I_{BQ} will change with β to maintain the values of I_{CQ} and V_{CEQ} .
- **Exact method** can be applied to any voltage divider circuit
- **Approximate method** : direct method, saves time and energy,
- Two methods of analyzing a voltage divider bias circuit are.
 - 1st step: Locate capacitors and replace them with an open circuit
 - 2nd step: Simplified circuit using **Thevenin**
 - 3rd step: Locate 2 main loops which,
 - BE loop
 - CE loop

 


VOLTAGE DIVIDER

BIAS CIRCUIT

Thevenin Theorem

2nd step: : Simplified circuit using

 

Thevenin Theorem;

From Thevenin Theorem;

$$R_{TH} = R_1 // R_2 = \frac{R_1 \times R_2}{R_1 + R_2}$$



$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

VOLTAGE


BIAS CIRCUIT

DIVIDER


- 2nd step: Locate 2 main loops.

  

BE Loop

 


CE Loop

 

VOLTAGE DIVIDER BIAS CIRCUIT

● BE Loop

Analysis

 

■ From KVL;

$$-V_{TH} + I_B R_{TH} + V_{BE} + I_E R_E = 0$$

Recall; $I_E = (\beta + 1)I_B$

Substitute for I_E

$$-V_{TH} + I_B R_{TH} + V_{BE} + (\beta + 1)I_B R_E = 0$$


$$\therefore I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1)R_E}$$

VOLTAGE DIVIDER BIAS

CIRCUIT

● CE Loop

Analysis

 

■ From KVL;


$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

■ Assume; $I_E \approx I_C$

■ Therefore;

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Approximate analysis:

 

$$R_i \parallel R_2 \rightarrow I_{R2} \parallel I_{R1}$$

$$(\beta + 1)R_E \parallel R_2 \parallel R_1 \approx R_2 \parallel R_1$$


\Rightarrow

□ If this condition applied then you can use approximation method.

□ This makes IB to be negligible. Thus I1 through R1 is almost same as the current I2 through R2.

Thus R1 and R2 can be considered as in series.

 Voltage divider can be applied to find the voltage across R2 (VB)



Approximate Analysis

When $\beta R_E > 10 R_2$, Then $I_B \ll I_{E2}$ and $I_{E1} \cong I_{E2}$:

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$V_E = V_B - V_{BE}$$


$$I_E = \frac{V_E}{R_E}$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$I_E \cong I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

 


This is a very stable bias circuit. The currents and voltages are nearly independent of any variations in β .

DC Bias with Voltage Feedback

Another way to improve the stability of a bias circuit is to add a feedback path from collector to base.

 In this bias circuit the Q-point is only slightly dependent on the transistor beta, β .



Base-Emitter Loop

From Kirchhoff's voltage law:

$$-V_{CC} + I_C R_C + I_B R_B + V_{BE} + I_E R_E = 0$$

Where $I_B \ll I_C$:


Where $I_B \ll I_C$:

Knowing $I_C = \beta I_B$ and $I_E \approx I_C$, the loop equation becomes:

$$-V_{CC} - \beta I_B R_C - I_B R_B + V_{BE} - \beta I_B R_E = 0$$

Solving for I_B :
 
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$



Collector-Emitter Loop

Applying Kirchoff's voltage law:


$$I_E + V_{CE} + I_C' R_C - V_{CC} = 0$$

Since $I_C' \cong I_C$ and $I_C = \beta I_B$:

$$I_C (R_C + R_E) + V_{CE} - V_{CC} = 0$$

Solving for V_{CE} :

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

 

,f Pro'b\ e.w- - \c_vl,....._,." \ "i. • 12,ifo\ c,,(0 c, ~ ~
 <;o\ v\ d e i,ve_ 11 c e_d f {01 o<-J + wtool e: cl
 y (6f f_k: c_u LdYl>> le..-
 l,l~, 'f t~e yVtql, h at7e/<ll'o'V\ is ncl\, dbv"t°ctUS - S "1<:lk3
 . i
 J- ~5Juv1 Ue fh vt +~C.. t•ctll\ s, st-c, y' YJ, '° W ~(:
 e. f_cYt\, Jar-e: l 7 , -S Wl ad (;1 ~ , c-t, 'se: p(e
 -., I I; E, - et. C/7 If is J J~ '°) / Tc ,,,
 Q_ ~ t. L.,,,, J fh. c/, aAlb Lv f~ (Jl ta
 ~ & ce +", Ot. JfWMf+~
 3- ev~ie.. e. r e s ;« lt<~ <; j \~c: " \ r~si~to~,,;
 rf f~ c- (°vi l +~e. ' <f/v\ wt~ ~Cl. he. C . ~
 VcE > VcE (s, 1/6) a, re, f, u e, P~M~ f~ ~C-J \l. -"" \--
 °'- SJu (s & > vteGb. 1~ V , 'f , ~
 r e t, 0 ~ e, r\ . ~ e tr e, t_ V\ 5 \ S' t lS } r A-...., '5' cur-lb
 ~ , <, "C£ < o fkc: frc::u, l, jlf-r tj , ~
 f , - l. } \1'k~

4- If ^{5~1~} the initial assumption is proven incorrect
 then a new assumption must be made and
 the new circuit must be analyzed, Step 3
 must then be repeated.

بالمختصر: افرضنا active 2 تأكد من حالة التيارات اذا صح كل اذا خطا غير
 الفرضية وعلينا حل .

(\
)

}1,od<,

C\Llfk

) Ci.Aua, ,61

UAA, -//

r~=-~

'1/1

Tb = 5 &o

Tc.< "Sib

Ic.-= I

el{, ~,lc,,v!.)

Tb
'-JBE.

=-,t

'-Jge,~,?< dR ,l.

oJ\ |~ e w(f~
~ ("~| 'ti v<.

c~ ' O

$$I_E = I_B + I_C$$

Example 1: $V_{BE} = 0.7$, $\beta = 100$ find Q point

Assume active

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{10 - 0.7}{10k + (100 + 1)5k} = 1.1 \mu A$$


$$I_C = \beta I_B = 100 \times 1.1 \mu A = 1.1 mA$$

$$I_E = I_C + I_B = 1.21 mA$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 10 - 1.1 \times 10 - 1.21 \times 5 = 3.95 V$$

$$V_{CE} = 3.95 V$$

$$I_C = 1.1 mA, V_{CE} = 3.95 V$$


 


ملحوظات مفيدة
 ① حاول تنسيق المطلوب مع السؤال وابدأ بحل السؤال مباشرة
 واجب أن تنسق الإجابة بحسب
 ② حاول استخدام كل المعلومات المعطاة
 ③ دائماً أكتب input loop و output loop

[2]

$\sim \sim \parallel se$
 $C: I$
 $\{? \dots lo 0$
 $2..$
 $\sim \sim \sim \sim (2-) 5 \sim$
 $6 S' \sim \sim$
 $5 k I \tilde{f} \sim k < 5 k$

find Q points, I_L
 12

  

$ti \sim_0 - I_f + S \therefore g \cdot J) r,$
 $k \parallel k \parallel V (\sim, \therefore A$
 $-t-l) Jk$

le. @lb $s \sim uo \prime l. \prime 6 \cdot \sim, < JS \prime \prime A$
 $Z,$

$r \sim, r \sim, ci \sim J$

$\sim \{ J + 9 J b \sim$
 MA
 $\sim 6 \{ I_C + R_{th} + V_{CE} + 5k \times I_E - 5 = 0$

$\backslash JC. t \sim (\sim \sim S \sim 1 \cdot k - 5 \sim, g \sim 1 J$
 $\backslash - \therefore l.f.$

$"l \sim \sim \sim c. s \sim cc; -t \prime 1 \sim$
 $\sim C- -S, -, k J_{s:} -/=/-'$

$\sim \prime l_{c, r.} 3 \cdot D5$

$\overline{Cfl5} \therefore 11 = \frac{3-C}{fl} s, -=/t. \sim A.$

$\cdot \$(<$
 $;$

\cdot

\cdot

Q_1 :
if $v_B = 1$, find v_C, β, α

T..., .. 1 .. 1
 $\backslash c.c.k., \sim A \sim \cdot o_r \cdot i$

$\sim - \sim, \backslash 6t \sim - - , \backslash f B_s \backslash$

+ : \ < i , '1 c
 $\therefore J E 'I-s -$

15: 'J, < , '1
 $\therefore \underline{f} \underline{S_k} \cdot s \cdot (\cdot ' ' A$
 $\underline{\varepsilon}$


$\therefore I G - ; < (31 - ' \cdot P - : 1$

) $J_b 3^{1(5} < \backslash (o$

$\sim s, f s \sim - : \backslash f c t$
 $\{J, \cdot \backslash (i, L_j$

-
 $I c. \sim (3 \bar{T} 1 u ' J_{J o f o} \bar{6} = \{'$

 $r: \backslash \} c, \sim ' - l o \sim ; k, \dots \backslash . ' A$
 $\backslash, 0 - - I f \pi' \cdot, i' \cdot) \sim$
 $- = : Z$



4

$\{ \sim, \vdash, \vdash^* \} =$ "C.t. $S \sim S$: l 2
 \vdash, \vdash^*

$$\{t, t'\} = s$$
$$r_{i'} \sim_{\text{IS}}^{\text{7}} +_{S: i'} \text{ISJ M}$$

— 121 — w\

$$\frac{1}{2} \sum_{i=1}^n \frac{1}{i} \left(\frac{1}{i} - \frac{1}{i+1} \right) = \frac{1}{2} \sum_{i=1}^n \frac{1}{i(i+1)} = \frac{1}{2} \sum_{i=1}^n \left(\frac{1}{i} - \frac{1}{i+1} \right) = \frac{1}{2} \left(1 - \frac{1}{n+1} \right) = \frac{1}{2} \cdot \frac{n}{n+1} = \frac{n}{2(n+1)}$$
$$\frac{J_c}{I_c} = \beta I_b = 100 \times 1026 \times 10^{-3} = 2.6 \text{ m}$$

- $\sim_{C..C} \leq '1_{\sim \sim \sim}$

OU« C(JJvI"1'f;l'~
1? . ,./(~.


$$\therefore Q \sim \nu e_- \quad (\text{tr-s' StG''Y} \quad , \quad \sim \sim \sim , \sim \sim \quad J \quad , \quad)$$
$$\text{c.e.} \sim_{\perp} L$$
$$\mathbf{r}^{(CiM)} = \begin{bmatrix} z_1 & z_2 & \dots & z_n \\ \vdots & \vdots & \ddots & \vdots \end{bmatrix} \sim \mathcal{Z}_{n \times 1}(\boldsymbol{\mu}, \boldsymbol{\Sigma}), \mathbf{A}_{n \times p}$$
$$'' \sim , - , 2 , 2 , 1.5$$

[5]

Handwritten signature

Example:

find V_o , P_Z

 

••

--- ~'o - 'la f -

• - t.o' - q. e/
f q

'..T

M./1

^aL,

(~ 1..
lf

S.;S
lo.-=7

q.'f || ~ fl

Tet

= 1.2k

~

$$I_C \approx I_E = 5.55 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{5.55 \times 10^{-3}}{150} \approx 37 \mu\text{A}$$

$$I_Z = I_R - I_B = 9.416 \times 10^{-3} - 37 \times 10^{-6} = 9.379 \text{ mA}$$

$$P_Z = 10.7 \times 9.379 \text{ m} = 100.36 \text{ mW}$$

[6]

16

$$\begin{array}{cc} \bullet & \bullet \\ \sim & \sim \end{array}$$

$$\frac{-,7 + 10}{100k} - \frac{10 + ,7}{100k} = ,093 - ,107 = -,014mA$$

$I_b = -104 \mu A \rightarrow$ X wrong assumption

The transistor is cut-off

$\mathbf{J} = \begin{pmatrix} 0 & 1 \\ -1 & 0 \end{pmatrix}$
 $I_c = 1$
 $T = 1$
 $V_t = 0$
 $V_c = -10$
 $V_D = 0$

$$G_{lu} \sim \frac{1}{\sqrt{2}} \left(\frac{1}{\sqrt{2}} \right) \sim \frac{1}{2}$$

-\\-+ -z."Tt -t\\uokTb T1"t+l k.TEs ..

- $T_u = (\tau + \mathbf{r}_b)$

1b-; Lo-, 1-

6 ,oi..l,,,,,4


$$1 \leq j \leq k, \quad \text{if } (\sim t \sim \{k + 1, k - 1\})$$

$$T_{\text{eff}} = \frac{1}{1 + \frac{1}{\alpha} \ln \left(\frac{1}{1 - \alpha} \right)} \approx 1 - \frac{1}{\alpha} \ln \left(\frac{1}{1 - \alpha} \right)$$

$$\mathcal{C}_{\{i\}}^b; \quad {}^b 2..31_{w..A}$$

$$\approx_{CE} \cdot \log_{10} \frac{1.5}{1.1} \approx 0.17$$

[illegible]

  $\sim c,$ 

لاحظ هذه الدائرة مستحبه التصير

[7]

Example: find ϕ

$$I_1 = I_b + 20 \mu A$$

$$-104 \text{ k} (I_1 + I_c) + 100 \text{ k} \times J_1 = 750$$

$\frac{1}{2} \left(\frac{1}{2} + \frac{1}{2} \right) = 1$


$$r^b = [0, 1] \times f = I(0, 1, c_w) / 1$$

~ to ~ %.. -t t <> q
I< i Lok k
\.I,J'(tos

-S

M

[illegible]

 

Example: find ϕ

$$-V_0 - I_b R_b - I_b R_c + (\beta + 1) I_b R_e = 0$$


$$\dots 11. I_c, 1 - \sim @$$

$$\therefore \sim \dots = e J, f \dots f? J I$$

$$- b k \sim \} \setminus +, f 1' (\sim r \setminus) 11 b 10 y \{ L$$

$$\sim \dots ((1 + \dots) T b \setminus^*$$

$$1 \dots, 1 b i k x < \dots (Q i$$

 

$$-V_0 - I_b R_b - I_b R_c + (\beta + 1) I_b R_e = 0$$

$$I_c = \beta I_b$$

$$\sim I_f \dots k \dots a k$$

$$\therefore \setminus, \setminus (J'' 9 l. Lo$$

$$I_b \dots S \dots M \sim$$

$$I_i \dots 10 \lg \dots A \dots 11 - 10 \lg C f \dots w,$$

$$\{ C, C : I_{ij} \dots 10 \lg \dots (i)) \dots \sim 2 \dots q M)$$

$$S I' ($$

$$-(x t \sim$$

$$\dots, O_0 ? t l o$$

$$'s l.$$

[9]

ttv1 Q

$$\sim J > u. \quad \text{ct } \mathbb{H}^n \sim$$
$$z_{\text{eff}} = v_{A \sim e}$$

u...-e

C:\accv.\:

$$\therefore \sim e..vl < - \sim V_{je,r} \circ -ff\{'''$$
 $\sim |c/V|$

////

1.1.1

$$y^3 \tilde{q}^c_{if} \langle X_{\text{vf}} \rangle_{\text{u}}^{(l, 1-\epsilon)} \rangle$$
$$\log \sim$$

c' S c/ ~

'110 x

~d

 $\circ'_{-}(f$
$$I(\lambda \sim$$

L'QVW

$$w_{l, \sim} : V \rightarrow Q \otimes J_{\sim}.$$
$$\{ \phi_1, \dots, \phi_n \} \in S, \quad \phi_i = \frac{r_i}{\|r_i\|} \quad (8)$$
$$\sim 'o\backslash:z: "f_{so_2} '1. f.: ', \wedge, -, 1 \quad i \cdot \parallel$$
$$J_E = \langle i, \dots, j \rangle \sim \text{osk. } LW \setminus Tc..$$

$$V_{CE} = V_S - 2m(10k + 4.05k) = -13.14 \therefore \Rightarrow$$

our assumption is wrong the transistor is saturation \rightarrow Residue

~ 0...ss\..t. y«u/'''~ ,:,.....

~C:

~ -- \lc.<.(5-v\)\ s l(..

 O'

"1 ~)

 ~ 0

C::t

R

C.E.

"1 = S - I ~ (j ~) S (~ :S \ V C J + m m > Q
lok + 4.05k 10 + 4.05

(

• ,

 $S \sim$

[10]

Example: (PNP).

UeG--k

$f_{f.t} \text{ cat } t \sim q, S'' \times Z / < / L_0$


'> :s ~(.)" \forall k t.. to k

~ 'idk s g

$$V_E = 8.7$$

$$I_E = \frac{10.7 - 8.7}{2k} = 1m$$
 
$$V_{CE} = 10.7 - 8k \times 1m = 9.7 > V_{CE(sat)}.$$





11

ANALOG CIRCUITS

**Presented By,
G.R.Mahendra Babu,
Assistant Professor,
Dept of ECE / FoE / KAHE**

High Frequency BJT Model

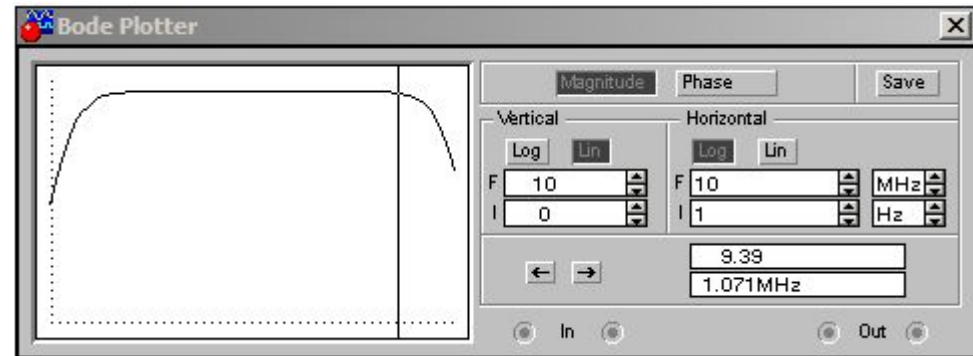 Gain of 10 Amplifier – Non-ideal Transistor




Gain starts dropping at about 1MHz.


Why!

Because of internal transistor capacitances that we have ignored in our models.

 Sketch of Typical Voltage Gain Response for a CE Amplifier



High Frequency Small-signal Model

 

SPICE
CJC = $C_{\mu 0}$
CJE = C_{je0}
TF = τ_F
RB = r_x

Two capacitors and a resistor added.

A base to emitter capacitor, C_{π}

A base to collector capacitor, C_{μ}

A resistor, r_x , representing the base terminal resistance ($r_x \ll r_{\pi}$)

$$C_{\pi} = \frac{C_{\pi 0}}{1 - \frac{V_{BE}}{V_{0e}}} \approx C_{\pi 0} \left(1 + \frac{V_{BE}}{V_{0e}} \right) \approx C_{\pi 0} \left(1 + \frac{I_C}{I_{S0}} \right) = C_{\pi 0} \left(1 + \beta_F \right)$$

τ_F = forward-base transit time


High Frequency Small-signal Model

The internal capacitors on the transistor have a strong effect on circuit high frequency performance! They attenuate base signals, decreasing v_{be} since their reactance approaches zero (short circuit) as frequency increases.

As we will see later C_μ is the principal cause of this gain loss at high frequencies. At the base C_μ looks like a capacitor of value $k C_\mu$ connected between base and emitter, where $k > 1$ and may be $\gg 1$.

This phenomenon is called the *Miller Effect*.

Frequency-dependent “beta” h

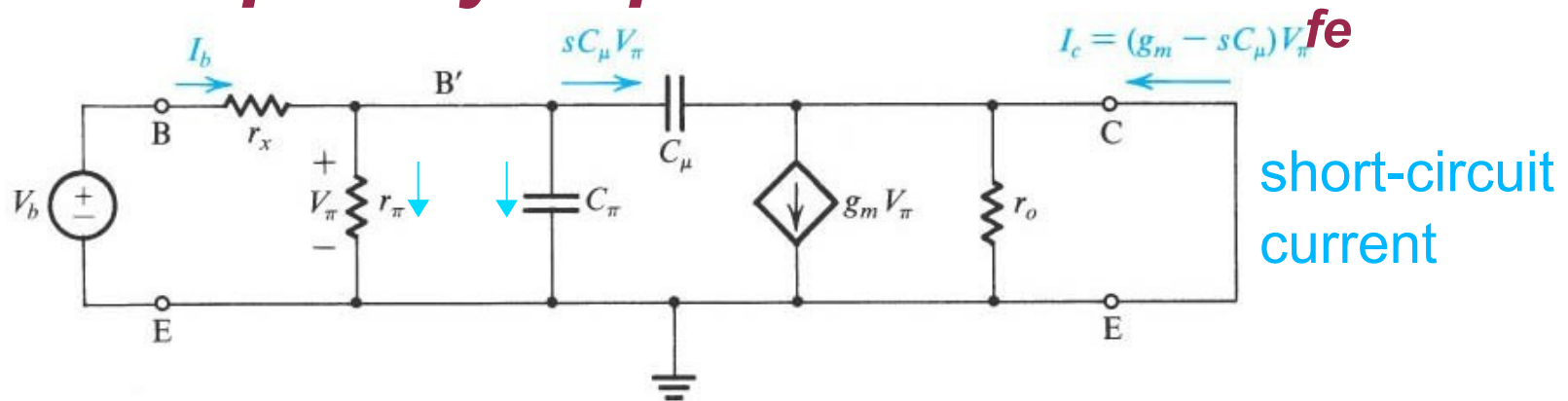

The relationship $i_c = \beta i_b$ does not apply at high frequencies $f > f_H$!

Using the relationship $i_c = f(V_\pi)$ – find the new relationship


between i_c and i_b . For i_b (using π)

phasor notation (I_x & V_x) for frequency domain analysis:

@ node B':
$$\frac{1}{r_\pi} V_\pi + s C_\pi V_\pi = I_b$$
 where $r_x \approx 0$ (ignore r_x)

NOTE: $s = \sigma + j\omega$, in sinusoidal steady-state $s = j\omega$.

Frequency-dependent h_{fe} or “beta”

 

$I_b = \frac{1}{r_{\pi}} V_{\pi} + s C_{\pi} V_{\pi} + s C_{\mu} V_c$ @ node C: $I_c = g_m V_{\pi} - s C_{\mu} V_{\pi}$ (ignore r_o)

Leads to a new relationship between the I_c and I_b :

$$h_{fe} = \frac{I_c}{I_b} = \frac{g_m - s C_{\mu}}{\frac{1}{r_{\pi}} + s C_{\pi} + s C_{\mu}}$$

Frequency Response of h_{fe}

$$h_{fe} = \frac{g_m - sC_c}{\frac{1}{r} + sC_c + sC_e}$$

multiply N&D by r and set $s = j\omega$

$$h_{fe} = \frac{r g_m - j r C_c}{1 + j r C_c + j r C_e}$$

factor N to isolate g_m

$$h_{fe} = \frac{1 - j \frac{C_c}{g_m r}}{1 + j \frac{C_c}{g_m r} + j \frac{C_e}{g_m r}} g_m r$$

$$g_m = \frac{I_C}{V_T} \quad r = \frac{V_T}{I_C}$$

For small ω : $\omega \ll \frac{g_m}{C_c} \ll \frac{1}{10}$

and: $\omega \ll \frac{1}{r C_c} \ll \frac{1}{10}$

Note: $\omega \ll \frac{1}{r C_c} = \frac{g_m}{C_c} \gg \frac{1}{g_m r}$


We have:

$$h_{fe} = g_m r$$

Frequency Response of h_{fe} cont.

$$h_{fe} = \frac{(1 - j\omega C_{\pi} r_{\pi}) g_m}{1 - j\omega C_{\pi} r_{\pi}} = \frac{g_m r_{\pi}}{1 - j\omega C_{\pi} r_{\pi}} = \frac{g_m r_{\pi}}{1 - j\omega C_{\pi} r_{\pi}}$$
 
$$\frac{C_{\pi} r_{\pi}}{g_m} \gg \frac{C_{\mu}}{g_m} \Rightarrow f_z \gg f_{\beta}$$



Hence, the lower break frequency or $-3dB$ frequency is f_{β}

$$f_{\beta} = \frac{1}{2\pi C_{\pi} r_{\pi}} = \frac{g_m}{2\pi C_{\pi}} \quad \text{the upper:} \quad f_z = \frac{1}{2\pi C_{\mu} / g_m} = \frac{g_m}{2\pi C_{\mu}}$$

where $f_z \gg 10 f_{\beta}$

Frequency Response of h_{fe} cont.

Using Bode plot concepts, for the range where: $f \ll f_z$

$$h_{fe} = g_m r_{\pi}$$

For the range where: $f \ll f_z$ s.t. $|1 - jf/f_z| \approx 1$

We consider the frequency-dependent numerator term to be 1 and focus on the response of the denominator:

$$h_{fe} = \frac{g_m r_{\pi}}{1 - j \frac{f}{f_z}}$$

Frequency Response of h_{fe} cont.

Neglecting numerator term:

$$h_{fe} = \frac{g_m r_{\pi}}{1 + j \frac{f}{f_{\pi}}}$$

And for $f/f_{\pi} \gg 1$ (but $< f/f_z$):

$$|h_{fe}| \approx \frac{g_m r_{\pi}}{f/f_{\pi}}$$

Unity gain bandwidth: $|h_{fe}| = 1 \Rightarrow \frac{f}{f_{\pi}} = 1 \Rightarrow f = f_{\pi}$

$$f_T = \frac{f_{\pi}}{2} = f_{\pi}$$

BJT unity-gain frequency or GBP

Frequency Response of h_{fe} cont.

$$\beta = 100 \quad r_{\pi} = 2500 \, \Omega \quad C_{\pi} = 12 \, \text{pF} \quad C_{\mu} = 2 \, \text{pF} \quad g_m = 40 \times 10^{-3} \, \text{S}$$

$$\omega_{\pi} = \frac{1}{C_{\pi} r_{\pi}} = \frac{1}{12 \times 10^{-12} \times 2500} = 28.57 \times 10^6 \, \text{rps}$$

$$f_{\pi} = \frac{\omega_{\pi}}{2\pi} = \frac{28.57}{6.28} \times 10^6 \, \text{Hz} = 4.55 \, \text{MHz} \quad f_T = \omega_{\pi} \quad f_{\mu} = 455 \, \text{MHz}$$


$$\omega_z = \frac{g_m}{C_{\mu}} = \frac{40 \times 10^{-3}}{2 \times 10^{-12}} \, \text{Hz} = 20 \times 10^9 \, \text{rps}$$

$$f_z = \frac{\omega_z}{2\pi} = 3.18 \times 10^9 \, \text{Hz} = 3180 \, \text{MHz}$$


Scilab f_T Plot

```
//fT Bode Plot
Beta=100;
KdB= 20*log10(Beta);
fz=3180;
fp=4.55;
f= 1:1:10000;
term1=KdB*sign(f); //Constant array of len(f)
term2=max(0,20*log10(f/fz)); //Zero for f < fz;
term3=min(0,-20*log10(f/fp)); //Zero for f < fp;
BodePlot=term1+term2+term3;
plot(f,BodePlot);
```

h_{fe} Bode Plot

 


Multisim Simulation

 


Insert 1 ohm resistors – we want to measure a current ratio.

$$h_{fe} = \frac{I_c}{I_b} = \frac{g_m - s C_{\mu}}{\frac{1}{r_{\pi}} + s C_{\pi}}$$

Simulation Results

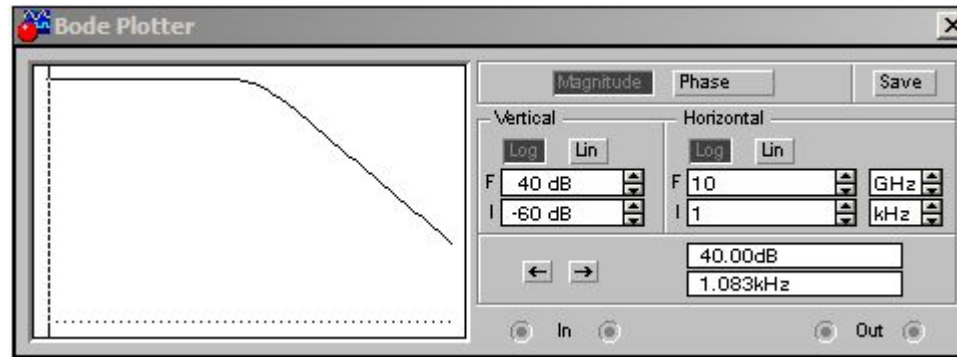

Low frequency $|h|$
 f_e

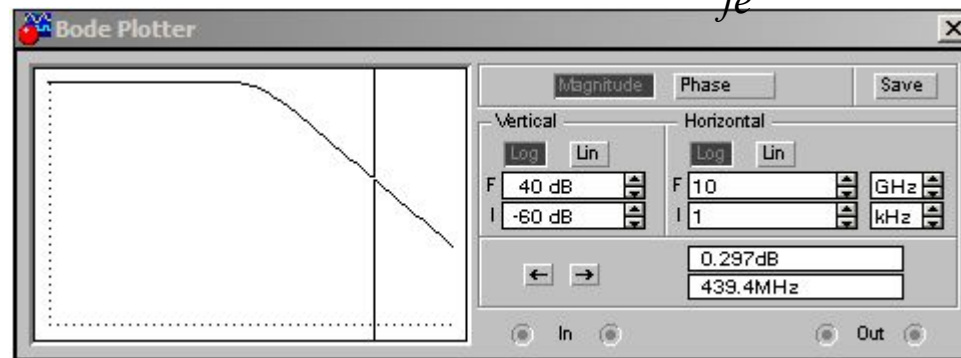

Unity Gain frequency about **440 MHz**

Theory:

$$f_T = \frac{1}{2\pi} \frac{g_m}{C_{eq}} = 455 \text{ MHz}$$



ANALOG CIRCUITS

**Presented By,
G.R.Mahendra Babu,
Assistant Professor,
Dept of ECE / FoE / KAHE**

Feedback and Oscillators

9.1 Effect of Feedback on Gain

Closed-Loop Gain

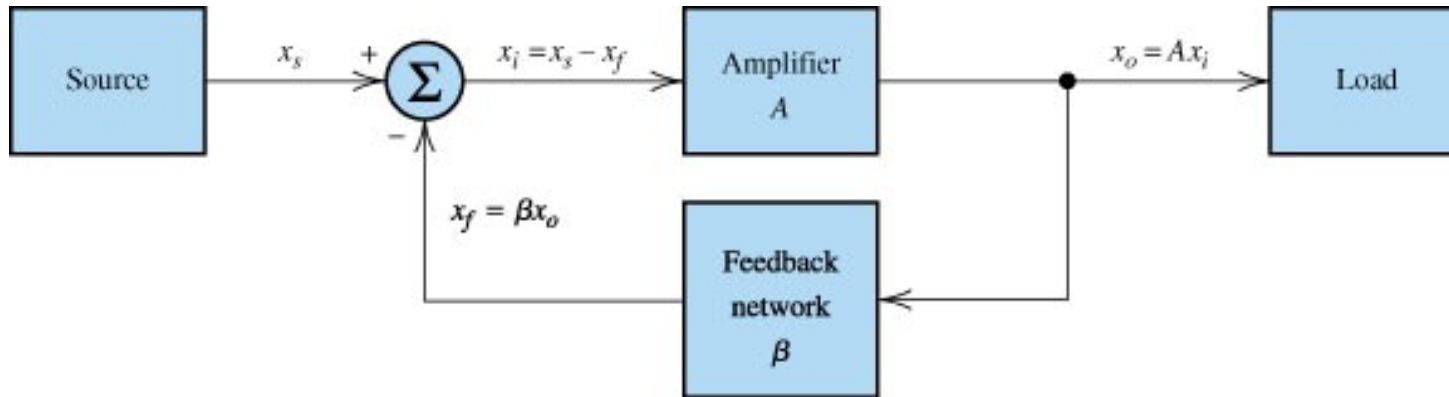


Figure 9.1 Feedback amplifier. Note that the signals are denoted as x_s , x_i , x_o , and so on. The signals can be either currents or voltages.

$$x_i = x_s - \beta x_o$$

$$x_o = A(x_i - \beta x_o)$$

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + A\beta} \quad (9.1)$$

A_f – closed-loop gain;

A – open-loop gain;

$A\beta$ – loop gain;

If $A\beta > 0$ – negative feedback;

if $A\beta < 0$ – positive feedback.

Problems Associated With Positive Feedback

$$A_f = \frac{x_o}{x_s} = \frac{A}{1 + A\beta} \quad (9.1)$$

1. Positive feedback:

Let $A = -10$; $\beta = 0.099$. $A_f = -104$.

Let $A = -9.9$; $\beta = 0.099$. $A_f = -901$.

1% change of A causes 91% change of A_f .

2. Negative feedback:

Let $A = 10^4$; $\beta = 0.01$. $A_f = 100$.

Let $A = 9000$; $\beta = 0.01$. $A_f = 98.9$.
10% change of A causes 1% change of A_f .

Conclusion: *Positive feedback* increases the gain, but the gain is unstable. In contrast *negative feedback* decreases the gain and stabilizes it.

Gain Stabilization

$$\frac{dA_f}{A_f} = \frac{1 + A\beta - A\beta}{(1 + A\beta)^2} = \frac{1}{(1 + A\beta)^2} \frac{dA}{A}; \quad \frac{dA_f}{A_f} = \frac{A}{1 + A\beta} \frac{dA}{A}$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \frac{A}{1 + A\beta}$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \frac{1}{1 + A\beta} \quad (9.2)$$

dA_f/A_f – relative instability of the closed-loop gain;

dA/A – relative instability of the open-loop gain.

Exercise

9.2 (a) An amplifier has $A = 10^5 \pm 10\%$. Suppose that we want a feedback amplifier with A_f that varies by no more than $\pm 1\%$ due to variations in A . What is the maximum value of nominal gain A_f allowed?
(b) Repeat if A_f is allowed to vary by only $\pm 0.1\%$.

Solution:

(a) In (9.2)

$$\frac{dA}{A_f} = \frac{dA}{A} \frac{1}{(1 + A\beta)} \tag{9.2}$$
$$\frac{dA}{A} = 10\% = 0.1; \quad \frac{dA_f}{A_f} = 1\% = 0.01$$
$$0.1 = 0.01 \frac{1}{(1 + A\beta)} \Rightarrow (1 + A\beta) = 10;$$


Since $A = 10^5$ the maximum gain with variation less than 1% is

$$A_f = \frac{A}{1 + A\beta} = \frac{10^5}{10} = 10^4$$


(b)

$$\frac{dA}{A} = 10\% = 0.1; \quad \frac{dA_f}{A_f} = 0.1\% = 0.001$$
$$0.1 = 0.001 \frac{1}{(1 + A\beta)} \Rightarrow (1 + A\beta) = 100;$$
$$A_f = \frac{A}{1 + A\beta} = \frac{10^5}{100} = 10^3$$

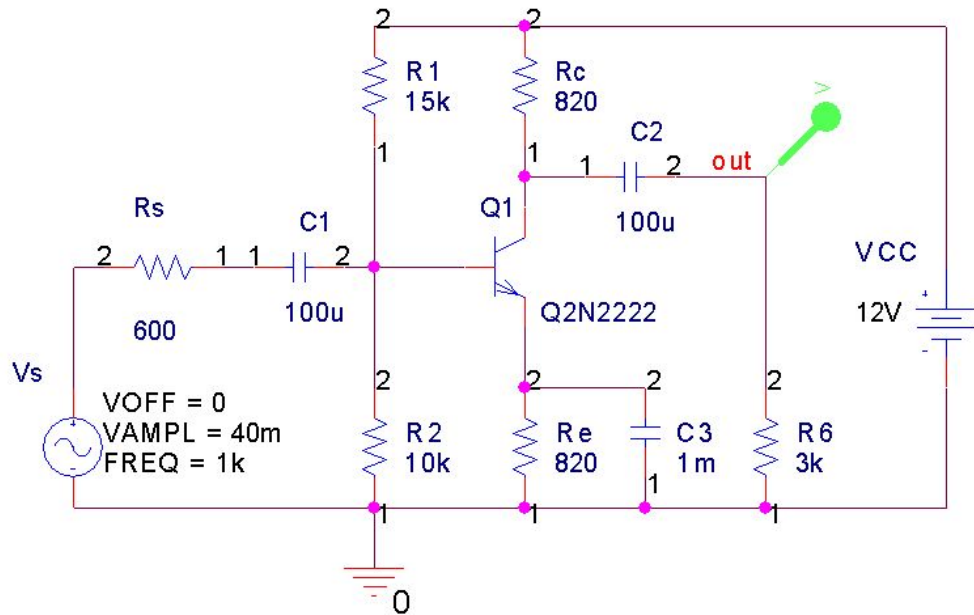9.2 Reduction of Nonlinear Distortion and Noise



 A circuit of common-emitter amplifier from BAC exercises (Exercise 8) and its output waveshape. The signal at the output is distorted.



The distortion of the output signal is basically due to the curvature of the input characteristic of the BJT.

The output signal is not any more sinusoidal and has harmonics.

Figure of merit of the distortion: the amplitudes of the harmonics.

Total harmonic distortion (THD:

$$THD = \frac{\sqrt{V_2^2 + V_3^2 + V_4^2 + \dots}}{V_1}$$

V_1 – amplitude of the fundamental harmonic;
 V_2, V_3, \dots – amplitudes of the higher harmonics.

 


Figure 9.2 Transfer characteristic of a certain nonlinear amplifier.

Gain of the nonlinear amplifier in Figure 9.2:

- if $0 < x_i < 10$; $A = 10$;
- if $-10 < x_i < 0$; $A = 5$.

 


Figure 9.3 Output of amplifier of Figure 9.2 for $x_{in} = \sin(\omega t)$. Notice the distortion resulting from the nonlinear transfer characteristic.

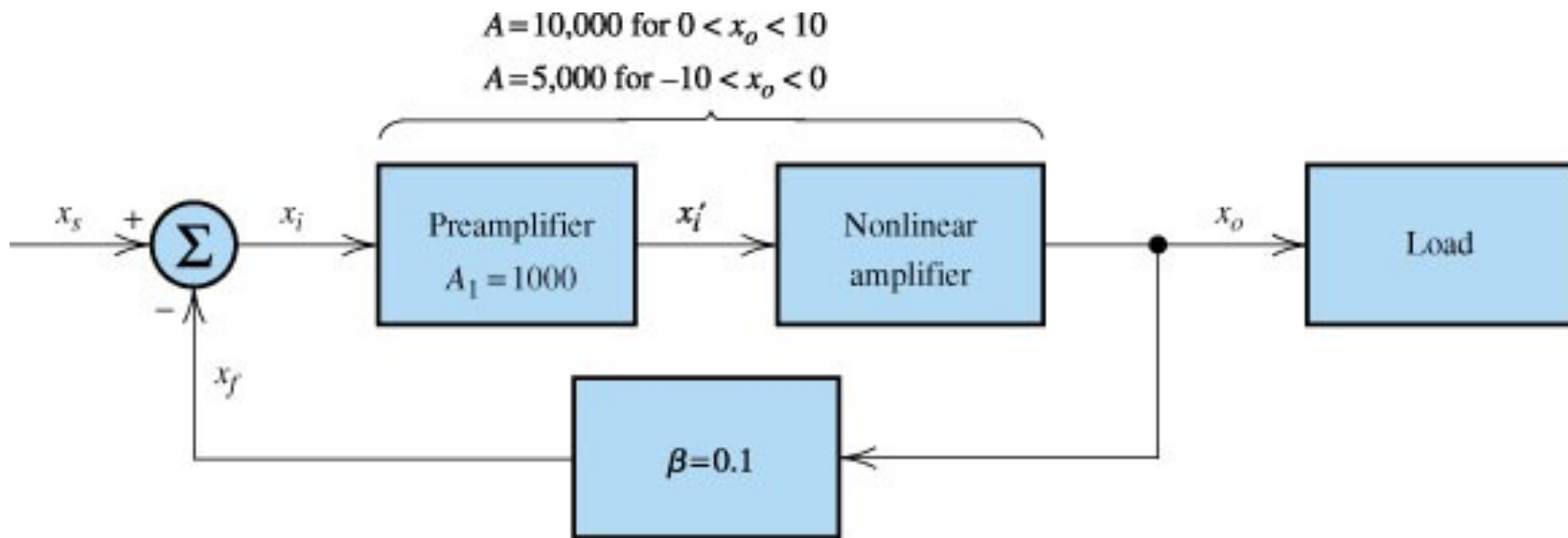


Figure 9.4 Addition of a linear high-gain preamplifier and negative feedback to reduce distortion.

Open loop gain of the cascade of preamplifier and nonlinear amplifier:

- if $0 < x_i < 10$; $A = 10^4$;
- if $-10 < x_i < 0$; $A = 5000$.

Closed loop gain of the whole amplifier:

- if $0 < x < 10$

$$A_f = \frac{A}{1 + A\beta} = \frac{10^4}{1 + 10^4 \times 0.1} = 9.99$$

- if $-10 < x < 0$

$$A_f = \frac{A}{1 + A\beta} = \frac{5000}{1 + 5000 \times 0.1} = 9.98$$

Compensatory Distortion of the Input Signal

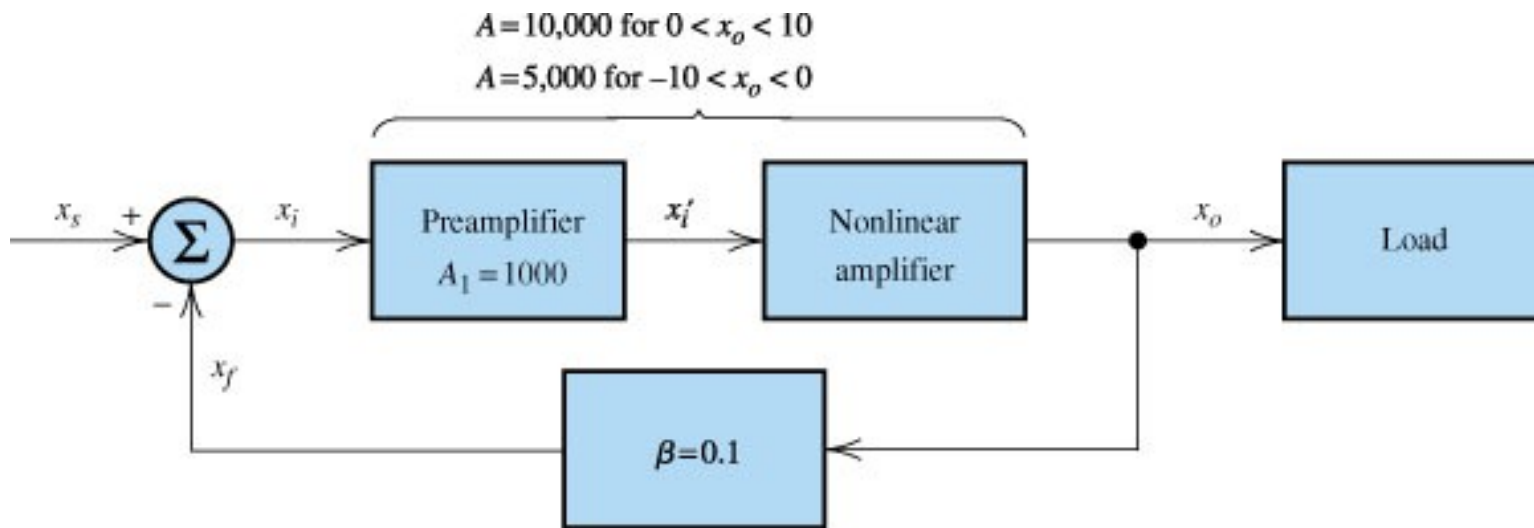


Figure 9.4 Addition of a linear high-gain preamplifier and negative feedback to reduce distortion.

$$x_i = x_s - x_f \frac{A\beta}{1 + A\beta} \quad (9.4)$$

$$x_i = x_s \frac{1}{1 + A\beta} \quad (9.5)$$

$$x_i = x_s / 1001 \quad \text{for } 0 < x^i < 10^{-3}$$

$$x_i = x_s / 501 \quad \text{for } -2 \times 10^{-3} < x^i < 0$$

 


Figure 9.5 Predistorted input signal.

An Example with Crossover Distortion

 


Figure 9.7 Nonlinear class-B power amplifier.

$$v_o = v_s - 0.6 \quad \text{for} \quad v_s > 0.6$$

$$v_o \cong v_s + 0.6 \quad \text{for} \quad v_s < -0.6$$


 


Figure 9.8 Transfer characteristic for the amplifier of Figure 9.7.

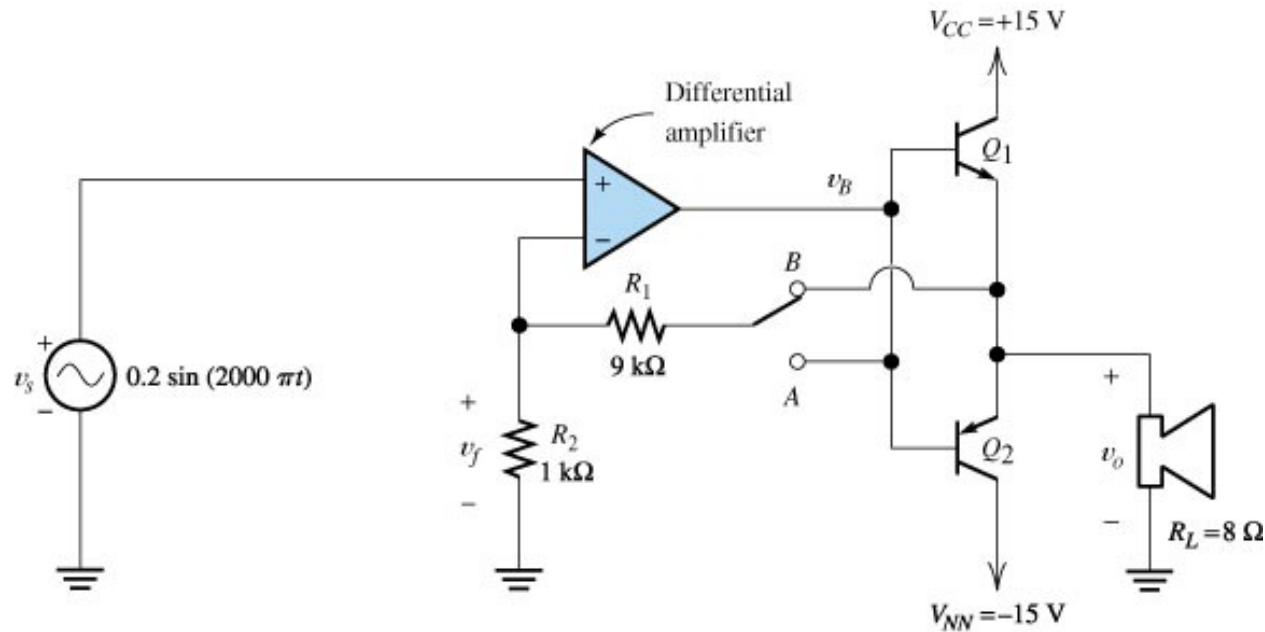

(a) Circuit diagram

Figure 9.9a Class-B power amplifier with feedback. The feedback has effect to reduce the distortion if the source of the distortion is included in the feedback loop. In the circuit above the switch must be in position B. If the switch is in position A, the feedback has no effect on the distortion.

Influence of the Feedback on the Noise in Amplifiers

Noise – a random signal, generated in the circuit or penetrating from outside in the circuit. The noise adds to the desired signal and deteriorates its quality. The noise generation in the circuit is basically due to the transfer of the current by charged particles (electrons and holes) and the thermal agitation.

All electronic elements, except capacitors and inductors generate noise.

Generally the **negative feedback doesn't reduce the noise in the amplifier**, since the feedback also generates noise.

The negative feedback can help in some particular cases, when the source of the noise is localized in one stage of the circuit only. Then including this stage in a feedback loop reduces the noise.

 



Figure 9.13 Feedback amplifier with a noise source. The noise is generated in one stage of the circuit (A_1) and the feedback can reduce this noise only.

9.3 Input and Output Impedance

Types of Feedback


Conditionally the feedback is divided in 4 types:

 - series voltage;
- series current;
- parallel voltage;
- parallel current.



(a) Series voltage feedback

Figure 9.14 Types of feedback. (a) Series voltage feedback.

 

(b) Series current feedback

Figure 9.14 Types of feedback. (b) Series current feedback.

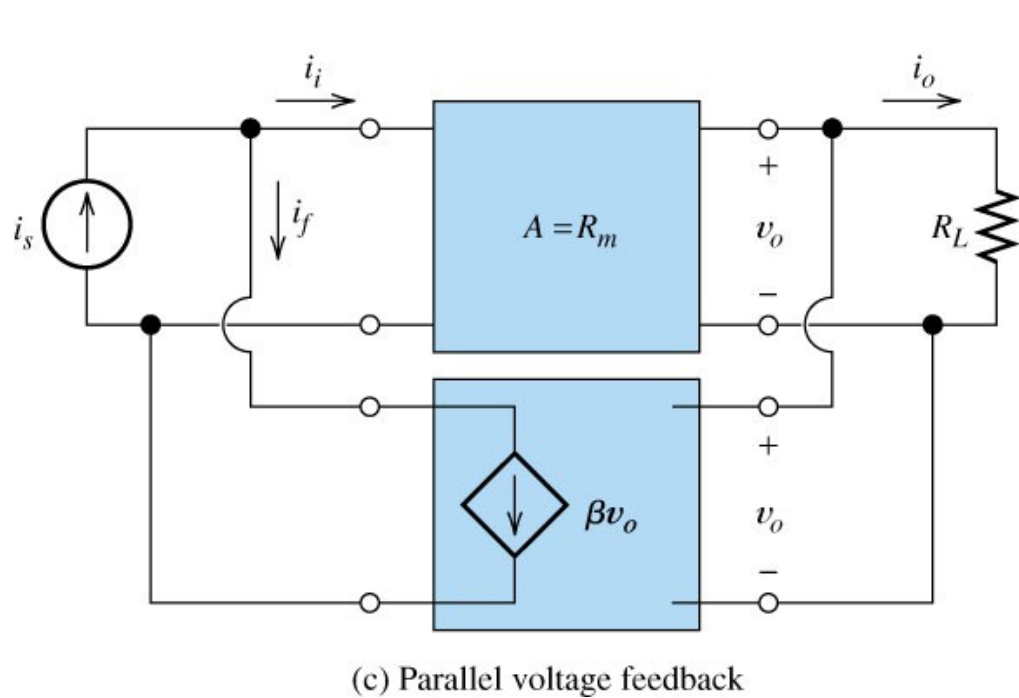


Figure 9.14 Types of feedback. (c) Parallel voltage feedback.

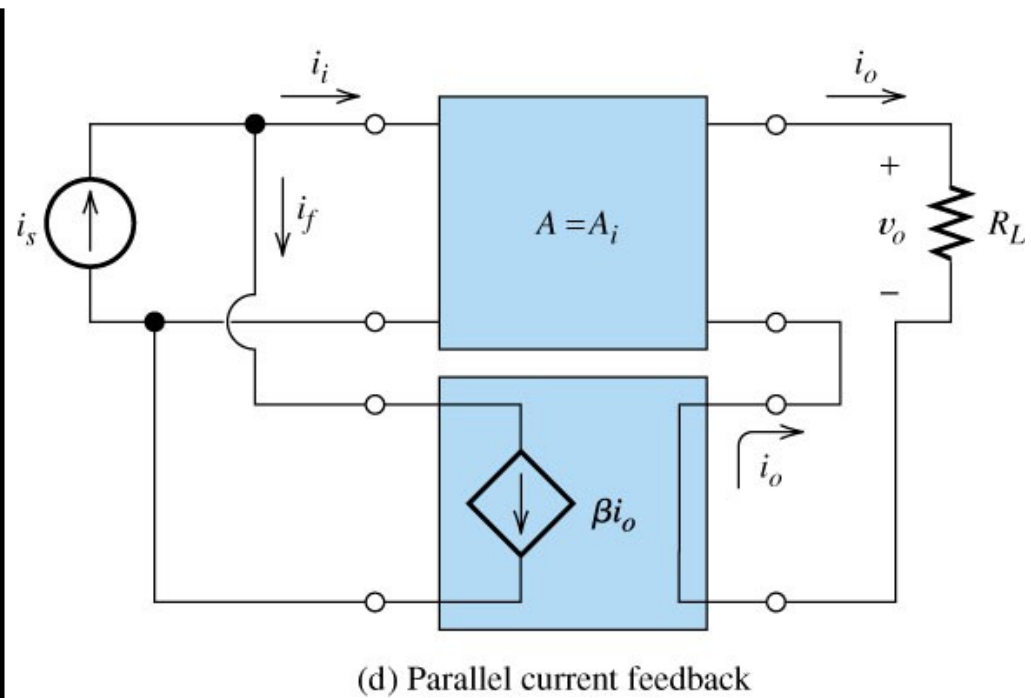


Figure 9.14 Types of feedback. (c) Parallel current feedback.

The Effects of Various Types of Feedback on Gain

The general formula

$$A_f = \frac{x_o}{x_s} = 1 + \frac{A}{A\beta}$$

is valid for all feedback types. For the different feedback types the gains assumed as A , A and β are different quantities.

For series voltage feedback: $x_o = v$, $x_s = v$.

A , A and β are voltage gains. A_o , A_s , β_s

For series current feedback: $x_o = i$, $x_s = v$. A_o and A_s are transconductances: $G_o = i_o / v$; $G_s = i_s / v$;

β^f is a transresistance: $\beta = v / i$. β_m , β_o , β_s

For parallel voltage feedback: $x_o^f = v$, $x_s = i$.

A_o and A_s are transresistances: $R_o = v / i_o$; $R_s = v / i_s$;

β^f is a transconductance: $\beta = i / v$. β_o , β_s , β_f

For parallel current feedback: $x_o = i_o$, $x_s = i_s$.

A_o , A_s and β are current gains. A_o , A_s , β_f

The Effects of Series Feedback on Input Impedance

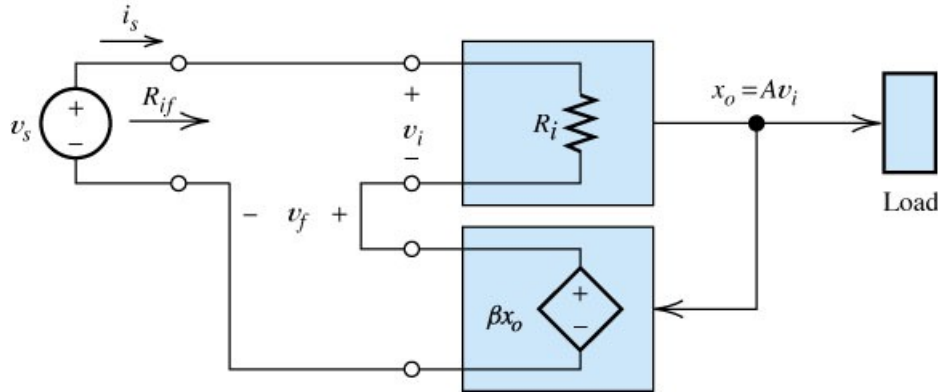


Figure 9.15 Model for analysis of the effect of series feedback on input impedance.

$$R_{if} = \frac{v_s}{i_s} = R_i (1 + A\beta) >$$

The series feedback increases the input impedance.

The Effects of Parallel Feedback on Input Impedance

 


Figure 9.16 Model for analysis of the effect of parallel feedback on input impedance.

$$R_{if} = \frac{v_s}{i_s} = \frac{R_i}{1 + A\beta} < R_i$$

The parallel feedback decreases the input impedance.

The Effects of Voltage Feedback on Output Impedance

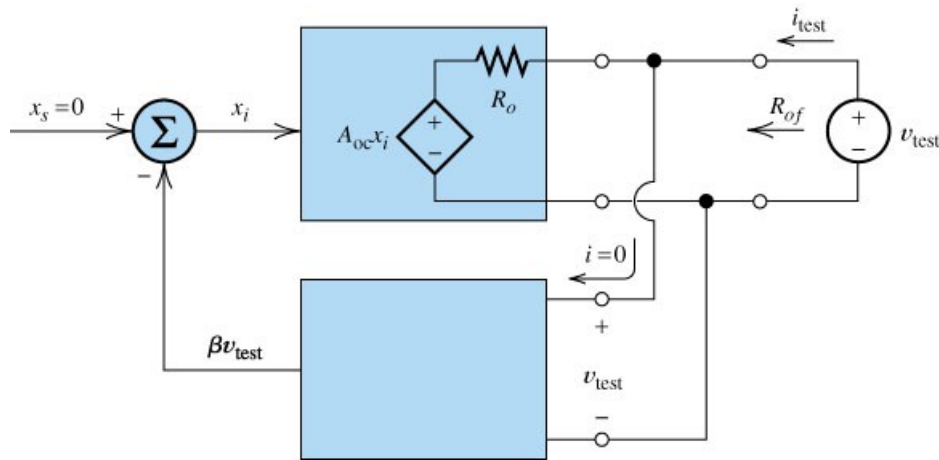


Figure 9.17 Model for the analysis of output impedance with voltage feedback.

$$R_{of} = \frac{v_{test}}{i_{test}} = \frac{R_o}{1 + A\beta} < R_o$$

The voltage feedback decreases the output impedance.

The Effects of Current Feedback on Output Impedance

 


Figure 9.18 Model for the analysis of output impedance with current feedback.

$$R_{of} = \frac{v_{test}}{i_{test}} = R_o (1 + A\beta) > R_o$$

The current feedback increases the output impedance.

9.7 Effect of Feedback on Pole Locations

Dominant - Pole Amplifiers

Poles – roots of the denominator of the gain. Gain is expressed as a function of Laplace transform variable s .

Expression for open-loop gain

$$A(s) = \frac{A_0}{(s/2\pi f_b) + 1} \quad (9.42)$$

If β is constant, the closed-loop gain is

$$A_f(s) = \frac{\frac{A_0}{(s/2\pi f_b) + 1}}{1 + \frac{A_0 \beta}{(s/2\pi f_b) + 1}}$$

The closed-loop gain can be put into the form

$$A(s) = \frac{A_{0f}}{(s/2\pi f_{bf}) + 1} \quad (9.43)$$

The closed-loop dc gain is

$$A_{0f} = \frac{A_0}{1 + A_0 \beta} \quad (9.44)$$

The closed-loop break frequency

$$f_{bf} = f_b (1 + A_0 \beta) \quad (9.45)$$

Conclusion: **negative feedback increases the upper break frequency of the amplifier.**

Example 9.5 Bode Plots for a Dominant - Pole Amplifier with Feedback

A certain integrated - circuit operational amplifier has a single pole in its gain function. The open - loop dc gain is $A_0 = 10^5$ and the open - loop break frequency is $f_b = 10$ Hz. Prepare magnitude Bode plots for $A(f)$ and $A_f(f)$ if $\beta = 0.01, 0.1$, and 1 .

Solution:

Open-loop dc gain in dB is

$$A_{0\text{ dB}} = 20 \log_{10} |A_0| = 20 \log_{10} 10^5 = 100\text{dB}$$

For $\beta = 0.01$

$$A_{0f} = \frac{A}{1 + A\beta} = \frac{10^5}{1 + 0.01 \times 10^5} = 99.9 \approx 40\text{dB}$$

$$f_{bf} = f_b (1 + A\beta) = 10 \times (1 + 0.01 \times 10^5) \approx 10\text{kHz}$$

For $\beta = 0.1$: $A_{0f} = 20\text{dB}$ and $f_{bf} = 100\text{kHz}$.
For $\beta = 1$: $A_{0f} = 0\text{dB}$ and $f_{bf} = 1\text{MHz}$.

 


Figure 9.38 Bode plots for the feedback amplifier of, Example 9.5.

Gain Bandwidth Product

$$A_{0f_{bf}} = \frac{A_0}{1 + A_0 \beta} \times f_b (1 + A_0 \beta) = A_0 f_b \quad (9.46)$$

The product of dc gain and the bandwidth of an amplifier is independent of the feedback. It is an important parameter of the amplifier and is called **gain-bandwidth product** or **unity gain frequency**.

Influence of Negative Feedback on Amplifiers - Summary

1. **Gain** is decreased and divided by $1 + \beta A$.
2. **Gain stability** is improved. Relative gain variation dA/A is divided by $1 + \beta A$.
3. **Nonlinear distortion** is reduced.
4. In general the **noise** is increased. Only in some particular cases, when the noise source is localized in a part of the amplifier, the negative feedback can reduce the noise from this source.
5. **Input and output impedances** are affected from the feedback. Depending on its type (series or parallel, voltage or current) input and output impedances are increased or decreased.
6. **Upper half-power frequency** is increased and multiplied by $1 + \beta A$.

9.11 Oscillator Principles

Linear Oscillators

Oscillators: circuits, which produce periodic ac signals with prescribed properties: waveform; frequency and amplitude.

Linear oscillators: the output is approximately sinusoidal. The transistors are operating basically in active region.

Switching oscillators: the electronic devices operate like switches. Usually rectangular pulses at the output.

Basic principle of the linear oscillator: part of the output signal is returned at the input of the amplifier via positive feedback loop. The returned signal is enough to produce after amplification the same output signal.

The Barkhausen Criterion

 


Figure 9.69 Linear oscillator with external signal X_{in} injected.

$$\mathbf{X}_{out} = A(f) [\mathbf{X}_{in} + \beta(f) \mathbf{X}_{out}] \quad (9.52)$$

$$\mathbf{X}_{out} = \frac{A(f)}{1 - A(f)\beta(f)} \mathbf{X}_{in} \quad (9.53)$$

To have output signal when $\mathbf{X}_{in} = 0$, closed-loop gain must be infinity. This is possible if its denominator is 0, i.e.

$$A(f)\beta(f) = 1 \quad (9.54)$$

Example 9.12 Analysis of an Oscillator Circuit

An oscillator is shown in Figure 9.70. The amplifier is an ideal voltage amplifier (infinite input impedance and zero output impedance) with a voltage gain of A_v . The RC network connected from the amplifier output to the input forms the feedback network. Find the value of gain A_v required for oscillation, and find the frequency of oscillation of the circuit.

 


Figure 9.70 Typical linear oscillator.

Solution:

$$\beta(f) = \frac{V_o}{V_{in}} = \frac{R(1/j\omega C)}{R + \frac{1}{j\omega C} + R + \frac{1}{j\omega C}}$$

$$\beta(f) = \frac{R(1/j\omega C)}{R^2 + 3R/j\omega C - 1/\omega^2 C}$$

$$\beta(f) = \frac{R}{3R + j(\omega R^2 C - 1/\omega C)}$$

$$A_{\beta} = 1$$

$$R(3-A) + j\left(\omega R - \frac{1}{\omega C}\right) = 0$$

$$R(3-A) = 0$$

$$A_{min} = 3$$

$$\omega R^2 C - \frac{1}{\omega C} = 0$$

$$\omega = \frac{1}{RC}$$

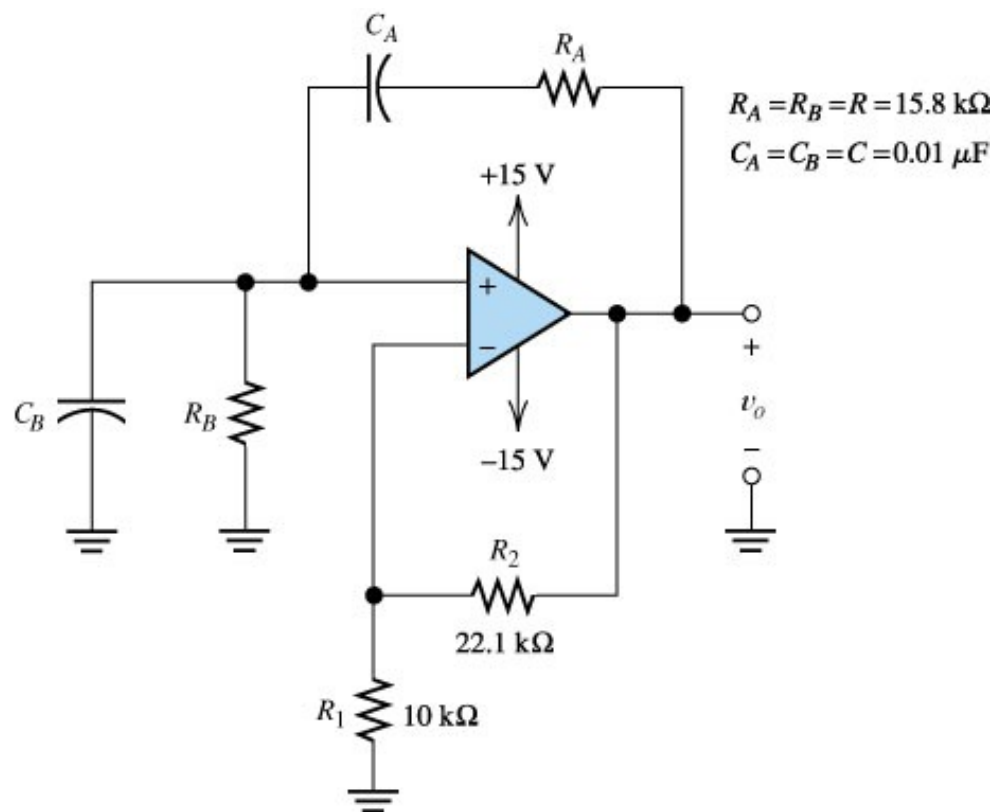


Figure 9.74 An example of a Wien-bridge oscillator designed on the basis of Example 9.12.

 


Figure 9.75 Output voltage of the oscillator in Figure 9.74.

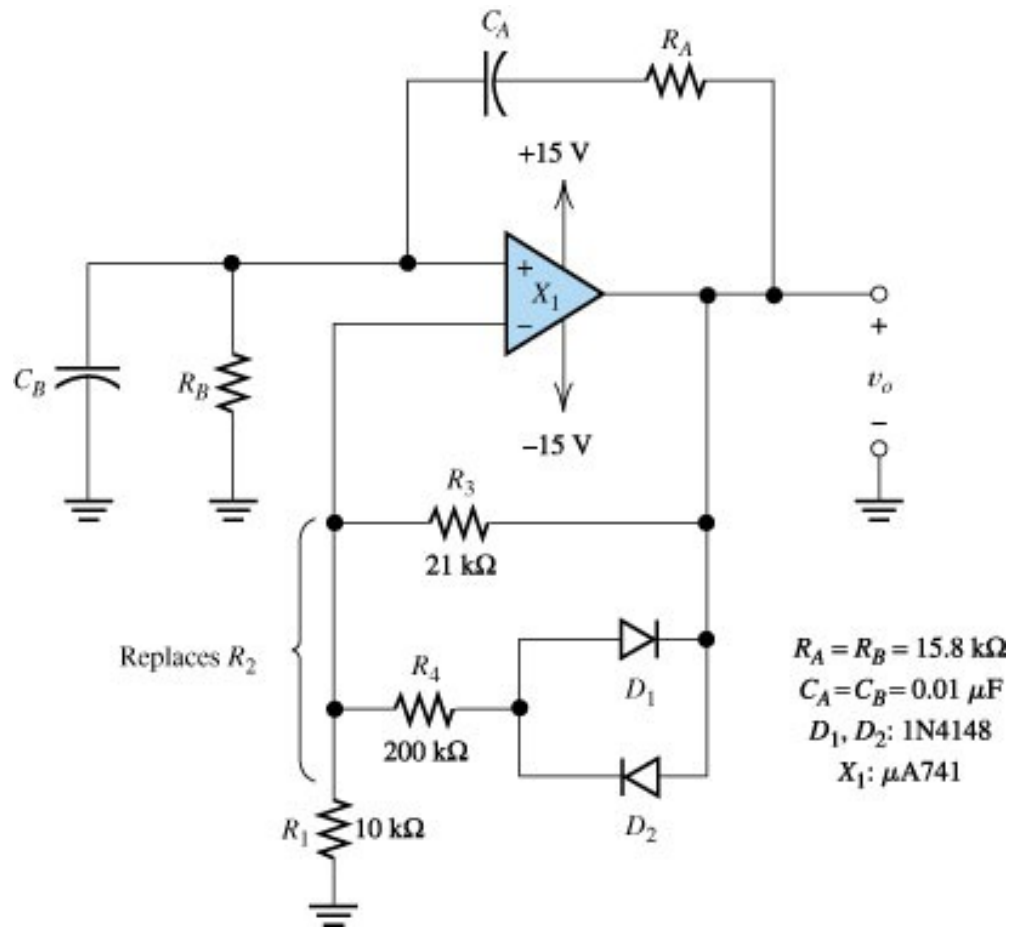


Figure 9.77 Modification of the circuit of the Wien-bridge oscillator. The diodes and the resistor R_4 limit the amplitude of the output signal. In this way is avoided its clipping.

 


Figure 9.78 Output voltage of the oscillator of Figure 9.77.

Chapter IIIa

The operational Amplifier and applications.

III.1. Basic Model for the Operational Amplifier.

The OPERational AMPlifier (OPAMP) is a key building block in analog integrated circuit design. The OPAMP is composed by several transistors and passive elements (resistors and capacitors) and arranged such that its low frequency voltage gain is very high; the dc gain of the OPAMP-741 is around 10^5 V/V (10 μ V at the input give us 1 V at the output). The design of such complex circuit is discussed in chapter 6; here we will use a simplified linear macromodel to analyze the principles of OPAMP based circuits and their operation. Several circuits are studied such as basic amplifiers, first order and second order filters and some non-conventional applications. The versatility of the OPAMP will be evident at the end of this chapter.

To define the fundamental parameters of a system, let us consider a linear two-port system with two terminals grounded, as the one shown in Figure 3.1. There are 4 variables v_i , i_i , v_o and i_o to be studied. The interaction between the four variables can be defined in many different ways, depending on the definition of the dependent and independent variables; in real circuits these definitions depend on the input variable (current or voltage) and the most relevant output variable. Usually in voltage amplifiers the input signal is defined as v_i while the output is v_o .

 


Fig. 3.1. Electronic circuit represented by a black box.

Since we are assuming that the circuit is linear, among other representations, we can describe the electronic circuit by using the following hybrid matrix representation:

$$\begin{bmatrix} i_i \\ v_o \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_i \\ i_o \end{bmatrix} \quad \text{g-parameters} \quad (3.1a)$$

or

$$\begin{aligned} i_i &= g_{11} v_i + g_{12} i_o \\ v_o &= g_{21} v_i + g_{22} i_o \end{aligned} \quad (3.1b)$$

Notice that we are mixing currents and voltages in the matrix, then we call it hybrid representation of the circuit, and the resulting model is termed hybrid model. In many text books you can find at least 4 different set of parameters, but this is one of the most relevant ones for voltage amplifiers. Bipolar and MOS transistors models are based on another model called π -hybrid, to be discussed in the following chapters.

In equations 3.1b, the parameter g_{11} defines the input conductance, and it relates the input current and the input voltage needed by the circuit without considering the effect of the output current ($i_o=0$); the circuit's input conductance is formally defined as follows:

$$g_{11} = \frac{1}{Z_i} = \frac{i_i}{v_i} \bigg|_{i_o=0} \quad (3.2)$$

This parameter is measured by applying an input voltage source and measuring the input current; the output node is left open such that $i_o=0$. Since g_{11} is the ratio of the input current to the input voltage, while the output is left open, its units are amps/volts or $1/\Omega$.

The parameter g_{12} defines the reverse current gain of the topology, and it is defined as

$$g_{12} = \left. \frac{i_i}{i_o} \right|_{v_i=0} \quad (3.3)$$

This parameter represents the reverse current gain: current generated at the input due to the output current. In the ideal case this parameter is zero since usually the operational amplifiers are unidirectional; e.g. the input signal applied to the system generates an output signal, but the output signals (current or voltage) should not generate any signal at the input. For measuring this parameter it is required to short circuit the input port such that $v_i=0$, then apply a current at the output and measure the current generated at the input port. In practical circuits this parameter is very small and usually it is ignored.

The Forward voltage gain is defined as the ratio of the output voltage and input voltage without any load connected at the output.

$$g_{21} = A_V = \left. \frac{v_o}{v_i} \right|_{i_o=0} \quad (3.4)$$

This is certainly one of the most important parameters of the two-port system; ***we also refer to A_V as the open-loop gain of the OPAMP.*** It represents the circuit's voltage gain without any load impedance attached (output current equal zero).

Another important parameter is the system's output impedance, which relates the output voltage and the output current without taking the effects of the input signal. It is defined by

$$g_{22} = Z_0 = \left. \frac{v_o}{i_o} \right|_{v_i=0} \quad (3.5)$$

Thus, the two-port system can be represented by the four aforementioned parameters; the resulting macromodel is shown in Figure 3.2. For sake of clarification we are using impedances instead of admittances in this representation. Notice that a current controlled current source (ICCS) is used for the emulation of parameter g_{12} since it represents the input current (input port) being generated by the output current (output port). A resistor can not represent this parameter since current is flowing in one port but the voltage at the other port controls it. Similar comments apply to the voltage controlled voltage source represented by $A_V v_i$ ($g_{21} v_i$).

 


Fig. 3.2. Linear macromodel of a typical voltage amplifier using hybrid parameters.

Model for the OPAMP. The ideal OPAMP is a device that can be modeled by using the circuit of Fig. 3.2 with $A_V=\infty$, $g_{12}=0$, $Z_i=\infty$, and $Z_o=0$. This is of course an unrealistic model, but it is enough for understanding the basic circuits and their operation. We will see that when you connect several circuits in cascade for complex signal

processing, both input and output impedances are important parameters that affect the overall performance of the system. In this section, however these effects are not considered.

Discuss here the main limitations such as input impedance, limited DC gain and DC offsets and input bias current.

III.2. Basic configurations: Inverting and non-inverting amplifier.

Inverting configuration. The first topology to be studied is the inverting amplifier shown in fig. 3.3a. It consists of an impedance connected between the input source and the OPAMP's inverting terminal; the second impedance is connected from the inverting terminal to the output of the OPAMP. Z_2 provides a negative feedback (connecting the OPAMP's output and the negative input); this is the main reason for the excellent properties of this configuration. The simplified linear macromodel of the OPAMP is used for the representation of the inverting amplifier, and the equivalent circuit shown in fig. 3.3b. By using basic circuit analysis techniques it can be easily find that

$$\frac{v_i - v_x}{Z_1} + \frac{v_o - v_x}{Z_2} = 0 \quad (3.5)$$

and

$$v_o = -A_v v_x \quad (3.6)$$

Solving these equations as function of the input and output voltages yields;

$$\frac{v_o}{v_i} = - \left(\frac{1}{1 + \frac{Z_2/Z_1}{A_v}} \right) \left(\frac{Z_2}{Z_1} \right) \quad (3.7)$$

This relationship is also known as closed-loop amplifier's gain since the feedback resistor in combination with the OPAMP form a closed loop. If the open-loop gain of the OPAMP A_v is very large, then the first factor can be approximated as unity and the closed-loop voltage gain becomes

$$\frac{v_o}{v_i} = - \frac{Z_2}{Z_1} \quad (3.8)$$

This result shows that **if negative feedback is used and if the open-loop gain of the OPAMP is large enough, the overall amplifier's voltage gain depends on the ratio of the two impedances.** Unlike to the gain of the open-loop gain of the OPAMP that can vary by more than 50 % due to transistor's parameters variations and temperature gradients, as will be explained in the following sections, the closed loop gain is quite accurate, especially if same type of impedances are used. Usually ratio of impedances is more precise than the absolute value of components; e.g. ratio of capacitors fabricated in CMOS technologies can be as precise as 99.5 % while the absolute value of the capacitance may change by more than 20%.

 


Fig. 3.3. Inverting amplifier: a) the circuit and b) the linear macromodel assuming that OPAMP input is infinity and output impedance is zero.

Another important observation is that the differential voltage at the OPAMP input v_x (see Fig. 3b) is ideally zero. The reasoning behind this observation is as follows: according to 3.8, the output voltage is bounded (not infinity) if Z_1 is not zero or Z_2 is not infinite, hence v_i is also bounded. Under these conditions and according to expression 3.6 the OPAMP input voltage v_x is very small if A_v is large enough; the larger the OPAMP open loop gain the smaller signal at the input of the OPAMP. Therefore the **inputs of the OPAMP can be considered as a virtual short; the voltage difference between the two input terminals ($v_+ - v_-$) is very small but they are not physically connected**. The virtual short principle is extremely useful in practice; most of the transfer functions can be easily obtained if this property is used. To illustrate its use, let us consider again the circuit of fig. 3.3b. Due to the virtual ground at the input of the OPAMP, $v_x=0$ (virtual short) and the input current i_i is determined by v_i/Z_1 . Since the input impedance of the OPAMP is infinite, i_i flows throughout Z_2 , leading to an output voltage given by $-i_i Z_2$. As a result, the closed-loop voltage gain becomes equal to $-Z_2/Z_1$, as stated in equation 3.8.

If the impedances Z_1 and Z_2 are replaced by resistors as shown in Fig. 3.4a, we end up with the basic resistive inverting amplifier. The closed-loop gain is then obtained as

 


Fig. 3.4. Resistive amplifiers: a) inverting configuration and b) non-inverting configuration.

$$\frac{v_o}{v_i} = -\frac{R_2}{R_1} \quad (3.9)$$

Notice that in the case of the inverting configuration, the amplifier's input impedance is determined by R_1 ; this is a result of the virtual ground present at the inverting terminal of the OPAMP. Hence, if several inverting amplifiers are connected in cascade we have to be aware that the amplifier must be able to drive the input impedance of the next stage.

Non-inverting voltage gain configuration. If the input signal is applied at the non-inverting terminal and R_1 is grounded, as shown in fig. 3.4b, the non-inverting configuration is obtained. Notice that the **feedback is still negative**. If R_2 is connected to the positive terminal, the circuit becomes unstable and useless for linear applications; this will be evident in the following sections. The closed-loop voltage gain of the non-inverting configuration can be easily obtained if the virtual short principle is used. Due to the high gain of the OPAMP, the voltage difference between the inverting and non-inverting terminals is very small; hence the voltage at the non-inverting terminal of the OPAMP is also v_i . The current flowing through R_1 and R_2 is then given by v_i/R_1 ; therefore the output voltage is computed as

$$\frac{v_o}{v_i} = \frac{v_i + i_1 R_2}{v_i} = \frac{v_i + (v_i/R_1)R_2}{v_i} = 1 + \frac{R_2}{R_1} \quad (3.10)$$

The voltage gain is therefore greater or equal than 1. An important characteristic of this configuration is that ideally its input impedance is infinity; hence several stages can be easily connected in cascade. A special case of the non-inverting configuration is the buffer configuration shown in figure 3.5. If $R_1=\infty$, according to equation 3.10, the voltage gain is unity; in this case the value of R_2 is not critical and can even be short-circuited ($R_2=0$). This topology is also known as unity gain amplifier or buffer, and it is very popular for driving small impedances; e.g. speakers, motors, etc.

 


Fig. 3.5 OPAMP in unity gain buffer configuration

Emphasis on loading effects; discuss these issues in class!

III.3. Amplifier with multiple inputs and superposition.

Input signals can be applied to the two inputs of the OPAMP, as shown in Fig. 3.6. R_1 and R_2 are a voltage divider; the input voltage at the non-inverting (v_+) terminal is then

 


Fig. 3.6. Amplifier configuration with two input signals applied to the non-inverting and inverting terminals.

$$\frac{v_+}{v_{i2}} = \frac{R_2}{R_1 + R_2} \quad (3.11)$$

If a virtual short at the OPAMP inputs is assumed, the voltage at the inverting and non-inverting terminals is the same, and determined by v_+ . Using KCL at the inverting terminal of the circuit leads to

$$\frac{v_o - v_+}{R_4} = \frac{v_+ - v_{i1}}{R_3} \quad (3.12)$$

Using equations 3.11 and 3.12, the output voltage is obtained, yielding

$$v_o = -\left(\frac{R_4}{R_3}\right)v_{i1} + \left(\frac{R_2}{R_1 + R_2}\right)\left(1 + \frac{R_4}{R_3}\right)v_{i2} \quad (3.13)$$

Notice that the output voltage is a linear combination of the two input signals: the first component is determined by the v_{i1} and the other one determined by v_{i2} . This analysis can always be used, but we can also take advantage of the properties of linear systems.

Superposition principle for a linear system. *If the OPAMP is considered as a linear device and only linear impedances are used, then the output voltage is a linear combination of all the inputs applied.* If several inputs are applied to the linear circuit, then the output can be obtained considering each input signal at a time; e.g. grounding all other input signals and applying the input signal under study. **Therefore, the following property holds:** if

$$v_o(v_{i1}, v_{i2}, \dots, v_{iN}) = \sum_{j=1}^N \left(k_j v_{ij} \Big|_{v_{ik} \neq j=0} \right) \quad (3.14a)$$

then

$$v_o(v_{i1}, v_{i2}, \dots, v_{iN}) = v_o(v_{i1}, 0, \dots, 0) + v_o(0, v_{i2}, \dots, 0) + \dots + v_o(0, 0, \dots, v_{iN}) \quad (3.14b)$$

This property is known as the **superposition principle**. Let us apply this principle to the topology shown in Fig. 3.6, where two inputs are applied to the amplifier. The circuit is analyzed by applying one input signal at a time: if v_{i1} is considered, v_{i2} is made equal zero. The equivalent circuit is shown in Fig. 3.7a.

 


Fig. 3.7 Equivalent circuits for the computation of the output voltage: a) for v_{i1} and b) for v_{i2} .

Since the input impedance of the OPAMP is infinite, the current flowing through $R_1 \parallel R_2$ is zero, and $v_+ = 0$. The resulting circuit is the typical inverting amplifier where the output voltage is given by $-(R_4/R_3)v_{i1}$; notice that this output corresponds to the first term in equation 3.13. If the first input is grounded and signal v_{i2} is considered, the resulting equivalent circuit is depicted in fig. 3.7b. The voltage at the non-inverting terminal is given by equation 3.11, and the output voltage is equal to $v_o = (1 + R_4/R_3)v_+$; the final result leads to the second term of equation 3.13.

Generalization of basic configurations. The concepts of infinite input impedance, zero output impedance, virtual short of the OPAMP inputs and linear superposition are especially useful when complex circuits are designed. An analog inverting adder is shown in fig. 3.8a; the output voltage can be easily found if we apply the superposition principle to each input. The equivalent circuit for the j th-input is depicted in fig. 3.8b. Since only R_j is connected to v_{ij} , the resistors connected to the other inputs must be grounded. These resistors are connected between the physical ground and the virtual ground generated by the negative feedback and the large open-loop voltage gain of the OPAMP, as a result of this the current flowing through all grounded resistors is zero, then i_j , generated by v_{ij} , R_j and the virtual ground node $v_x (=0)$ flows throughout R_f . The output voltage is then obtained as $-(R_f/R_j)v_{ij}$. By using the same concept to all inputs, the amplifier's output voltage is found as

 


Fig. 3.8. a) Analog adder and b) equivalent circuit for analyzing the output voltage due to v_{ij} .

$$v_o = -\sum_{j=1}^N \left(\frac{R_f}{R_j} \right) v_{ij} \quad (3.15)$$

An interesting advantage of this circuit is that each one of the input resistors independently controls the voltage gain for each input. This is an important circuit property used for the design of analog-digital converters for instance where the addition of binary weighted signals are required.

An analog non-inverting adder is depicted in fig. 3.9a. Similarly to the previous case, the output voltage can be computed by using superposition. Shown in fig. 3.9b is the equivalent circuit for the j th-input signal, and making all other inputs equal zero. The voltage at the non-inverting terminal is the result of the voltage divider determined by the resistors lumped to node v_{+j} as follows:

 


Fig. 3.9. a) Non-inverting amplifier with multiple inputs and b) equivalent circuit for the j th input.

$$\frac{v_{+j}}{v_{ij}} = \frac{R_1 \parallel R_2 \cdots R_{j-1} \parallel R_{j+1} \cdots R_N \parallel R_X}{(R_1 \parallel R_2 \cdots R_{j-1} \parallel R_{j+1} \cdots R_N \parallel R_X) + R_j} \quad (3.16)$$

Since many components are in parallel, for the analysis of this type of networks it is very often more convenient to use admittances instead of impedances. For this example, the previous equation can also be expressed as

$$\frac{v_{+j}}{v_{ij}} = \frac{\frac{1}{R_j}}{\frac{1}{R_j} + \frac{1}{R_1 \parallel R_2 \cdots R_{j-1} \parallel R_{j+1} \cdots R_N \parallel R_X}} \quad (3.16b)$$

The numerator $(1/R_j)$ is identified as the admittance of the element connected between the input signal and v_{+j} . The denominator represents the parallel of all elements attached to v_{+} . The **parallel connection of impedances is also equivalent to the reciprocal of the addition of their admittances**; then 3.16 can be expressed by the following equivalent expression

$$\frac{v_{+j}}{v_{ij}} = \frac{g_j}{\sum_{i=1}^N (g_i) + g_X} \quad (3.17)$$

where $g_i = 1/R_i$. Once v_{+j} is obtained, the output voltage generated by v_{ij} can be obtained. Since v_{+j} is the voltage at the non-inverting terminal, to find the output voltage for this input is straightforward as $v_{oj} = (1 + R_f/R_i) v_{+j}$. Taking into account all the input signals and applying the superposition principle, it can be shown that the overall output voltage is a linear combination of all inputs; the result of this analysis yields,

$$v_o = \left(1 + \frac{R_f}{R_i}\right) \left(\sum_{j=1}^N v_{+j} \right) = \left(1 + \frac{R_f}{R_i}\right) \left(\sum_{j=1}^N \frac{g_j v_{ij}}{\sum_{i=1}^N (g_i) + g_X} \right) = \left(\frac{1 + \frac{R_f}{R_i}}{\sum_{i=1}^N (g_i) + g_X} \right) \left(\sum_{j=1}^N g_j v_{ij} \right) \quad (3.18)$$

Each input signal has a contribution to the output voltage that depends of all resistors, unlike the case of the inverting topology. The input impedance for each input depends on the array of resistors; for instance the input impedance seen by the j th-input signal is


$$Z_j = R_j + (R_1 \parallel R_2 \cdots R_{j-1} \parallel R_{j+1} \cdots \parallel R_N \parallel R_X) \quad (3.19)$$

Similar expressions can be obtained for all other input sources.

 Example: Design a circuit that implements the following equation:

$$v_o(t) = 10v_1 + 20v_2 + 5$$

If needed use the supply voltages ± 15 V. The circuit shown below can be used; this is not the only solution, combinations of inverting and non-inverting circuits might be used as well. The design process consists of finding the resistance values. For that purpose, the following equations must be solved:



$$10 = \left(1 + \frac{R_5}{R_4}\right) \left(\frac{g_1}{g_1 + g_2 + g_3} \right)$$

$$20 = \left(1 + \frac{R_5}{R_4}\right) \left(\frac{g_2}{g_1 + g_2 + g_3} \right)$$

$$5 = \left(1 + \frac{R_5}{R_4}\right) \left(\frac{g_3}{g_1 + g_2 + g_3} \right)$$

Solve this set of equations, and find the numerical values; it is evident that $g_1 = 2g_3$ and that $g_2 = 4g_3$.

III.4. Amplifiers with very large gain/attenuation factors.

Very large gain amplifiers require large spread of the components. In analog integrated circuits design, it is difficult to control properly such large ratios, and very often they are very demanding of silicon area. Some configurations allow us to reduce this spread.

Large gain inverting amplifier using resistors in a T-array. Large voltage gain factors require very large resistors; the array of resistors shown in figure 3.10 can be used to “increase” the effective feedback resistor. The circuit’s transfer function can obviously be obtained by using conventional circuit analysis techniques such as KCL. It is however to useful to analyze the circuit based on the following observations:

1. Since the inverting terminal is at the ground potential due to the virtual short at the OPAMP input, the resistor R_2 is connected between node v_x and (virtual) ground; then it is in parallel with R_3 if you analyze the circuit from the output. Therefore, the voltage v_x can be computed as

$$v_x = \left(\frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_4} \right) v_0 \quad (3.20)$$

Notice that v_x is an attenuated version of the output voltage.

2. Also, as a result of the virtual ground at the OPAMP's input, the current flowing through R_2 is given by v_x/R_2 . If the OPAMP is ideal, the current flowing through R_1 is equal to the one flowing through R_2 , and then the output voltage can be computed from the following expression:

$$\frac{v_i}{R_1} = -\frac{v_x}{R_2} = -\left(\frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_4} \right) \left(\frac{v_0}{R_2} \right) \quad (3.21)$$

Therefore, the voltage gain is

$$\frac{v_0}{v_i} = -\left(\frac{(R_2 \parallel R_3) + R_4}{R_2 \parallel R_3} \right) \left(\frac{R_2}{R_1} \right) \quad (3.22)$$

The voltage gain is therefore equivalent to the gain of a two-stage amplifier; larger gain factors are obtained with reduced resistive spread.

 


Fig. 3.10. Resistive voltage amplifier for high-gain applications.

If further reduction on the resistive spread is needed, two T-networks can be used as shown in Fig. 3.11. Similarly to the previous case, the voltage v_x is equal to $-(R_2/R_1)v_i$; notice that v_x is an attenuated version of v_y and this last voltage is an attenuated version of v_o . These voltages are related by the following expressions:

$$\frac{v_x}{v_y} = \frac{(R_2 \parallel R_3)}{(R_2 \parallel R_3) + R_4} \quad (3.23)$$

$$\frac{v_y}{v_0} = \frac{((R_2 \parallel R_3) + R_4) \parallel R_5}{((R_2 \parallel R_3) + R_4) \parallel R_5 + R_6} \quad (3.24)$$

Then the closed loop voltage gain is obtained as

$$\frac{v_o}{v_i} = - \left(\frac{v_o}{v_y} \right) \left(\frac{v_y}{v_x} \right) \left(\frac{v_x}{v_{in}} \right) = - \left(\frac{((R_2 \parallel R_3) + R_4) \parallel R_5 + R_6}{((R_2 \parallel R_3) + R_4) \parallel R_5} \right) \left(\frac{((R_2 \parallel R_3) + R_4)}{(R_2 \parallel R_3)} \right) \left(\frac{R_2}{R_1} \right) \quad (3.25)$$

This voltage gain can be very large; it is in fact determined by multiplication of 3 terms, which is equivalent to a 3-stage amplifier. Notice that the input impedance of the non-inverting circuit is determined by R_1 .

 


Fig. 3.11. Resistive amplifier using a T-configuration for large gain factors

Very large attenuation factors. The T-network can also be used for the design of large attenuation factors, for instance in applications related to power amplifiers where the input signal might be in the range of 100 V or more but the OPAMP can handle only 12 V or less. The resulting circuit using a T-network at the input is shown in figure 3.12. The voltage v_x is an attenuated version of the incoming signal, and the voltage gain is adjusted to the proper level by the typical inverting configuration (R_3 and R_4). The attenuating factor, considering again a virtual ground at the input, is determined by R_1 and the parallel of R_2 and R_3 ; the voltage gain between v_x and v_o is determined by the ratio of resistors R_4 and R_3 . Therefore, the output voltage is given by:

 


Fig. 3.12. Resistive amplifier using a T-configuration for large attenuation factors

$$\frac{v_o}{v_i} = \left(\frac{v_o}{v_x} \right) \left(\frac{v_x}{v_i} \right) = \left(- \frac{R_4}{R_3} \right) \left(\frac{R_2 \parallel R_3}{R_1 + (R_2 \parallel R_3)} \right) \quad (3.26)$$

The first factor is the result of the voltage divider at the input of the structure, while the second factor is the result of the non-inverting amplification of v_x . You can also use the double T-cell structure; it is left to the student to find out the voltage gain in that case; **DO IT, this can be a midterm question.**

III.5. RC Circuits: Integrators and differentiators.

Basic integrators. If the feedback resistor is replaced by a capacitor, we obtain a lossless integrator; the circuit is shown below. In this circuit, the input voltage v_i is converted into a current by R_1 and the virtual ground present at the input of the OPAMP, similarly to the case of the resistive amplifier. The resulting current is injected into the feedback capacitor C_2 where it is integrated; the resulting output voltage is the integral of the injected current. The

analysis of this circuit can easily be done in the frequency domain where the characteristic impedance of the capacitor is given by $1/(j\omega C_2)$. The transfer function of the inverting configuration is, as in the previous cases, determined by the ratio of the impedance in feedback and the input impedance, leading to the following result:

 


Fig. 3.13. Lossless inverting Integrator

$$H(s) = \frac{v_o}{v_i} = -\frac{1}{sR_2C_1} \quad (3.27)$$

where $s=j\omega$. This circuit has a pole at the origin and a “phantom” zero at $\omega=\infty$ (why?). The magnitude response is extremely large at low frequencies, and decreases at higher frequency with a rolloff of -20 dB/decade. The phase response is $+90$ (-270) degrees and independent of the frequency. Notice that at $\omega=1/R_2C_1$, the magnitude of the voltage gain is unity. Usually this circuit is not used as a standalone device, but is the key building block for high-order filters and analog-digital converters.

The combination of resistors and capacitors lead to the generation of poles and zeros; for example, the circuit implementation of a first order filter is shown in figure 3.14. This circuit is also known as a lossy integrator because while R_1 injects charge into C_2 , the resistor R_3 leaks (introduces losses) the charge stored in the capacitor. The gain of this circuit is also determined by the ratio of the equivalent impedance in feedback and the input impedance. In this circuit, the equivalent feedback impedance is composed by the parallel of the impedance of the capacitor ($1/j\omega C_2$) and R_3 . The low frequency gain, where the impedance of the capacitor can be ignored, is determined by the ratio of the two resistors; it is evident that the voltage gain is given by $-R_3/R_1$. At very high frequencies, the impedance of C_2 dominates the feedback and the circuit behaves as the lossless integrator shown in figure 3.19 (gain defined by $-1/sR_1C_2$). The overall voltage gain is given by:

 


Fig. 3.14. First order lowpass filter

$$H(s) = -\frac{R_3}{R_1} \frac{1}{1 + sR_3C_2} \quad (3.28)$$

The low-frequency gain is, as expected, determined by the ratio of the resistors. The pole is located at $\omega=1/R_3C_2$, and for frequencies beyond this frequency the voltage gain decreases with a rolloff of -20 dB/decade.

The main differences between this circuit and the passive lowpass filter (voltage divider) are twofold: a) in the active realization (with OPAMP) the low frequency gain can be greater than 1 by adjusting the ratio of the resistors while in the passive filter the gain is always less than 1; b) the OPAMP allows us to connect the circuit to the next

stage without affecting the transfer function; this is due to the small output impedance of the OPAMP. A typical transfer function obtained with this circuit is depicted in the following plot;

 


Fig. 3.15. Magnitude response for a first order filter.

The unity gain frequency is another important parameter; it can be obtained by taking the magnitude (or square magnitude) of equation 3.28, and equating it to 1. The resulting equation can be solved for the frequency, leading to the following result (find it yourself)

$$\omega_u = \left(\frac{1}{R_2 C_1} \right) \sqrt{\left(\frac{R_2}{R_1} \right)^2 - 1} \quad (3.29)$$

For $R_2 \gg R_1$, this frequency is approximately given by $\omega_u = 1/R_1 C_1$. Notice that for $R_2 < R_1$ the solution is imaginary, meaning that the unity gain frequency does not exist; in fact you can not find any frequency where the gain is unity for an attenuator (dc gain less than 1). For $R_2 < R_1$, the low frequency gain is less than 1; hence the transfer function does not have any intersection with the 0 dB curve.

The general first order transfer function can be implemented by using the topology shown in fig. 3.16. Since the elements are in parallel, it is very convenient to find the voltage gain as the ratio of the equivalent input admittance and the equivalent feedback admittance as follows:

 


Fig. 3.16. General first order filter

$$H(s) = -\frac{g_1 + sC_0}{g_3 + sC_2} = -\left(\frac{R_3}{R_1} \right) \left(\frac{1 + sR_1C_0}{1 + sR_3C_2} \right) \quad (3.30)$$

With this circuit, you can design the following filters:

- Lowpass filters if C_0 is removed. The pole's frequency is given by $1/R_3C_2$
- Amplifier if C_0 and C_2 are removed. Gain = $-R_3/R_1$
- Amplifier if the resistors are removed. Gain = $-C_0/C_2$ (not very practical, especially for low frequency applications)

(d) High-pass if R_1 is removed. Pole's frequency at $1/R_3C_2$, and high frequency gain = $-C_0/C_2$.

The high-pass transfer function can also be realized if a series of a capacitor and resistor is used, as shown in the figure below. Low frequency components are blocked by the capacitor due to its high impedance at low frequencies. At high frequencies the capacitor behaves as a short circuit, and the gain is given by the ratio of the resistors. Using typical circuit analysis techniques, the overall transfer function can be obtained as

 


Fig. 3.17. First order High-pass filter using a series capacitor.

$$H(s) = -\frac{R_3}{R_2 + \frac{1}{sC_1}} = -\left(\frac{R_3}{R_2}\right) \left(\frac{sR_3C_1}{1 + sR_2C_1}\right) \quad (3.31)$$

A DC zero and a pole located at $\omega = 1/R_2C_1$ can be observed. After the pole's frequency the voltage gain is mainly determined by the ratio of the resistors $-R_3/R_2$.

Non-inverting integrator. A non-inverting amplifier is implemented by using the following circuit. It is usually an expensive implementation, since the topology requires matched elements. The transfer function can be easily obtained by noting that the voltage at the non-inverting terminal is the result of a voltage divider between R and C ($v_+/v_{in} = 1/(1+sRC)$). The voltage at the non-inverting terminal is then amplified by a factor 1 plus the ratio of the feedback impedance $1/sC'$ and the resistor R' . The resulting transfer function yields;

 


Fig. 3.18. Non-inverting lossless integrator

$$H(s) = \left(\frac{1}{sR'C'}\right) \left(\frac{1 + sR'C'}{1 + sRC}\right) \quad (3.32)$$

That corresponds to a non-inverting integrator if $R'C' = RC$; in this case, the voltage gain decreases when the frequency increases with a rolloff of -20 dB/decade and its phase is -90 degrees. The phase at DC is $+90$ degrees.

III.6. Instrumentation amplifiers.

In many practical applications, it is desirable to use amplifiers with very large input impedance and very low output impedance. This is the case when the sensors have large output impedance and or limited current driving capabilities. For those applications, the inverting amplifier based on two resistors can not be used since its input impedance is finite; e.g. defined by the input resistance. The only option is to use non-inverting amplifiers, as the ones shown in figure 3.19. In case the incoming signal is differential carried out by v_{i1} and v_{i2} , therefore two non-

inverting amplifiers are used. In a differential system, the information is determined by the voltage difference between the two inputs rather than by the voltage at each node.

The circuit shown in figure 3.19a is composed by 2 single-ended non-inverting amplifiers. The circuit is a particular case of the circuit shown in Fig. 7b; $R_1=0$, $R_2=\infty$, $R_3=\infty$, $R_4=0$ that leads to a unity-gain amplifier (buffer) with very large input impedance. Since the OPAMP output impedance is very small you can easily connect inverting amplifiers after this structure if required. The benefits of these buffers will be evident in the following chapters.

 


Fig. 3.19. Fully-differential amplifiers based on: buffers and b) non-inverting amplifiers.

The topology shown in figure 3.19b is more useful and can provide voltage amplification greater than 1; the input impedance is very large as well and determined by the input impedance of the OPAMP. The analysis of this circuit is straightforward if we take advantage of the virtual short principle. As shown in figure 3.20, the voltages at the inverting terminals are given by v_{i1} and v_{i2} , respectively. The current flowing through R_1 is then given by $(v_{i1}-v_{i2})/R_1$; this current flows throughout the resistors R_f , generating a voltage drop due to R_f given by $(v_{i1}-v_{i2}) R_f / R_1$. The output voltage v_{o1} is then equal to $v_{i1} + (v_{i1}-v_{i2}) R_f / R_1$ while the output voltage v_{o2} is given by $v_{i2} - (v_{i1}-v_{i2}) R_f / R_1$. The differential voltage gain is then computed as

$$\frac{v_{od}}{v_{id}} = \frac{v_{o1} - v_{o2}}{v_{i1} - v_{i2}} = 1 + \frac{2R_f}{R_1} \quad (3.33)$$

 


Fig. 3.20. Practical fully-differential instrumentation amplifier.

Notice in this expression that the output voltage is also differential $v_{od}=v_{o1}-v_{o2}$. Since the gain of the previous expression is defined as the ratio of the differential output voltage and the differential input v_{id} it is known as differential voltage gain.

Discuss here the properties of differential and common-mode signals.
Common-mode input impedance and differential mode input impedance.

The most popular single-ended instrumentation amplifier is depicted in Fig. 3.21; this topology is very useful for instrumentation applications. There are two inputs, and the important information is in differential format $v_{id}=v_{i1}-v_{i2}$. A major advantage of fully-differential circuits is that they are little sensitive to noise and signal interferences that affect both inputs; e.g. common-mode signals. The single ended output then should be proportional to v_{id} , and signals that are present in both inputs with same amplitude and same phase are cancelled by the differential nature of the amplifier. Applying the superposition principle to the circuit shown in fig. 3.21, it can be shown that the output voltage is given by a linear combination of v_{o1} and v_{o2} as follows:

 


Fig. 3.21. Practical single-ended instrumentation amplifier.

$$v_o = \left(1 + \frac{R_5}{R_3}\right) \left(\frac{R_6}{R_4 + R_6}\right) v_{o2} - \left(\frac{R_5}{R_3}\right) v_{o1} \quad (3.34)$$

Using the previous equations 3.33 and 3.34, the output voltage can be obtained as

$$v_o = \left(\frac{R_6}{R_4 + R_6}\right) \left(1 + \frac{R_5}{R_3}\right) \left[\left(1 + \frac{R_2}{R_1}\right) v_{i2} - \frac{R_2}{R_1} v_{i1}\right] - \left(\frac{R_5}{R_3}\right) \left[\left(1 + \frac{R_2}{R_1}\right) v_{i1} - \frac{R_2}{R_1} v_{i2}\right] \quad (3.35)$$

After some algebra we get the following result:

$$v_o = \left[\left(\frac{R_6(R_3 + R_5)}{R_3(R_4 + R_6)}\right) \left[\left(1 + \frac{R_2}{R_1}\right) + \left(\frac{R_5}{R_3}\right) \left(\frac{R_2}{R_1}\right)\right]\right] v_{i2} - \left[\left(\frac{R_6(R_3 + R_5)}{R_3(R_4 + R_6)}\right) \left(\frac{R_2}{R_1}\right) + \left(\frac{R_5}{R_3}\right) \left(1 + \frac{R_2}{R_1}\right)\right] v_{i1} \quad (3.36)$$

If we introduce the conditions $R_3=R_4$ and $R_5=R_6$, this equation simplifies to the required differential output

$$v_o = \left(\frac{R_5}{R_3}\right) \left(\frac{R_1 + 2R_2}{R_1}\right) (v_{i2} - v_{i1}) \quad (3.37)$$

The important properties of this amplifier are:

1. The **input impedance is extremely large** and determined by the OPAMP. Therefore, it can be easily connected to a number of sensors regardless the type of sensor's output impedance.
2. The **output voltage is sensitive to differential input voltage** $v_{id}=v_{i1}-v_{i2}$.
3. **Common-mode noise present at both terminals is rejected** by the differential nature of the topology. The ability to reject common-mode noise (electromagnetic interference present at both amplifier's inputs for

instance) by an amplifier is measured by the common-mode rejection ratio (CMRR) parameter, to be discussed in next sections.

ELEN-325. Part III.b

7.- Design examples.

Workout some additional examples: e.g. fig. P3.19, Sedra-Smith 1st edition.

8.- Filters and other non-conventional circuits.

Filters are used in electronics for the selection of information that is located in a specific frequency band. A popular structure is the so-called multiple feedback topology shown in figure 3.1b. Two feedback paths can be observed in this circuit, the first one due to Y_4 and the second one due to Y_5 . Both feedback trajectories provide negative feedback, that makes the circuit is stable. The voltage gain of this structure can be found by solving the nodal equations at node v_x and the OPAMP's inverting terminal. Those equations can be written as (find it!):

 


Fig. 3.1b. Multiple feedback second-order filter.

$$\begin{bmatrix} Y_1 + Y_2 + Y_3 + Y_4 & -Y_3 & -Y_4 \\ -Y_3 & Y_3 + Y_5 & -Y_5 \end{bmatrix} \begin{bmatrix} v_x \\ v_- \\ v_o \end{bmatrix} = \begin{bmatrix} Y_1 v_{in} \\ 0 \end{bmatrix} \quad (3.1b)$$

Please write the equations and check the matrix (don't believe in professor's result!). Solving the system of equations we should be able to find the output voltage of the circuit. Notice that we are not writing any equation for the output node of the OPAMP, and we should not! The OPAMP output voltage is generated by a voltage controlled voltage source, where the current demanded by the elements connected to the OPAMP is provided by that element. For ideal OPAMPs, v_o is controlled by the elements connected in feedback and the input voltage, and not by the elements connected at the OPAMP output! For the solution of the equations 3.1b make $v_- = 0$ since we have a virtual ground at the input of the OPAMP.

We might write these equations by inspection noticing that:

1. For the **first row we consider the nodal equation at node v_x** . For the element 11 of the admittance matrix we have to consider all the admittances connected to v_x ; since v_x is the first node we are considering. In fig. 3.1b, the elements connected to v_x are Y_1 , Y_2 , Y_3 , and Y_4 .
2. The 12 element of the matrix is determined as the negative of the admittance between v and v_- , since the second node considered in the admittance matrix is v_- .
3. The element 13 is the negative of the element(s) connected between v_x and v_o , in this case $-Y_4$.
4. For the **second row we considered the nodal equation at node v_-** . Matrix term 21 is the negative of the admittance connected between v_- and v_x .
5. The element 22 is composed by all admittances connected to v_- (the node under consideration).
6. Finally the matrix term 23 is the negative of the admittances connected between v_- and v_o .
7. For the right hand side of 3.1b, we considered the input voltage and the admittance connected between v_{in} and v_x .
8. Since we do not have any element connected between v_- and v_i the second term of the right hand side is zero.

Another approach for finding the transfer function is using the properties of linear circuits. Applying superposition, v_x is a linear combination of v_{in} and v_o . Since the OPAMP inverting terminal is a virtual ground, computation of v_x yields (check it!)

$$v_x = \frac{Y_1}{Y_1 + Y_2 + Y_3 + Y_4} v_{in} + \frac{Y_4}{Y_1 + Y_2 + Y_3 + Y_4} v_o \quad (3.2b)$$

Also, notice that v_o is generated by Y_5 , Y_3 and v_x as

$$v_o = -\frac{Y_3}{Y_5} v_x \quad (3.3b)$$

Solving those equations, the voltage gain can be found as:

$$H(s) = \frac{v_o}{v_{in}} = \frac{-Y_1 Y_3}{Y_5 (Y_1 + Y_2 + Y_3 + Y_4) + Y_3 Y_4} \quad (3.4b)$$

Both methods are useful.

A Particular case of this circuit is the **Second order LOW-PASS transfer function**. Replacing some of the admittances in Fig. 3.1b by the resistors and capacitors shown below, the circuit behaves as a second order lowpass filter. From equation 3.4b it can be found that

 


Fig. 3.2b. Multiple feedback Low-pass filter.

$$H(s) = \frac{-G_1 G_3}{s^2 C_5 C_2 + s C_5 (G_1 + G_3 + G_4) + G_3 G_4} \quad (3.5b)$$

The properties of this circuit are evident just analyzing the location of poles and zeros. There are two poles defined by the different components, and two zeroes at $\omega = \infty$ (why?). Therefore, the magnitude response will remain relatively flat until the frequency of the dominant poles if real poles are implemented. For frequencies above the first (dominant) pole, the magnitude response decreases monotonically with a roll-off of -20 dB/decade. Beyond the frequency of the second pole the roll-off becomes -40 dB/decade due to the effect of the second pole, as shown in the figure below.

 


Fig. 3.3b. Magnitude response for a second order transfer function with two real poles.

For better rejection of high frequency components usually the poles are located close to each other as shown in the dashed curve; in this case the high-frequency rolloff of the magnitude response is -40 dB/decade. For the design of a low-pass second order transfer it is more convenient to express equation 3.5b as

$$H(s) = -\left(\frac{G_1 G_3}{C_5 C_2}\right) \left(\frac{1}{s^2 + s \frac{(G_1 + G_3 + G_4)}{C_2} + \frac{G_3 G_4}{C_5 C_2}} \right) \quad (3.6b)$$

The poles of the system are determined by the denominator of the previous equation and can be obtained as

$$\omega_{P1,2} = -\left(\frac{G_1 + G_3 + G_4}{2C_2}\right) \left(1 \pm \sqrt{1 - \frac{4 \frac{G_3 G_4}{C_5 C_2}}{\left(\frac{G_1 + G_3 + G_4}{C_2}\right)^2}} \right) = -\left(\frac{G_1 + G_3 + G_4}{2C_2}\right) \left(1 \pm \sqrt{1 - \frac{4G_3 G_4 \left(\frac{C_2}{C_5}\right)}{(G_1 + G_3 + G_4)^2}} \right) \quad (3.7b)$$

Selecting the proper values for the components, the poles can be real or complex conjugate; the conditions for these cases are the following:

$$\omega_{P1,2} = \begin{cases} \text{Real if } \frac{4G_3 G_4 \left(\frac{C_2}{C_5}\right)}{(G_1 + G_3 + G_4)^2} \leq 1 \\ \text{Complex conjugated if } \frac{4G_3 G_4 \left(\frac{C_2}{C_5}\right)}{(G_1 + G_3 + G_4)^2} > 1 \end{cases} \quad (3.8b)$$

The phase response is also important for the full characterization of the low-pass filter. The inverting filter configuration has a phase shift of -180 degrees at very low frequencies; this can be verified on the original transfer function, equation 3.6b, evaluating it at $s=0$. Each pole introduces a phase shift of -45 degrees around its pole

frequency, as discussed in previous sections. If the poles are far away from each other, the phase response looks like the one depicted by the solid line in the following phase plot.

 


Fig. 3.4b. Phase response for an inverting second-order transfer function.

If the system have the two poles close to ω_{p1} , then the system's phase response presents a roll-off of -90 degrees/decade around ω_{p1} , due to phase contribution of two poles, as shown in the dashed line plot.

The following design example will be discussed in class:

Lowpass filter design: DC GAIN = 20 dB, $\omega_{p1}=\omega_{p2}=100$ Krad/sec. The design equations are obtained from the desired filter's transfer function as follows:

$$H(s) = -\left(\frac{10\omega_1^2}{(s + \omega_{p1})(s + \omega_{p1})} \right) = -\left(\frac{10\omega_{p1}^2}{s + 2\omega_{p1}s + \omega_{p1}^2} \right)$$

Note that the numerator $10\omega_{p1}^2$ is needed to obtain the desired DC voltage gain. Equation the terms of this equation with the ones of equation 3.6b, the design conditions are obtained

$$R_4/R_1=10$$

$$(10^5)^2=1/(R_3R_4C_2C_5)$$

$$2(10^5)=(1/R_1+1/R_3+1/R_4)/C_2$$


Lets design the filter based on power consumption considerations. To avoid the use of very small resistors, which implies very large currents and more power consumption, lets fix the smaller resistor to $R_1=10$ k Ω and to use $R_3=R_4$. Hence:

$$R_3=R_4=100 \text{ k}\Omega$$



$$C_2C_5=1/(10^{10} \times 10^{10})=10^{-20}$$

$$C_2=(1.2 \times 10^{-4})/(2 \times 10^5)=0.6 \times 10^{-9}$$

 Then $C_5=10^{-20}/0.6 \times 10^{-9}=16.6 \times 10^{-12}$. The final design is shown below. The circuit has been simulated in PSPICE, the magnitude and phase response are also shown.



Component values for the LOWPASS filter

  

Relationship between frequency domain and time domain. In many cases we are more interested into see the response of the circuit in time domain; e.g. impulse and/or pulse response. An approach for the analysis of a circuit

in time domain is to write the nodal or mesh equations in time domain using the integro-differential equations for capacitors and inductors. Another approach is to obtain the transfer function in the frequency domain as in the previous examples and to convert it into a differential equation by using the properties of the laplace transform. Among many other properties of the laplace transform, one of the fundamental ones is the following:

$$\ell\left(\sum_{i=0}^N a_i \left(s^i x\right)\right) = \sum_{i=0}^N a_i \frac{d^i x(t)}{dt^i} \quad (3.9b)$$

This property of the laplace transform is used for the conversion of rationale linear functions in the s-domain to the differential equation in the t-domain. To illustrate its use, let us consider the following s-domain (frequency domain) lowpass transfer function:

$$\frac{v_o(s)}{v_{in}(s)} = \frac{-a_0}{s^2 + b_1 s + b_0} \quad (3.10b)$$

It can also be re-written as

$$(s^2 + b_1 s + b_0)v_o(s) = -a_0 v_{in}(s) \quad (3.11b)$$

if the laplace transform is applied to both sides of this equation, the time-domain equivalent is obtained leading to the following second-order differential equation

$$\frac{d^2}{dt^2}(v_o(t)) + b_1 \frac{d}{dt}(v_o(t)) + b_0 v_o(t) = -a_0 v_{in}(t) \quad (3.12b)$$

The next step is to solve this equation taking into account the type of input signal; e.g. impulse response, pulse response or even sinusoidal input response. It is not the purpose of this chapter to discuss the time domain analysis, and the student should be referred to more specialized books for detailed analysis and more examples.

Bandpass transfer function. Very often the information to be processed is within a given pass band, hence lowpass and high pass filtering might not be the most efficient approach for signal detection. A bandpass filter is more suitable for this purpose; it can be obtained if in addition to the two poles of the lowpass transfer function, one of the zeros is located at low frequency and the other one at very high frequencies. These zeros can be easily implemented if they are located at $\omega = 0$ and $\omega = \infty$, respectively. If the general multiple feedback transfer function, equation 3.4b, is considered the zero at low frequencies is generated if one of the two elements Y1 or Y3 is replaced by a capacitor while the other one is a conductance, respectively. A suitable option for filter realization is shown in the following figure. The analysis of this circuit is similar to the one used for the lowpass filter; the transfer function is

 


Fig. 3.5b. Multiple feedback band-pass filter.

$$H(s) = \frac{-sG_1C_3}{s^2C_3C_4 + sG_5(C_3 + C_4) + (G_1 + G_2)G_5} = -\left(\frac{G_1}{C_4}\right) \left(\frac{s}{s^2 + s \frac{G_5(C_3 + C_4)}{C_3C_4} + \frac{(G_1 + G_2)G_5}{C_3C_4}} \right) \quad (3.13b)$$

The resulting transfer function has two zeros, one at DC and the other one (phantom) at $\omega = \infty$. If the poles are at the same frequency, the magnitude and phase responses can be approximated by piece wise linear functions as depicted in the following plots.

 


Fig. 3.6b. Magnitude and phase response of a second order bandpass transfer function.

Exercise: Design a Bandpass filter with both poles at 50 MHz and peak gain of 0 dB. Do it!

10.- Partial positive feedback.

10.1 Resistive amplifiers with partial positive feedback. Partial positive feedback can also be used for the implementation of demanding applications. For instance, negative resistors have to be used for the design of voltage controlled oscillators to cancel the effects of resistors lumped to inductors and capacitors (resistive losses). In partial positive feedback circuits, both terminals inverting and non-inverting are embedded in feedback loops; an example is the circuit shown in Fig. 3.7b. The voltage at the positive terminal is a sample of the output voltage v_o , and then it can be found that

 


Fig. 3.7b. Resistive amplifier with negative and positive feedback

$$v_x = \frac{R_3}{R_3 + R_4} v_o \quad (3.14b)$$

The output voltage is composed by the contribution of v_i (inverting amplifier with a voltage gain $= -R_2/R_1$) and v_x (non-inverting amplifier given by $(1 + R_2/R_1)v_x$). Hence, the output voltage can be obtained as:

$$v_o = \left(1 + \frac{R_2}{R_1}\right) v_x - \left(\frac{R_2}{R_1}\right) v_i = \left(\frac{R_3}{R_3 + R_4}\right) \left(1 + \frac{R_2}{R_1}\right) v_o - \left(\frac{R_2}{R_1}\right) v_i \quad (3.15b)$$


The solution of this expression for output voltage yields;

$$v_o = - \left(\frac{\frac{R_2}{R_1}}{1 - \left(\frac{R_3}{R_1}\right) \left(\frac{R_1 + R_2}{R_3 + R_4}\right)} \right) v_i \quad (3.16b)$$

The positive feedback is reflected in the negative term of the denominator. The voltage gain can be further increased if $R_3(R_1 + R_2)/(R_1(R_3 + R_4))$ is close to unity. Notice that the gain can potentially be infinite. This situation is undesirable because a small variation in any of the components has a huge impact on the overall voltage gain; these variations could be due to temperature variations or aging of the components. Thus, if positive feedback is used, be sure that negative feedback is dominant and that variations on components do not drastically affects circuit's performances.

Realization of negative impedances.

The circuit shown below uses partial positive feedback as well since the R_4 links the output voltage and the non-inverting terminal. To understand the operation of the circuit, let us find the voltage at the non-inverting terminal. Applying superposition, v_x is composed by the contribution of v_i and v_o . The first component can be obtained by considering v_i , and grounding v_o ; this can be done because the output of the OPAMP is a low-impedance node, and v_o is defined by the voltages applied at the OPAMP inputs. The second component is obtained by considering v_o and grounding v_i , then

 

3.8b. Amplifier with partial positive feedback.

$$v_x = \frac{R_4 \parallel Z}{R_3 + R_4 \parallel Z} v_i + \frac{R_3 \parallel Z}{R_3 \parallel Z + R_4} v_o \quad (3.17b)$$

Once this voltage is obtained, the output voltage can be easily determined, because

$$v_o = \left(1 + \frac{R_2}{R_1}\right) v_x = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 \parallel Z}{R_3 + R_4 \parallel Z} v_i + \frac{R_3 \parallel Z}{R_3 \parallel Z + R_4} v_o \right) \quad (3.18b)$$

After some algebra we can find the overall transfer function as

$$\frac{v_o}{v_i} = \frac{\left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4 \parallel Z}{R_3 + R_4 \parallel Z} \right)}{1 - \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_3 \parallel Z}{R_3 \parallel Z + R_4} \right)} \quad (3.19b)$$

Once again, the positive feedback is reflected in the negative term of the denominator. An important special case is when $R_1=R_2$ and $R_3=R_4$; the previous equations can be simplified as follows:

$$\frac{v_o}{v_i} = \frac{2(R_3 \parallel Z)}{R_3 - (R_3 \parallel Z)} = \frac{2Z}{R_3} \quad (3.20b)$$

Therefore, the circuit behaves as a non-inverting amplifier. The most interesting properties of this circuit are associated with the input impedance. From 3.17b, it is obtained for the case $R_1=R_2$ and $R_3=R_4$ that

$$v_x = \left(\frac{Z}{R_3 + 2Z} \right) (v_i + v_o) = \left(\frac{Z}{R_3 + 2Z} \right) \left(1 + \frac{2Z}{R_3} \right) v_i = \left(\frac{Z}{R_3} \right) v_i \quad (3.21b)$$

Therefore the current flowing throughout Z can now be obtained as

$$i_Z = \frac{v_x}{Z} = \frac{v_i}{R_3} \quad (3.22b)$$

As can be noticed in this result, the current flowing through Z is determined by R_3 ; this current is independent of Z . Therefore, this circuit can be considered as a voltage controlled current source; the current is controlled by the input voltage and the resistors $R_3=R_4$, and this current is forced to flow through Z . On the other hand, the impedance at the input port is determined as follows (please work out the following expression).

$$Z_i = \frac{v_i}{i_i} = \frac{R_3^2}{R_3 - Z} \quad (3.23b)$$

For $Z < R_3$ the input impedance is positive, and negative for $Z > R_3$.

A useful circuit often used in filter's design is the negative impedance converter. The circuit, shown in Fig. 3.9b, is a variation of the schematic depicted in Fig. 3.8b. The input voltage is applied to the non-inverting terminal, and the output voltage v_o is given by $(1+R_2/R_1)v_i$. The input current i_i is computed as $(v_i - v_o)/Z$, leading to the result given in expression 3.24b.

 


Fig. 3.9b. Negative impedance converter.

$$Z_i = \frac{v_i}{i_i} = \frac{v_i}{v_i - v_o} Z = -\left(\frac{R_1}{R_2}\right) Z \quad (3.24b)$$

Therefore, the equivalent impedance is negative. A negative impedance means that, contrary to the case of a positive impedance, the circuit delivers current when positive signals are applied. The reason for this behavior is that the OPAMP altogether with R_1 and R_2 amplify the input and the output voltage is greater or equal than v_i . Hence positive v_i generates $v_o > v_i$; since Z is connected between them it generates a current that flows from v_o to v_i .

Think about the following questions:

What is the meaning of negative impedance?

Difference between positive and negative impedance?

10.2. Sallen & Key Filter. Positive feedback has been used for the design of filters for long time. The filter based on finite gain amplifier uses 5 admittances and an amplifier with finite gain K . Since the amplifier is a non-inverting structure, the feedback produced by Y_2 is positive leading to a filter with partial positive feedback. By following the analysis procedure used for the multiple feedback filters, the transfer function can be obtained by writing the admittance matrix as follows:

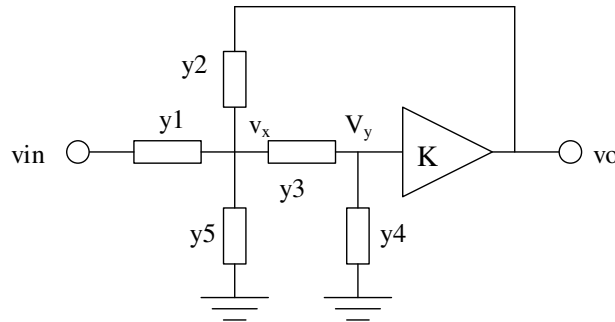


Fig. 3.10b. Sallen and Key second-Order filter.

$$\begin{bmatrix} y_1 + y_2 + y_3 + y_5 & -y_3 & -y_2 \\ -y_3 & y_3 + y_4 & -0 \\ -0 & -K & 1 \end{bmatrix} \begin{bmatrix} v_x \\ v_y \\ v_o \end{bmatrix} = \begin{bmatrix} y_1 v_{in} \\ 0 \\ 0 \end{bmatrix} \quad (3.25b)$$

The first two rows correspond to the nodal equations of nodes v_x and v_y , respectively. The third row corresponds to the finite amplifier gain given by $v_o = K v_y$. The solution of this system leads to the following filter's transfer function:

$$H(s) = \frac{y_1 y_3 K}{(y_1 + y_2 + y_5)(y_3 + y_4) + y_3(y_4 - y_2 K)} \quad (3.26b)$$

Selecting the proper elements lowpass, bandpass and highpass filters can be designed. These especial cases are:

- Selecting Y_1 and Y_3 as conductances, and Y_2 and Y_4 as capacitive admittances, the resulting transfer function leads to a lowpass transfer function. Even more, Y_5 might be removed in this case; the resulting filter is shown in the figure below. Equation 3.27b show the transfer function.

 


Fig. 3.11b. Second order Sallen and Key Filter. Notice that this filter uses partial positive feedback

$$H(s) = \frac{K \left(\frac{1}{R_1 R_2 C_1 C_2} \right)}{s^2 + s \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} (1-K) \right) + \frac{1}{R_1 R_2 C_1 C_2}} \quad (3.27b)$$

Similarly it can be shown that

- Y_1 and Y_4 conductances, and Y_3 and Y_5 capacitors lead to a bandpass transfer function.
- Y_2 and Y_4 conductances, and Y_1 and Y_3 capacitors lead to a high-pass transfer function.

Find yourself the resulting circuits! You may find one of these topologies in the first midterm.

11. Practical Limitations of the Operational Amplifiers. First at all, we must recognize that practical OPAMP are not even close to the ideal model: infinite input impedance, infinite gain, infinite bandwidth, and unlimited output current capability. Those parameters depends on the topology used (array of transistors, resistors and capacitors, technology used and power consumption); there are tons of different OPAMPs offered by different vendors; eg. Texas Instruments, Fairchild, National Semiconductor, etc. Although the origin of those limitations are not discussed in this course, the effects of on the overall transfer function of these parameters are briefly discussed in this section.

A more realistic OPAMP macromodel is depicted in the following schematic.

 


Figure 3.12b. Macromodel for the OPAMP.

Some values for commercially available OPAMPs are: $Z_i = 1\text{M}\Omega$, $r_o = 10\Omega$, and $A_v = 10^5$. These parameters introduce errors in the transfer function. Usually it is cumbersome to obtain the final results, and it is difficult to evaluate

system degradation especially for complex circuits. Here we obtain some results for a single inverting amplifier but most of the conclusions for this circuit are also valid for complex circuits. Let us consider the circuit shown in Figure 3.13b; we are considering the finite input impedance of the OPAMP Z_i and the input impedance of the stage driven by the OPAMP. Using the macromodel of Fig. 3.12b with $r_0=0$, the equivalent circuit can be obtained as depicted in Figure 3.13 (b). The transfer function can be obtained if the nodal equation at node v_- is written; notice that nodal equation at the OPAMP output can not be written because v_o is controlled by the voltage dependent voltage source ($v_o=A_v(v_+-v_-)$). The current demanded by Z_F and Z_L is provided by the ideal voltage source. Solving the fundamental equation ($i_1=i_i+i_0$) the circuit's transfer function yields,

 


Fig. 3.13b. a) Inverting amplifier with OPAMP input impedance Z_i and load impedance Z_L , and b) equivalent circuit with $r_0=0$.

$$H(s) = -\left(\frac{Z_F}{Z_i}\right) \left(\frac{1}{1 + \frac{(Z_F/Z_1) + (Z_F/Z_i)}{A_v}} \right) \quad (3.29b)$$

The effect of the finite DC gain and finite input impedance on the inverting amplifier can be better appreciated if the error function is considered; from equation 3.29b it follows that

$$H(s) = -\left(\frac{Z_F}{Z_i}\right) \left(\frac{1}{1 + \xi} \right) \cong -\left(\frac{Z_F}{Z_i}\right) (1 - \xi) \quad (3.30b)$$

where the error function ξ is defined as

$$\xi(s) = \frac{(Z_F/Z_1) + (Z_F/Z_i)}{A_v} = \left(\frac{1}{A_v} \right) \left(\frac{Z_F}{Z_1 \parallel Z_i} \right) \quad (3.31b)$$

If the OPAMP DC gain is limited, the assumption of virtual ground is not longer valid since any output voltage variation generates a finite variation on the differential input signal given by v_o/A_v . The smaller the OPAMP gain the larger the voltage variations at the OPAMP input are; hence the error should be inversely proportional to A_v . The voltage variations on the non-inverting terminal lead to current errors: firstly the input current is given by $(v_i - v_-)/Z_1$ hence an error proportional to Z_1 ($i_{\text{error1}} = -v_-/Z_1$) is introduced; Secondly, the OPAMP input impedance takes part of the current generated by Z_1 , leading to a second current error given by $i_{\text{error2}} = v_-/Z_i$. These current errors are converted into voltage errors by the feedback resistor R_F , and are evident in equation 3.31b.

Notice that even if the OPAMP input impedance is infinite, a gain error due proportional to the ideal gain Z_F/Z_1 is present. For a given OPAMP open-loop gain A_v , the larger the closed-loop amplifier's gain the larger the error is. The error that can be tolerated depends on the applications; notice that to keep the error below 1 % for instance it is required to satisfy

$$\xi(s) = \left(\frac{1}{A_v} \right) \left(\frac{Z_F}{Z_1 \parallel Z_i} \right) < 0.01 \quad (3.32b)$$

For instance if $Z_i = 1 \text{ M}\Omega$, and voltage gain of -10 , the voltage gain needed depends on the absolute values of the resistors used, as shown in table below

Z_F/Z_i	A_v
100/10	> 1000
10k/1k	> 1001
1M/100k	> 1100
10M/1M	> 2000

Notice that the errors are important when the input impedance Z_1 is comparable with the OPAMP input impedance Z_i . Another important limiting factor is of course the desired amplifier gain Z_F/Z_i . Notice that 3.31b can also be rewritten as

$$\xi(s) = \left(\frac{1}{A_v} \right) \left(\frac{Z_F}{Z_1} \right) \left(\frac{Z_1 + Z_i}{Z_i} \right) \quad (3.33b)$$

Effects of the OPAMP Finite bandwidth. Unfortunately the OPAMP bandwidth is very limited; believe or not, the bandwidth of the 741 is around 6 Hz only while the open-loop DC gain is around $2 \times 10^5 \text{ V/V}$. The product of the open-loop DC gain and bandwidth is defined as OPAMP's Gain-BandWidth product GBW. For the OPAMP 741, $\text{GBW} \sim 1.2 \text{ MHz}$. These parameters are illustrated in the following plot

 


Fig. 3.14b. Typical open-loop magnitude response of an OPAMP

The OPAMP open-loop voltage gain can be modeled by a finite DC gain and a low-frequency pole as

$$A_v(s) = \frac{A_{DC}}{1 + \frac{s}{\omega_p}} \quad (3.34b)$$

Notice that $\text{GBW} = A_{DC} \times \omega_p$; it is also known as the unity gain frequency ω_u . This frequency is important because it defines the upper limit for the operation of the OPAMP: beyond this frequency the OPAMP is not longer an amplifier but an attenuator. That does not mean that you can always use the OPAMP until ω_u ! Usually the useful frequency range is well below this limit. We learn in the previous discussion that an error is introduced if the open-

loop gain of the OPAMP is finite. For the inverting configuration, the error determined by equation 3.33b. If A_v is frequency dependent, then using 3.34b we can obtain a general form for the error function including the effects of the finite OPAMP bandwidth as shown in the following expression:

$$\xi(s) = \left[\left(\frac{1}{A_{DC}} \right) \left(\frac{Z_F}{Z_1} \right) \left(\frac{Z_1 + Z_i}{Z_i} \right) \right] \left(1 + \frac{s}{\omega_P} \right) \quad (3.33b)$$

Therefore, the pole of the OPAMP leads to a zero for the error transfer function as shown below. Therefore, the higher the bandwidth the larger the error is.

 


Fig. 3.15b. OPAMP open-loop magnitude response and error response for an inverting amplifier.

For the example discussed on the previous section we have: $A_{DC}=10^5$ v/v, $Z_F/Z_1=10$, $Z_i=1\text{M}\Omega$ then it follows:

Z_1/Z_i	ω/ω_p	error
0.001	0.01	$\sim 10^{-4}$
0.001	1	$\sim 1.4 \times 10^{-4}$
0.001	10	$\sim 10^{-3}$
0.001	100	$\sim 10^{-2}$
0.001	1000	$\sim 10^{-1}$
0.01	100	$\sim 10^{-2}$
0.1	100	$\sim 10^{-2}$
1	100	$\sim 2 \times 10^{-2}$

Notice that the error increases further for high frequency applications. This is a result of the limited bandwidth of the OPAMP; we have to remember that the open-loop voltage gain reduces proportional to the frequency. The error is less than 1 % if and only if the frequency of the applied signal is below 100 times the OPAMP pole's frequency. For the OPAMP 741; $f_p=6$ Hz; hence the signal's frequency has to be less than 600 Hz for an ideal amplification factor of -10.


The effects of the OPAMP finite input impedance are not very relevant if the used impedances Z_1 and Z_F are lesser than $Z_i/10$.

- Slew-rate limitations: will be discussed in class.
- Common-mode signals: will be discussed in class.



ANALOG CIRCUITS

 **Presented By,
G.R.Mahendra Babu,
Assistant Professor,
Dept of ECE / FoE / KAHE**




The World Leader in High-Performance Signal Processing Solutions



Data Conversion Fundamentals

Analog-Digital Converters

 

The World Leader in High-Performance Signal Processing Solutions




Introduction to A/D Converters




A/D Converter (ADC) Introduction

- ◆ **A/D Fundamentals**
 - Sampling
 - Quantization
- ◆ **Factors Affecting A/D Converter Performance**
 - Static Performance
 - Dynamic Performance
- ◆ **ADC Architectures**
 - SAR ADCs
 - Pipelined ADCs
 - Flash Type ADC
 - Sigma-Delta ADCs
- ◆ **High Speed ADC Application Considerations**


The Measurement & Control Loop

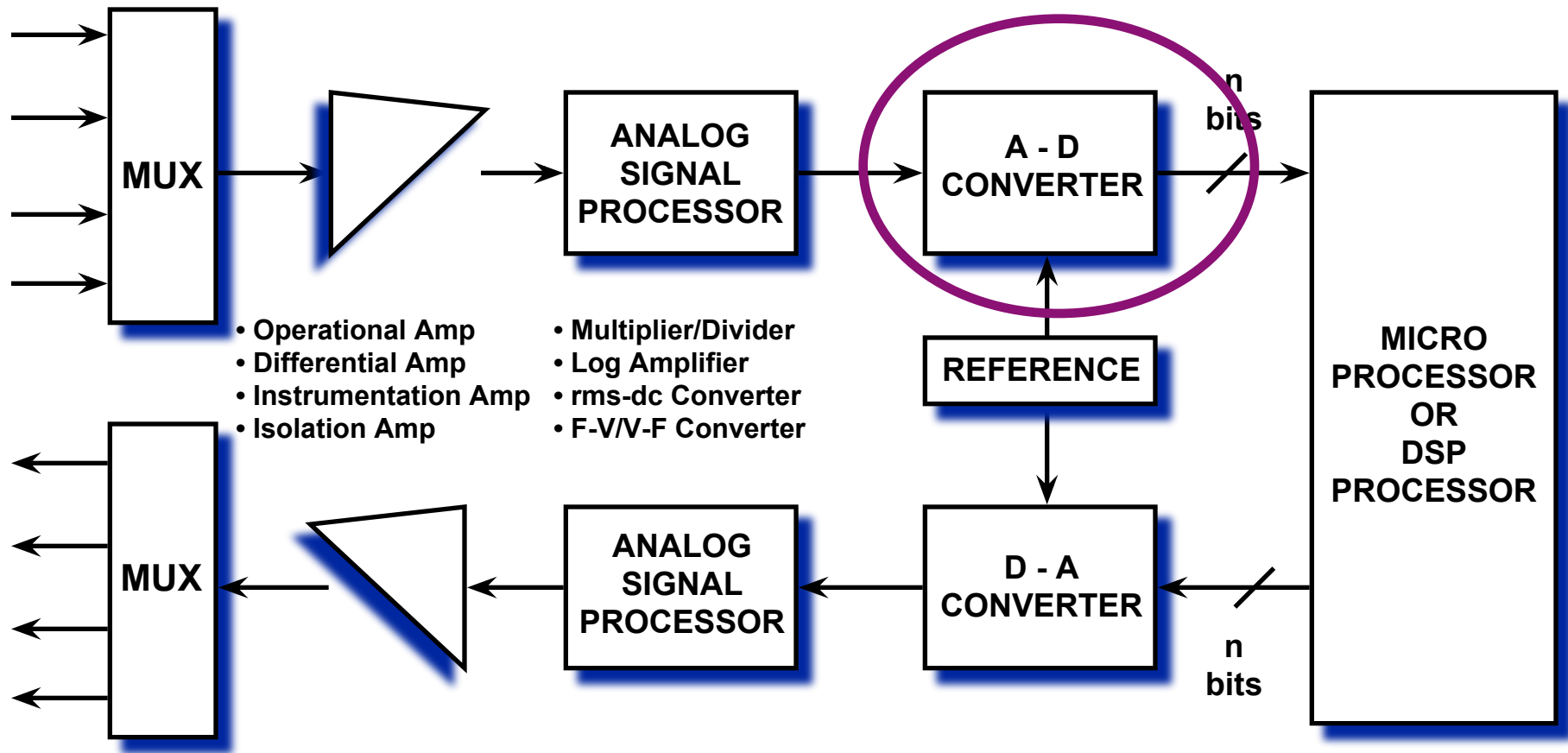

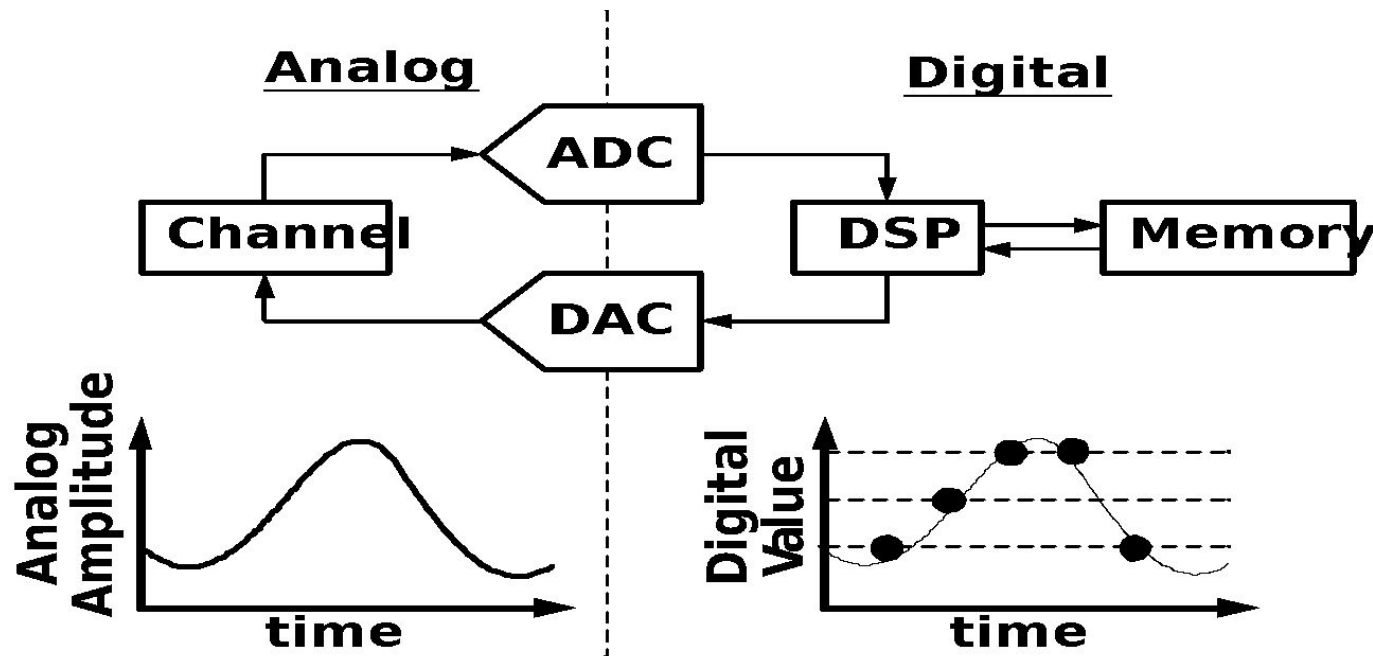
“REAL WORLD” SAMPLED DATA SYSTEMS CONSIST OF ADCs and DACs



**ADC SAMPLED AND
QUANTIZED WAVEFORM**

 

**DAC RECONSTRUCTED
WAVEFORM**

 

What is an Analog-Digital Converter?




$$\text{DIGITAL OUTPUT CODE} = \frac{\text{Analog Input}}{\text{Reference Input}} \times (2^N - 1)$$

- ◆ Produces a Digital Output Corresponding to the Value of the Signal Applied to Its Input Relative to a Reference Voltage
- ◆ Finite Number of Discrete Values : 2^N Resulting in Quantization Uncertainty
- ◆ Changes Continuous Time Signal into Discrete Time Sampled Representation
- ◆ Sampling and Quantization Impose Fundamental yet Predictable Limitations

Sampling Process

 
- ◆ Representing a continuous time domain signal at discrete and uniform time intervals
- ◆ Determines maximum bandwidth of sampled (ADC) or reconstructed (DAC) signal (**Nyquist Criteria**)
- ◆ Frequency Domain- “Aliasing” for an ADC and “Images” for a DAC




Quantization Process

◆ Quantization Process

 
- Representing an analog signal having infinite resolution with a digital word having finite resolution
- Determines Maximum Achievable Dynamic Range
- Results in Quantization Error/Noise



 
Conversion Relationship for an Ideal A/D Converter



Quantization Noise

 


Quantization Noise (con't)

 

- ◆ The RMS value of the quantization noise sawtooth is its peak value, $q/2$, divided by $\sqrt{3}$, or $q/\sqrt{12}$
- ◆ For Sine Wave Full Scale RMS Value is $2^{(N-1)}/\sqrt{2}$
- ◆ For Saw Tooth Quantization Error Signal RMS Value is $q/\sqrt{12}$
- ◆ Thus S/N is 1.225×2^N
- ◆ Expressed in dB as $1.76 + 6.02N$, where N is the resolution of the A/D converter

Quantization Noise (con't)

 

- ◆ If the quantization noise is uncorrelated with the frequency of the AC input signal, the noise will be spread evenly over the Nyquist bandwidth of $F_s/2$.
- ◆ If, however the input signal is locked to a sub-multiple of the sampling frequency, the quantization noise will no longer appear uniform, but as harmonics of the fundamental frequency




ADC Resolution vs. Quantization Parameters

Resolution, Bits (n)	2^n	LSB, mV (2.5V FS)	% Full Scale	ppm Full Scale	dB Full Scale
8	256	9.77	0.391	3906	-48.0
10	1024	2.44	0.098	977	-60.0
12	4096	0.610	0.024	244	-72.0
14	16,384	0.153	0.006	61	-84.0
16	65,536	0.038	0.0015	15	-96.0
18	262,164	0.0095	0.00038	3.8	-108.0


Analog Input Signal Definitions

(1) UNIPOLAR SINGLE ENDED


FS - FULL SCALE

 


(2) UNIPOLAR DIFFERENTIAL

 


(3) BIPOLAR SINGLE ENDED

 


(4) BIPOLAR DIFFERENTIAL

 


(5) PSEUDO DIFFERENTIAL

 


Unipolar and Bipolar Converter Codes

 

UNIPOLAR

 


OFFSET BINARY

 

2's COMPLEMENT


Factors Affecting A/D Converter Performance

- Offset And Gain for Unipolar Ranges

 


Factors Affecting A/D Converter Performance

- Offset And Gain for Bipolar Ranges

 


DC Specifications (Ideal)

 - ◆ Ideal ADC code transitions are exactly 1 **LSB** apart.
- ◆ For an N-bit ADC, there are 2^N codes. (1 **LSB** = $FS / 2^N$)
- ◆ For this 3-bit ADC, 1 **LSB** = $(1V / 2^3 = 1/8th)$
- ◆ Each “step” is centered on an eighth of full scale



DC Specifications (DNL)

 - ◆ **Differential Non-Linearity (DNL)** is the deviation of an actual code width from the ideal **1 LSB code width**
- ◆ **Results in narrow or wider code widths than ideal and can result in missing codes**
- ◆ **Results in additive noise/spurs beyond the effects of quantization**



DC Specifications (DNL)

- ◆ DNL error is measured in lsbs.
- ◆ A given ADC will have a typical DNL pattern.
- ◆ These patterns will also have an element of randomness to them.


 


Figure 13. Typical DNL

DC Specifications (INL)

 - ◆ **Integral Non-Linearity (INL)** is the deviation of an actual code transition point from **its ideal position on a straight line drawn between the end points of the transfer function.**
- ◆ **INL is calculated after offset and gain errors are removed**
- ◆ **Results in additive harmonics and spurs**



DC Specifications (INL)

- Some typical INL patterns

 


Figure 12. Typical INL

 



Figure 5. Typical INL



QUANTIFYING ADC DYNAMIC (AC) PERFORMANCE


- ◆ Harmonic Distortion
- ◆ Worst Harmonic
- ◆ Total Harmonic Distortion (THD)
- ◆ Total Harmonic Distortion Plus Noise (THD + N)
- ◆ Signal-to-Noise-and-Distortion Ratio (SINAD, or $S/N + D$)
- ◆ Effective Number of Bits (ENOB)
- ◆ Signal-to-Noise Ratio (SNR)
- ◆ Analog Bandwidth (Full-Power, Small-Signal)
- ◆ Spurious Free Dynamic Range (SFDR)
- ◆ Two-Tone Intermodulation Distortion
- ◆ Noise Power Ratio (NPR) or Multitone Power Ratio (MPR)

Dynamic Testing of A/D Converters

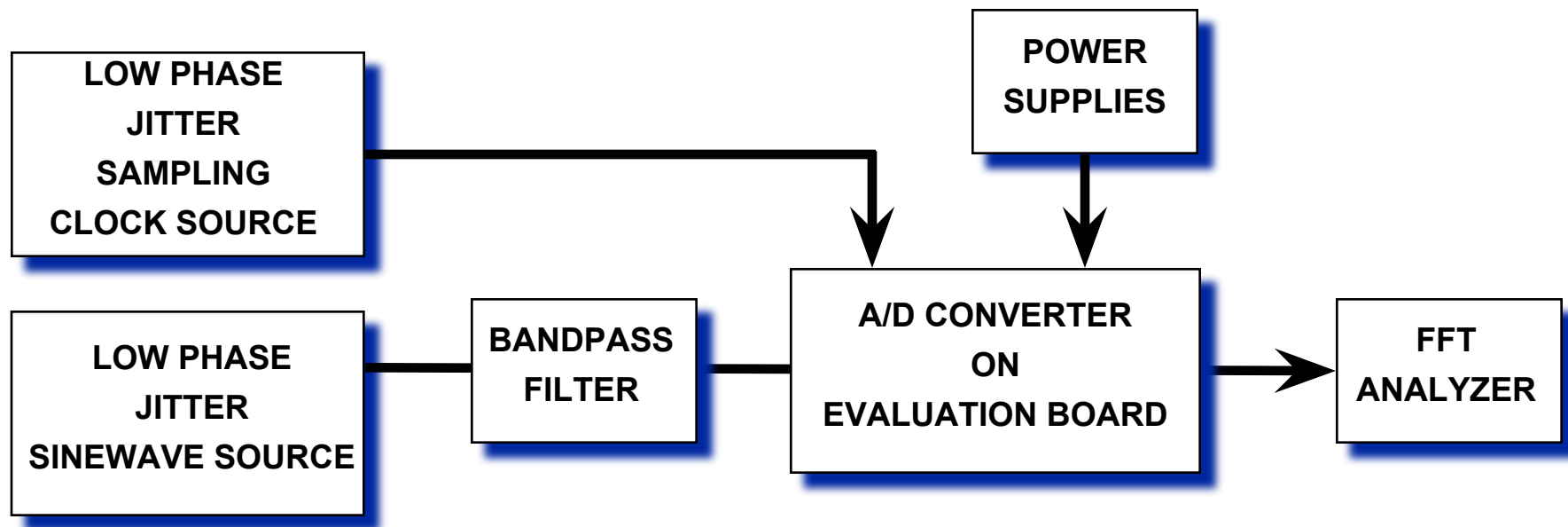


- ◆ ***A Fast Fourier Transform (FFT) Analyzer*** is used to measure dynamic performance


Fast Fourier Transform converts this...

 

...to this

 


An M-Point FFT

 

The Effective Noise Floor of an M-Point FFT Is Less Than The RMS Value of the Quantization Noise

 Actual FFT Plot for AD7484, 14-Bit SAR ADC Sampling at 3MHz






Nyquist Bandwidth & Aliasing

- ◆ 2 Signals that are Mixed Together Produce Sum and Difference Frequency Components
- ◆ Nyquist Theory Stipulates that the Signal Frequency, F_{SIGNAL} must be \leq to $\frac{1}{2} F_{\text{SAMPLING}}$ to Prevent a Condition Known As “Aliasing”, in which the Difference Component Appears Within the Signal Bandwidth of Interest

The Nyquist Bandwidth & Aliasing

 
$$(F_{\text{SIGNAL}} \leq \frac{1}{2} F_{\text{SAMPLING}})$$



The Signal Frequency Is $< 1/2$ the Sampling Frequency and So the Sum and Difference Components Fall Outside (Beyond) the Signal Passband

The Nyquist Bandwidth & Aliasing

 
($F_{\text{SIGNAL}} \geq \frac{1}{2} F_{\text{SAMPLING}}$)




The Signal Frequency Is $> 1/2$ (approx $2/3$) the Sampling Frequency. An “Alias” or False Image is Thus Created that Falls Within the Passband of Interest.

SINAD, ENOB, and SNR

- ◆ **SINAD (Signal-to-Noise-and-Distortion Ratio)**
 - The ratio of the rms signal amplitude to the mean value of the root-sum-squares (RSS) of all other spectral components, including harmonics, but excluding dc
- ◆ **ENOB (Effective Number of Bits)**
 - $$ENOB = \frac{SINAD - 1.76dB}{6.02}$$
- ◆ **SNR (Signal-to-Noise Ratio, or Signal-to-Noise Ratio Without Harmonics)**
 - The ratio of the rms signal amplitude to the mean value of the root-sum-squares (RSS) of all other spectral components, excluding the first five harmonics and dc

 

SFDR, THD, and SNR

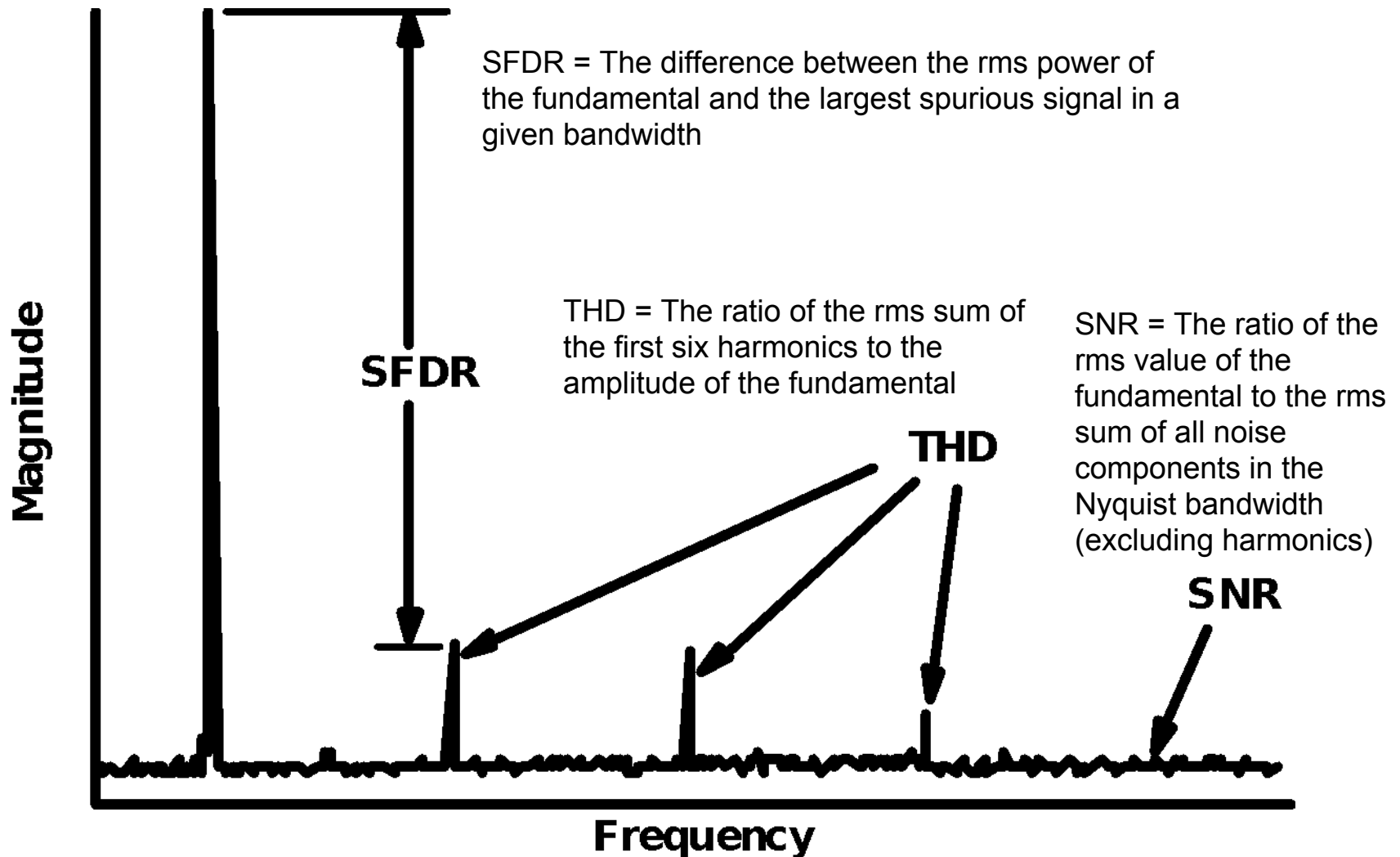




ADC LARGE SIGNAL (OR FULL POWER) BANDWIDTH


- ◆ Full-power bandwidth is defined as the input frequency where the fundamental in an FFT of the output, rolls off to its 3 dB point
- ◆ ADC's SHA generally determines the FPBW
 - FPBW often limited by slew rate of the internal circuitry.
 - May not be compatible with the converter's maximum operating rate
 - ◆ Ideally $f_{\text{FPBW}} \gg f_s / 2$
 - ◆ Many High Speed Converters have $f_{\text{FPBW}} < f_s / 2$
 - Use as a “prerequisite” specification for comparing ADC's IF undersampling capabilities. But need to consider distortion as well.

Successive Approximation ADC

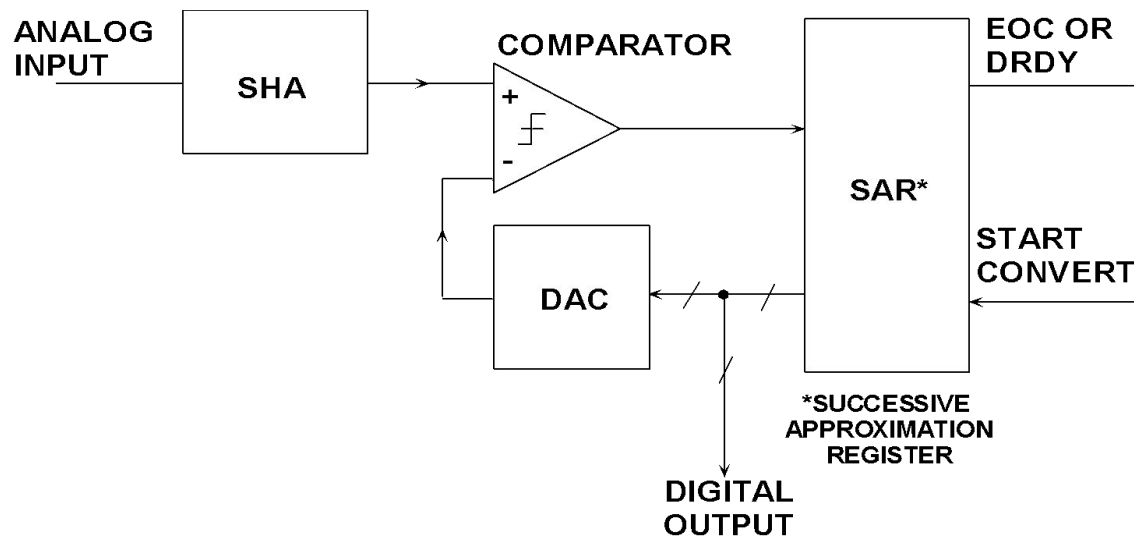“Recursive” One-Bit Sub-Ranging Architecture



Successive Approximation ADC

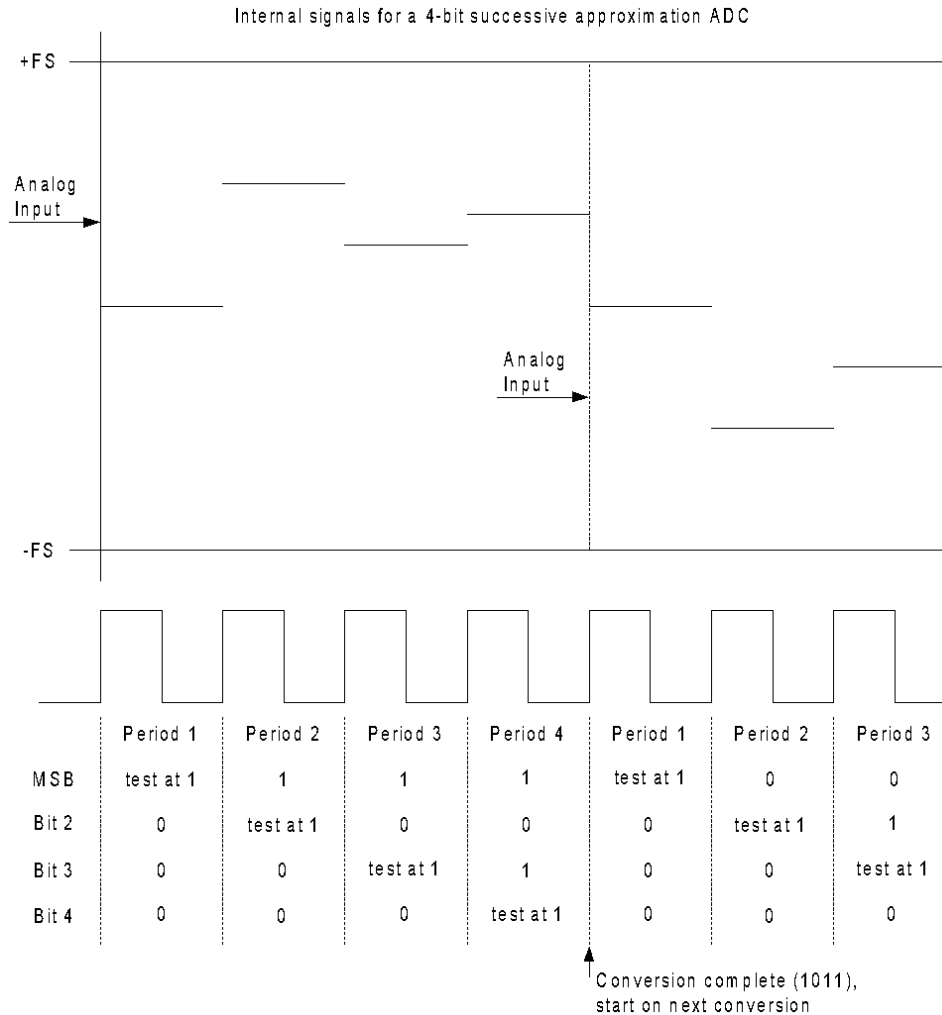




How a Successive Approximation A/D Converter Works

- ◆ **Rising/Falling Edge of Convert Start Pulse Resets Logic**
- ◆ **Falling/Rising Edge Begins Conversion Process**
- ◆ **Bit Comparisons Made on Each Clock Edge**
- ◆ **Conversion Time Equals Number of Comparisons (Resolution) Times Clock Period**
- ◆ **The Accuracy of Conversion Depends on the DAC Linearity and Comparator Noise**

How Successive Approximation Works

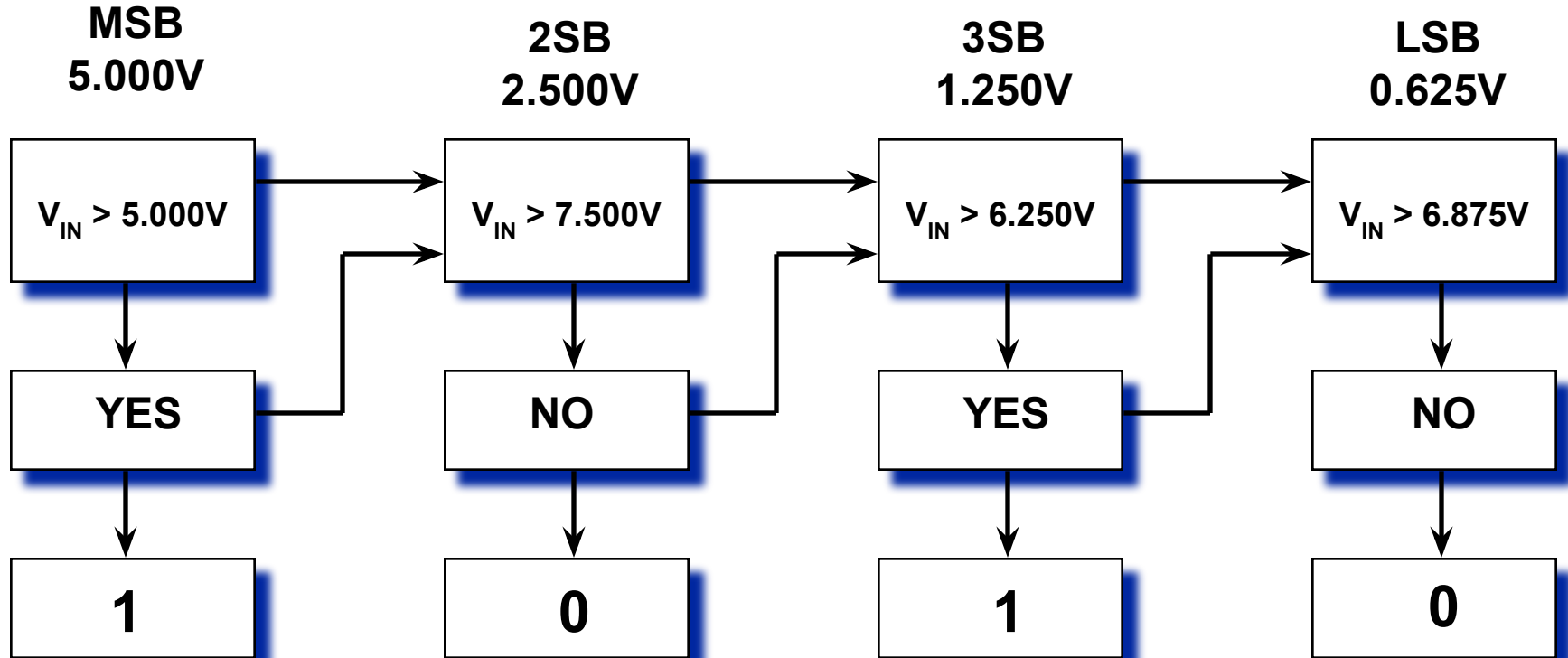EXAMPLE : ANALOG INPUT = 6.428V, REFERENCE = 10.000V





Successive Approximation ADC

Advantages to SAR A/D converters

- Low Power (12-bit/1.5 MSPS ADC: 1.7 mW)
- Higher resolutions (16-bit/1 MSPS)
- Small Die Area and Low Cost
- No pipeline delay

Tradeoffs to SAR A/D converters

- Lower sampling rates


Typical Applications

- Instrumentation
- Industrial control
- Data acquisition

Pipelined Sub-ranging ADC


Conversion divided into discrete stages thus causing pipeline delay

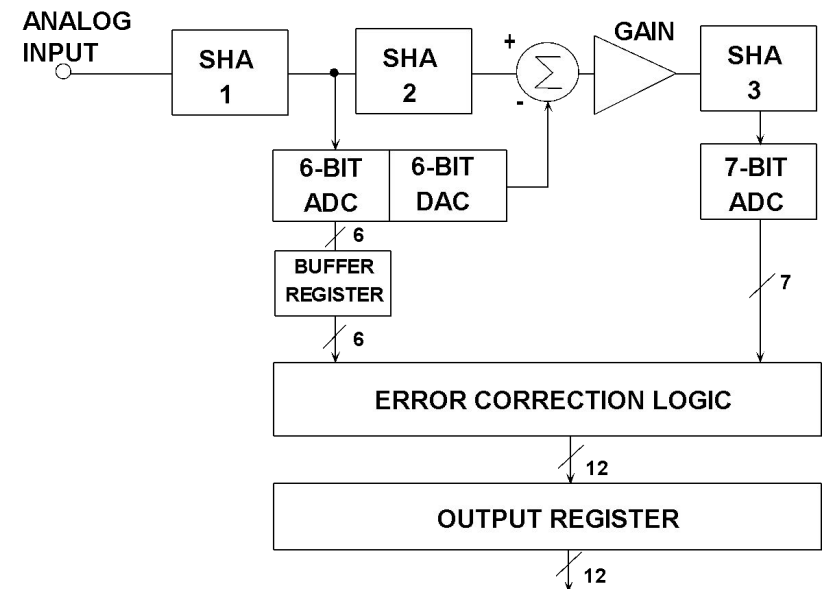- 1st Stage ADC is 6-bit FLASH
- 2nd Stage ADC is 7-bit Flash
- Total resolution is 12 bits (one bit used for error correction)



Pipelined Sub-ranging ADC

Internal signals for a pipelined ADC

 



Pipelined Sub-ranging ADC

Advantages to Pipelined Sub-ranging A/D converters

- Higher resolutions at high-speeds (14-bits/105 MSPS)
- Digitize wideband inputs

• Tradeoffs to pipelined sub-ranging A/D converters

- Higher power dissipation
- Larger die size

Typical Applications

- Communications
- Medical imaging
- Radar


Flash or Parallel ADC

$2N-1$ comparators form the digitizer array, where N is the ADC resolution

Analog input is applied to one side of the comparator array, a 1 lsb reference ladder voltage is applied to the other inputs.

The comparator array is clocked simultaneously and decides in parallel.

 Output logic converts from thermometer code to binary





Flash or Parallel ADC

Advantages to Flash A/D converters

- Fastest conversion times (up to 1 GSPS)
- Low data latency


Tradeoffs to Flash A/D converters

- Higher power consumption
- High capacitive input is difficult to drive







Typical Applications

- Video digitization
- High-speed data acquisition

FIRST-ORDER SIGMA-DELTA ADC

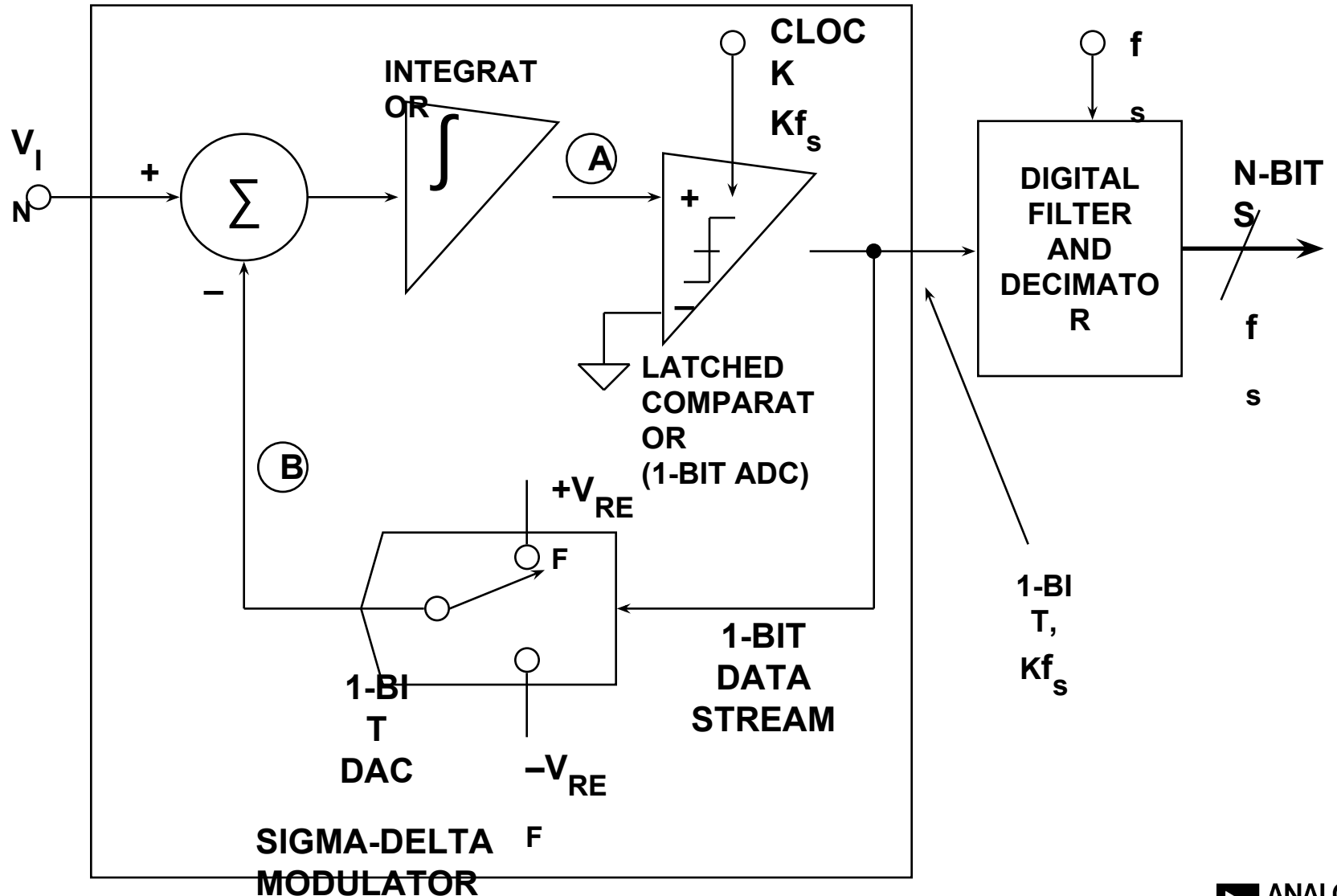

 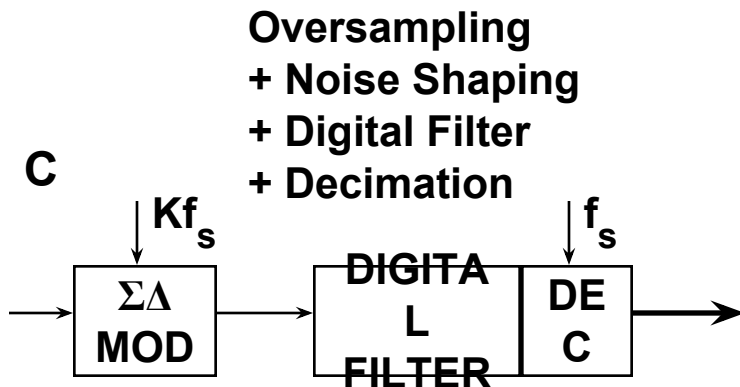    OVERSAMPLING, DIGITAL FILTERING, NOISE SHAPING, AND DECIMATION



DEFINITION OF "NOISE-FREE" CODE RESOLUTION

$$\begin{aligned} \text{EFFECTIVE RESOLUTION ON NOISE-FREE CODE RESOLUTION} &= \log_2 \left[\frac{\text{FULLSCALE RANGE}}{\text{RMS NOISE}} \right] \text{ BITS} \\ \text{NOISE-FREE CODE RESOLUTION} &= \log_2 \left[\frac{\text{FULLSCALE RANGE}}{\text{P-P NOISE}} \right] \text{ BITS} \end{aligned}$$

$$\text{P-P NOISE} = 6.6 \times \text{RMS NOISE}$$

$$\text{NOISE-FREE CODE RESOLUTION} = \log_2 \left[\frac{\text{FULLSCALE RANGE}}{6.6 \times \text{RMS NOISE}} \right] \text{ BITS}$$

16.5bits \swarrow \nwarrow 20mV \searrow 0.4uVrms

$$= \text{EFFECTIVE RESOLUTION} - 2.72 \text{ BITS}$$



SIGMA-DELTA ADCs

Advantages to Sigma-Delta A/D converters

- High resolutions and accuracy (24-bits)
- Excellent DNL and INL performance
- Noise shaping capability

Tradeoffs in Sigma-Delta A/D converters

- Limited input bandwidth
- Slower sampling rates

Typical Applications

- Precision data acquisition and measurement
- Medical instrumentation




High Speed ADC Time Domain Specifications Considerations

- ◆ **Aperture Jitter and Delay**
- ◆ **ADC Pipeline Delay**
- ◆ **Duty Cycle Sensitivity**
- ◆ **DNL Effects**

EFFECTS OF APERTURE AND SAMPLING CLOCK JITTER

◆ Jitter:

 
- Most systems assume the signal is sampled uniformly
- Clock noise leads to non-uniform sampling (*i.e.* jitter)



- Jitter leads to SNR degradation for high frequency inputs:


$$2\pi f_a T_j V_p < V_{LSB}$$

 SNR DUE TO APERTURE AND SAMPLING CLOCK JITTER




EFFECTIVE APERTURE DELAY TIME

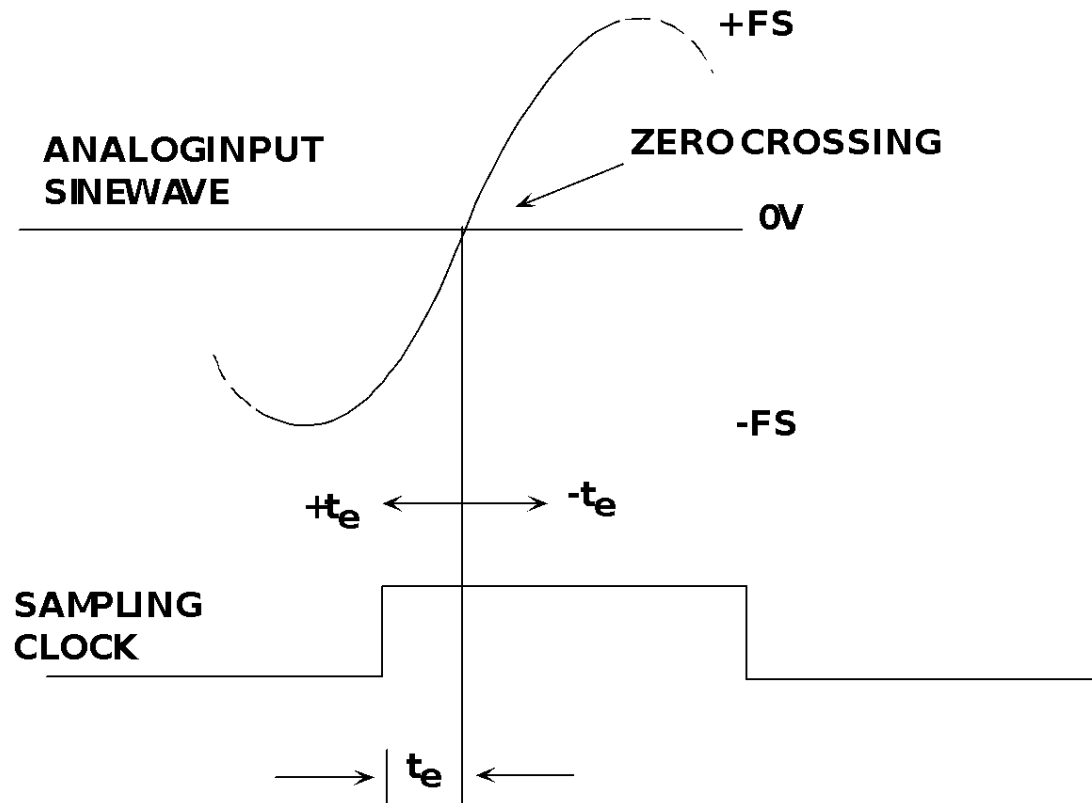- ◆ Typically not an issue in frequency domain applications
- ◆ May vary slightly among devices of same product due to variations in SHA bandwidth and CLK prop. delays




ADC LATENCY OR PIPELINE DELAY

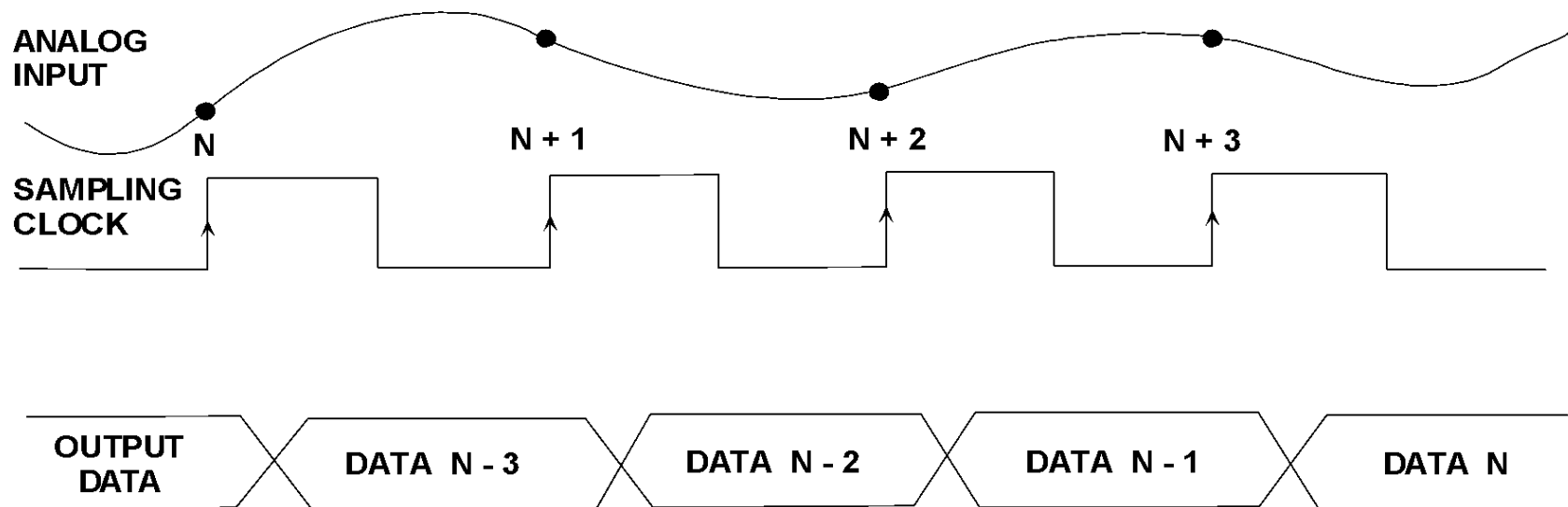- ◆ Many High Speed ADC's, such as subranging types, use pipeline architectures to:
 - Reduce chip size, and power consumption
 - Allows multiple samples to be converted simultaneously in ADC
 - Results in fixed delay between Sampled Input and corresponding digital output.



ADC DUTY CYCLE SENSITIVITY

 - ◆ High Speed ADCs are often sensitive to duty cycle of the CLK input
 - CLK oscillators are usually specified as 40/60 or 45/55
 - Digital Specifications of datasheet provide a minimum CLK HIGH/LOW period (nsec) to achieve rated performance.
 - Some datasheets show SNR/THD graphs as a function of duty cycle
 - Note, ADC also has minimum specified sample rate







DNL ERRORS LIMIT IDEAL NOISE AND SPUR FLOOR PERFORMANCE

- ◆ Ideal ADC code transitions are exactly 1 LSB apart. DNL is the deviation from this value.
- ◆ Results in additive noise/spurs beyond the effects of quantization
- ◆ Limits ultimate achievable SNR and low level signal SFDR performance
 - Predictable for a given device once error transfer function is known.
 - DNL error pattern varies among devices of a given product
- ◆ Dynamic correction techniques include adding “dither” or element shuffling

Example : AD9433 SFDR

SFDR ———→ ENABLED
 ↓
 DISABLED

  


Example : AD9433 SFDR


SFDR

DISABLED

ENABLED

 

Encode = 105Msps
Ain = 70MHz, -0.5dBFS

 

Example of Data Sheet Specifications for AD9430 ADC

AD9430—SPECIFICATIONS

DC SPECIFICATIONS (AVDD = 3.3 V, DRVDD = 3.3 V; T_{MIN} = -40°C, T_{MAX} = +85°C, f_{IN} = -0.5 dBFS, Internal Reference, LVDS Output Mode, unless otherwise noted.)

Parameter	Temp	Test Level	Min	AD9430BSV-170 Typ	Max	Unit
RESOLUTION				12		Bits
ACCURACY						
No Missing Codes	Full	VI		Guaranteed		
Offset Error	25°C	I	-3		+3	mV
Gain Error	25°C	I	-5		+5	% FS
Differential Nonlinearity (DNL)	25°C	I	-1	±0.3	+1	LSB
	Full	VI	-1	±0.3	+1.5	LSB
Integral Nonlinearity (INL)	25°C	I	-1.5	±0.5	+1.5	LSB
	Full	VI	-1.5	±0.5	+2.25	LSB
TEMPERATURE DRIFT						
Offset Error	Full	V		58		μV/°C
Gain Error	Full	V		0.02		%/°C
Reference Out (VREF)	Full	V		+0.12/-0.24		mV/°C
REFERENCE						
Reference Out (VREF)	25°C	I	1.15	1.235	1.3	V
Output Current ¹	25°C	IV			3.0	mA
I _{VREF} Input Current ²	25°C	I			20	μA
I _{SENSE} Input Current ²	25°C	I		1.6	5.0	mA
ANALOG INPUTS (VIN+, VIN-) ³						
Differential Input Voltage Range (S5 = GND)	Full	V		1.536		V
Differential Input Voltage Range (S5 = AVDD)	Full	V		0.766		V
Input Common-Mode Voltage	Full	VI	2.65	2.8	2.9	V
Input Resistance	Full	VI	2.2	3	3.3	kΩ
Input Capacitance	25°C	V		5		pF

Example of Data Sheet Specifications for AD7476 ADC

AD7476/AD7477/AD7478

AD7476—SPECIFICATIONS¹

(A Version: $V_{DD} = 2.7\text{ V to } 5.25\text{ V}$, $f_{SCLK} = 20\text{ MHz}$, $f_{SAMPLE} = 1\text{ MSPS}$ unless otherwise noted;
S and B Versions: $V_{DD} = 2.35\text{ V to } 5.25\text{ V}$, $f_{SCLK} = 12\text{ MHz}$, $f_{SAMPLE} = 600\text{ kSPS}$ unless otherwise noted; $T_A = T_{MIN}$ to T_{MAX} , unless otherwise noted.)

Parameter	A Version ^{1,2}	B Version ^{1,2}	S Version ^{1,2}	Unit	Test Conditions/Comments
DYNAMIC PERFORMANCE					
Signal-to-Noise + Distortion (SINAD) ³	69	70	69	dB min	$f_{IN} = 100\text{ kHz}$ Sine Wave
	70		70	dB min	$T_A = 25^\circ\text{C}$
Signal-to-Noise Ratio (SNR) ³	70	71	70	dB min	
Total Harmonic Distortion (THD) ³	-80	-78	-78	dB typ	
Peak Harmonic or Spurious Noise (SFDR) ³	-82	-80	-80	dB typ	
Intermodulation Distortion (IMD) ³					
Second Order Terms	-78	-78	-78	dB typ	$f_a = 103.5\text{ kHz}$, $f_b = 113.5\text{ kHz}$
Third Order Terms	-78	-78	-78	dB typ	$f_a = 103.5\text{ kHz}$, $f_b = 113.5\text{ kHz}$
Aperture Delay	10	10	10	ns typ	
Aperture Jitter	30	30	30	ps typ	
Full Power Bandwidth	6.5	6.5	6.5	MHz typ	@ 3 dB
DC ACCURACY					
Resolution	12	12	12	Bits	S, B Versions, $V_{DD} = (2.35\text{ V to } 3.6\text{ V})^4$; A Version, $V_{DD} = (2.7\text{ V to } 3.6\text{ V})$
Integral Nonlinearity ³	± 1	± 1.5	± 1.5	LSB max	Guaranteed No Missed Codes to 12 Bits
		± 0.6	± 0.6	LSB typ	
Differential Nonlinearity ³	± 0.75	$-0.9/+1.5$	$-0.9/+1.5$	LSB max	
		± 0.75	± 0.75	LSB typ	
Offset Error ³	± 0.5	± 1.5	± 2	LSB max	
				LSB typ	
Gain Error ³	± 0.5	± 1.5	± 2	LSB max	
				LSB typ	
ANALOG INPUT					
Input Voltage Ranges	0 to V_{DD}	0 to V_{DD}	0 to V_{DD}	V	
DC Leakage Current	± 1	± 1	± 1	$\mu\text{A max}$	
Input Capacitance	30	30	30	pF typ	

A decorative header bar at the top of the slide, divided into several colored segments. From left to right, the segments are green, orange, purple, yellow, pink, and blue. Each segment contains a stylized electronic symbol or text: a green triangle with 'Amplifier', an orange rectangle with a battery symbol and '+ -', a purple square with 'DSP', a yellow rectangle with 'RF' and a signal waveform, a pink rectangle with 'MEMS' and a gear, and a blue rectangle with 'Analog'.

**For complete information
on the World's most extensive line of
A/D converters visit**

WWW.ANALOG.COM

Questions

Flow of electrons is generally termed as ____.

A ____ is a material which offers very little resistance to the flow of current through it.

A silicon diode measures a low value of resistance with the meter leads in both positions. The trouble, if any, is the materials which behave like perfect insulators at low temperatures & at higher temperatures, they behave like

Under normal conditions a diode conducts current when it is

The movement of free electrons in a conductor is called

An n-type semiconductor material

The boundary between p-type material and n-type material is called

You have an unknown type of diode in a circuit. You measure the voltage across it and find it to be 0.3 V. The diode

What type of impurities are to be added to form a P type semiconductors ?

Doping of a semiconductor material means

What occurs when a conduction-band electron loses energy and falls back into a hole in the valence band?

The term bias in electronics usually means

How many valence electrons does a silicon atom have?

Which capacitance dominates in the forward-bias region?

What is the Cut in voltage of Silicon diode?

Germanium Knee Voltage is

Intrinsic Semiconductor means

Under normal conditions a diode conducts current when it is

Reverse breakdown is a condition in which a diode

There is a small amount of current across the barrier of a reverse-biased diode. This current is called

Since diodes are destroyed by excessive current, circuits must have:

Why is heat produced in a diode?

The diode schematic arrow points to the:

The voltage where current may start to flow in a reverse-biased pn junction is called the

The area at the junction of p-type and n-type materials that has lost its majority carriers is called the

DC power should be connected to forward bias a diode as follows:

A diode for which you can change the reverse bias, and thus vary the capacitance is called a

Avalanche breakdown results basically due to

The varactor diode is usually

The diode in which impurities are heavily doped is

The depletion region in a Junction Diode contains

Varactor diodes are used in FM receivers to obtain:

As the forward current through a silicon diode increases, the internal resistance

Reverse breakdown is a condition in which a diode

There is a small amount of current across the barrier of a reverse-biased diode. This current is called

What is the state of an ideal diode in the region of nonconduction?

Schottky diodes are also known as

zener breakdown refers to

What kind of diode is formed by joining a doped semiconductor region with a metal?

An intrinsic semiconductor at the absolute zero temperature

A pn junction allows current flow when

The forward characteristics curve of a diode grows in _____ form.

The reverse-saturation current level is typically measured in

Varying the _____ can control the location of the Zener region.

The _____ the current through a diode, the _____ the dc resistance level.

The reverse-bias current _____ with the increase of temperature.

What is the resistor value of an ideal diode in the region of conduction?

Diodes are connected _____ to increase the current-carrying capacity

A Zener diode:

Avalanche breakdown in semiconductor diode occurs when

The varactor diode is usually

Zener diodes are:

The capacitance of a varactor diode increases when the reverse voltage across it

The diode with a forward voltage drop of approximately 0.25 V is the

Since diodes are destroyed by excessive current, circuits must have:

Drift current is influenced by

What type of diode is commonly used in electronic tuners in TVs?

Which diode employs graded doping?

A PNPN diode is a

opt1

Electric current

good conductor

the diode is open.

good conductor

reverse-biased.

voltage.

is intrinsic.

a diode.

a silicon diode.

Trivalent

that a glue-type substance is added to hold the material together.

doping

the value of ac voltage in the signal.

1

Diffusion

0.5V

0.3V

Pure Semiconductor

reverse-biased

is subjected to a large reverse voltage

forward-bias current

higher voltage sources

due to current passing through the diode

trivalent-doped material

breakdown voltage

barrier potential

– anode, + cathode

varactor diode

impact ionisation

Forward biased

Varactor diode

only charge carriers

Automatic frequency control

increases.

is subjected to a large reverse voltage.

"

forward-bias current.

An open circuit

PIN diodes.

Reverse bias region

laser

behaves like a metallic conductor

the p-type material is more positive than the n-type material

linear

pA

forward current

higher, lower
decreases

0

in series
Has a high forward voltage rating
Reverse bias exceeds a certain value
Forward biased
Specially doped p–n junctions
Decreases
Step-recovery diode
current limiting resistors
magnitude of voltage
varactor
zener
negative resistance device

opt2

electric shock

insulator

the diode is shorted to ground.

insulator

forward-biased.

current.

has trivalent impurity atoms added.

a reverse-biased diode.

a germanium diode.

Pentavalent

that impurities are added to increase the resistance of the material.

recombination

the condition of current through a pn junction.

2

Transition

0.6V

0.4V

Impure Semiconductor

forward-biased

is reverse-biased and there is a small leakage current

reverse breakdown current

current limiting resistors

due to voltage across the diode

positive axial lead

barrier potential

depletion region

– cathode, – anode

tunnel diode

strong electric field across the junction

reverse biased

PIN diode

no charge at all

Automatic gain control

decreases.

is reverse-biased and there is a small leakage current.

reverse breakdown

current.

A short circuit

hot carrier diodes.

Forward bias region

tunnel

behaves like an insulator

the n-type material is more positive than the p-type material

exponential

μA

doping levels

lower, lower

increases

5 k

in parallel-series

Is useful as an amplifier

Forward bias exceeds a certain value

Reverse biased

Normally doped p–n junctions

Increases

Schottky diode

more dopants

concentration of carriers

Schottky

LED

voltage controllable device

opt3

semiconductor
semiconductor
the diode is internally shorted.
semiconductor
avalanched.
recombination.
has pentavalent impurity atoms added.
a pn junction.
a forward-biased silicon diode.
Octavalent
that impurities are added to decrease the resistance of the material.
generation
the value of dc voltages for the device to operate properly.

3

Depletion
0.7V
0.5V
Non doped Conductor
avalanched
has no current flowing at all
conventional current
more dopants
due to the power rating of the diode
anode lead
forward voltage
n region
+ anode, – cathode
zener diode
emission of electrons
Unbiased
Tunnel diode
vacuum, and no atoms at all
Automatic volume control
remains the same.
has no current flowing at all.
conventional
current.
Unpredictable
step-recovery diodes.
no bias
pin
has a large number of holes
both the n-type and p-type materials have the same potential
logarithmic
mA
forward voltage

lower, higher
remains the same
Undefined
in parallel-series
Has a sharp breakdown at low reverse voltage
Forward current exceeds a certain value
un biased
Lightly doped p–n junctions
Breaks down
Back diode
higher voltage sources
concentration gradient of carriers
LED
tunnel
current controllable negative resistance device

opt4

none of the above

none of the above

the diode is working correctly.

none of the above

saturated.

equilibrium.

requires no doping.

a forward-biased diode.

a reverse-biased germanium diode.

Divalent

that all impurities are removed to get pure silicon.

combination

the status of the diode.

4

None of the above

0.3V

None of these

Both A & C

saturated

is heated up by large amounts of current in the forward direction

reverse leakage current

higher current sources

due to the PN junction of the diode

cathode lead

biasing voltage

p region

+ cathode, + anode

switching diode

rise in temperature

holes and electrons

Zener diode

only ions i.e., immobile charges

None of the above

increases & decreases

is heated up by large amounts of current in the forward direction.

reverse leakage

current.

Undefined

tunnel diodes.

depletion region

Schottky

has a large number of electrons

there is no potential on the n-type or p-type materials

sinusoidal

A

dc resistance

higher, higher

None of the above

Infinity

in parallel

None of the above

the potential barrier is reduced to zero

in the breakdown region

None of the above

Stores charges

Constant-current diode

higher current sources

forward-bias current.

Gunn

step-recovery

switching device

opt5

opt6

Answer

Electric current

good conductor

the diode is internally shorted.

semiconductor

forward-biased.

current.

has pentavalent impurity atoms added.

a pn junction.

a germanium diode.

Trivalent

that impurities are added to decrease the resistance of the material.

recombination

the value of dc voltages for the device to operate properly.

4

Diffusion

0.7V

0.3V

Both A & C

forward-biased

is subjected to a large reverse voltage

reverse leakage current

current limiting resistors

due to current passing through the diode

cathode lead

breakdown voltage

depletion region

+ anode, – cathode

varactor diode

impact ionisation

reverse biased

Tunnel diode

only ions i.e., immobile charges

Automatic frequency control

decreases.

is subjected to a large reverse voltage.

reverse leakage current.

An open circuit

hot carrier diodes.

Reverse bias region

Schottky

behaves like an insulator

the p-type material is more positive than the n-type material

exponential

μA

doping levels

lower, higher

increases

0

in parallel

Has a sharp breakdown at low reverse voltage

Reverse bias exceeds a certain value

Reverse biased

Specially doped p–n junctions

Decreases

Schottky diode

current limiting resistors

magnitude of voltage

varactor

step-recovery

switching device

Questions

When transistors are used in digital circuits they usually operate in the

A transistor has a β of 250 and a base current, I_B , of 20 μ A. The collector current, I_C , equals:

A current ratio of I_C/I_E is usually less than one and is called:

In a C-E configuration, an emitter resistor is used for:

To operate properly, a transistor's base-emitter junction must be forward biased with reverse bias applied to which the C-B configuration is used to

provide which type of gain?

A transistor may be used as a switching device or as a:

If an input signal ranges from 20–40 μ A (microamps), with an output signal ranging from .5–1.5 mA (milliamps), what

Which is beta's current ratio?

A collector characteristic curve is a graph showing:

With low-power transistor packages, the base terminal is usually the:

When a silicon diode is forward biased, what is V_{BE} for a C-E configuration?

What is the current gain for a common-base configuration where $I_E = 4.2$ mA and $I_C = 4.0$ mA?

With a PNP circuit, the most positive voltage is probably:

If a 2 mV signal produces a 2 V output, what is the voltage gain?

The term BJT is short for

Most of the electrons in the base of an NPN transistor flow:

In a transistor, collector current is controlled by:

Total emitter current is:

Often a common-collector will be the last stage before the load; the main function(s) of this stage is to:

For a C-C configuration to operate properly, the collector-base junction should be reverse biased, while forward bi

The input/output relationship of the common-collector and common-base amplifiers is:

At saturation the value of V_{CE} is nearly _____, and $I_C =$ _____.

In which operation region(s) does the Ebers-Moll model describe a bipolar transistor?

Transistor act as a?

The part of the transistor which is heavily doped to produce large number of majority carriers is

A BJT is a _____-controlled device.

In a transistor

The principal advantage(s) of BJTs over MOSFETs is (are) that

What is the ratio of I_C to I_B ?

For normal operation of a pnp BJT, the base must be _____ with respect to the emitter and _____ with res

The term BJT is short for

For a silicon transistor, when a base-emitter junction is forward-biased, it has a nominal voltage drop of

What are the two types of bipolar junction transistors?

What is the order of doping, from heavily to lightly doped, for each region?

in what range of voltages is the transistor in the linear region of its operation?

What is (are) common fault(s) in a BJT-based circuit?

The dc load line on a family of collector characteristic curves of a transistor shows the

How many layers of material does a transistor have?

In which region are both the collector-base and base-emitter junctions forward-biased?

Which of the following is (are) the terminal(s) of a transistor?

Transistors are _____-terminal devices.

How many carriers participate in the injection process of a unipolar device?

In what decade was the first transistor created?

Which component of the collector current I_C is called the leakage current?

Clipping is the result of

In a NPN transistors Collector is

In a NPN transistors emitter is

In a NPN transistors base is

When a transistor is used as a switch, it is stable in which two distinct regions?

At which of the following condition(s) is the depletion region uniform?

Clipping is the result of

alpha refers to

Beta refers to

gamma refers to

In a transistor, collector current is controlled by:

How much is the base-to-emitter voltage of a transistor in the "on" state?

Which of the following equipment can check the condition of a transistor?

For what kind of amplifications can the active region of the common-emitter configuration be used?

A transistor can be checked using a(n) _____.

opt1

active region

500 A

beta

stabilization

collector-emitter

voltage

fixed resistor

0.05

I_C/I_B

emitter current (I_E) versus collector-emitter voltage (V_{CE}) with (V_{BB}) base bias voltage held constant

tab end

voltage-divider bias

16.8

ground

0.001

base junction transistor

out of the base lead

collector voltage

$I_E - I_C$

provide voltage gain

collector-emitter

270 degrees

zero, zero

Forward active.

conductor

emitter

current

$\beta = \alpha / (\alpha + 1)$

voltage drop across the transistor is important.

DC

positive, negative

base junction transistor

0.7 V.

nnp and npn

base, collector, emitter

$0 < V_{CE}$

opens or shorts internal to the transistor

saturation region.

1

Active

Emitter

2

1

1930s

Majority

the input signal being too large

Heavily doped

Heavily doped

Heavily doped

saturation and active

No bias

the input signal being too large.

I_c/I_b

I_c/I_b

$1+\alpha$

collector voltage

0 V

Current tracer

Voltage

curve tracer

opt2

breakdown region

5 mA

theta

ac signal bypass

base-collector

current

tuning device

20

VCC

collector current (I_C) versus collector-emitter volt:

middle

0.4 V

1.05

VC

0.004

binary junction transistor

into the collector

base current

$I_C + I_E$

provide phase inversion

base-emitter

180 degrees

VCC, $I_C(\text{sat})$

Saturation.

semi-conductor

base

voltage

$\beta = \alpha / (1 - \alpha)$

they are not as prone to ESD.

h_{FE}

positive, positive

binary junction transistor

0.3 V.

pnp and npn

emitter, collector, base

$0.7 < V_{CE} < V_{CE(\text{max})}$

open bias resistor(s)

cutoff region.

2

Cutoff

Base

3

2

1940s

Independent

the transistor being driven into saturation.

moderately doped

moderately doped

moderately doped

active and cutoff

$V_{DS} > 0 \text{ V}$

the transistor being driven into saturation

I_C/I_E

I_C/I_E

$1 - \alpha$

base current

0.7 V

Digital display meter (DDM)

Current

digital meter

opt3

saturation and cutoff regions

50 mA

alpha

collector bias

base-emitter

resistance

rectifier

50

I_B/I_E

collector current (I_C) versus collector-emitter voltage (V_C) with (V_{BB}) base b

right end

0.7 V

0.2

V_{BE}

100

both junction transistor

into the emitter

collector resistance

$I_B + I_C$

provide a high-frequency path to improve the frequency response

collector-base

90 degrees

zero, $I(\text{sat})$

Cut-off.

insulator

collector

-

$\alpha = \beta / (\beta - 1)$

both of the above

DC

negative, positive

both junction transistor

0.2 V.

ppn and npn

emitter, base, collector

$V_{CE(\text{max})} > V_{CE}$

external opens and shorts on the circuit board

active region.

3

Saturation

Collector

4

3

1950s

Minority

the transistor being driven into cutoff.

lightly doped

lightly doped

lightly doped

saturation and cutoff

$V_{DS} = V_P$

the transistor being driven into cutoff.

I_E/I_C

I_E/I_C

$1/\alpha$

collector resistance

0.7 mV

Ohmmeter (VOM)

Power

ohmmeter

opt4

linear region

0.208333333

omega

higher gain

collector-base

power

variable resistor

500

I_E/I_B

collector current (I_C) versus collector-emitter voltage (V_{CE}) with (V_{BE}) base bias voltage held constant

stud mount

emitter voltage

0.95

V_{CC}

1000

bipolar junction transistor

into the base supply

all of the above

$I_B - I_C$

buffer the voltage amplifiers from the low-resistance load and provide impedance matching for maximum power transfer

cathode-anode

0 degrees

V_{CC} , zero

All of the above.

thermionic valve

any of the above depending upon the nature of transistor

-

$\alpha = (\beta+1)/\beta$

none of the above

either β_{DC} or h_{FE} , but not β_{AC}

negative, negative

bipolar junction transistor

V_{CC} .

pins and steps

collector, emitter, base

none of the above

all of the above

all of the above

4

All of the above

All of the above

5

0

1960s

None of the above

all of the above
none of the these
none of the these
none of the these
none of the above
None of the above
all of the above
lb/lc
lb/lc
1/(1-alpha)
all of the above
Undefined
All of the above
All of the above
Any of the above

opt5

.transfer

opt6

Answer

saturation and cutoff regions

5 mA

alpha

stabilization

collector-base

voltage

variable resistor

50

I_C/I_B

collector current (I_C) versus collector-emitter voltage (V_{CE}) with (V_{BB}) base bias voltage held constant

middle

0.7 V

0.95

ground

1000

bipolar junction transistor

into the collector

base current

$I_B + I_C$

buffer the voltage amplifiers from the low-resistance load and provide impedance matching for maximum power t

collector-emitter

0 degrees

zero, $I(\text{sat})$

All of the above.

thermionic valve

emitter

current

$\alpha = \beta / (\beta - 1)$

both of the above

either β_{DC} or h_{FE} , but not β_{AC}

negative, positive

bipolar junction transistor

0.7 V.

nnp and npn

emitter, collector, base

$0.7 < V_{CE} < V_{CE(\text{max})}$

all of the above

all of the above

3

Saturation

All of the above

3

1

1940s

Minority

all of the above
moderately doped
Heavily doped
lightly doped
saturation and cutoff
No bias
all of the above
 I_c/I_e
 I_c/I_b
 $1+\alpha$
base current
0.7 V
All of the above
All of the above
Any of the above

Questions

When an input delta of 2 V produces a transconductance of 1.5 mS, what is the drain current delta?

When not in use, MOSFET pins are kept at the same potential through the use of:

D-MOSFETs are sometimes used in series to construct a cascode high-frequency amplifier to overcome the loss of:

A MOSFET has how many terminals?

IDSS can be defined as:

With the E-MOSFET, when gate input voltage is zero, drain current is:

With a 30-volt VDD, and an 8-kilohm drain resistor, what is the E-MOSFET Q point voltage, with ID = 3 mA?

When an input signal reduces the channel size, the process is called:

When applied input voltage varies the resistance of a channel, the result is called:

When is a vertical channel E-MOSFET used?

How will a D-MOSFET input impedance change with signal frequency?

What is the transconductance of an FET when ID = 1 mA and VGS = 1 V?

Which component is considered to be an "OFF" device?

For what value of ID is gm equal to 0.5 gm0?

Where do you get the level of gm and rd for an FET transistor?

The class D amplifier uses what type of transistors?

What is (are) the function(s) of the coupling capacitors C1 and C2 in an FET circuit?

What is the typical value for the input impedance Zi for JFETs?

MOSFETs make better power switches than BJTs because they have

MOSFET digital switching is used to produce which digital gates?

Which FET amplifier(s) has (have) a phase inversion between input and output signals?

MOSFET can be used as a

What limits the signal amplitude in an analog MOSFET switch?

Input resistance of a common- drain amplifier is

E-MOSFETs are generally used in switching applications because

For an FET small-signal amplifier, one could go about troubleshooting a circuit by _____.

The E-MOSFET is quite popular in _____ applications.

Material used for design of MESFET is

Secondary breakdown occurs in

CMOS is widely used in

In the transfer characteristics of a MOSFET, the threshold voltage is the measure of the

Input impedance of MOSFET is

MOSFET uses the electric field of

In MOSFET devices the N-channel type is better the P-channel type in the following respects

In a MOSFET, the polarity of the inversion layer is the same as that of the

Which of the following is expected to have highest input impedance?

Most small - signal E - MOSFETs are found in

Which insulating layer used in Fabrication of MOSFET?

What is used to higher the speed of operation in MOSFET fabrication?

A power MOSFET has three terminals called

MESFET can be operated on

The arrow on the symbol of MOSFET indicates

The operation of CCD is

What limits the signal amplitude in an analog MOSFET switch?

Input resistance of a common- drain amplifier is

E-MOSFETs are generally used in switching applications because

I_{DSS} can be defined as:

With the E-MOSFET, when gate input voltage is zero, drain current is:

With a 30-volt V_{DD} , and an 8-kilohm drain resistor, what is the E-MOSFET Q point voltage, with $I_D = 3 \text{ mA}$?

When an input signal reduces the

channel size, the process is called:

When applied input voltage varies the resistance of a channel, the result is called:

Most small - signal E - MOSFETs are found in

Which insulating layer used in Fabrication of MOSFET?

What is used to higher the speed of operation in MOSFET fabrication?

When an input delta of 2 V produces a transconductance of 1.5 mS, what is the drain current delta?

When not in use, MOSFET pins are kept at the same potential through the use of:

D-MOSFETs are sometimes used in series to construct a cascode high-frequency amplifier to overcome the loss of:

A MOSFET has how many terminals?

I_{DSS} can be defined as:

What is (are) the function(s) of the coupling capacitors C_1 and C_2 in an FET circuit?

opt1

666 mA

shipping foil

low output impedance

2 or 3

the minimum possible drain current

at saturation

6 V

enhancement

saturization

for high frequencies

As frequency increases input impedance increases.

1 kS

transistor

0 mA

from the dc biasing arrangement

JFETs

to create an open circuit for dc analysis

100 k

lower turn-off times.

inverters

common-gate

Current controlled capacitor

the switch input capacitance

$R_G \parallel R_{IN}(\text{gate})$.

of their very low input capacitance.

viewing the circuit board for poor solder joints

digital circuitry

Gallium arsenide (GaAs)

MOSFET but not in BJT

Digital wrist watches

minimum voltage to induce a n-channel/p-channel for conduction

less than of FET but more than BJT.

gate capacitance to control the channel current.

it has better noise immunity.

charge on the gate electrode

MOSFET.

heavy - current applications.

Aluminium oxide

Ceramic gate

Collector, emitter and gate.

Enhancement mode (normally OFF) only

that it is a N-channel MOSFET

captures light and converts it to digital data

the switch input capacitance

$R_G \parallel R_{IN}(\text{gate})$.

of their very low input capacitance.
the minimum possible drain current
at saturation
6 V

enhancement
saturation
heavy - current applications.
Aluminium oxide
Ceramic gate
666 mA
shipping foil
low output impedance
2 or 3
the minimum possible drain current
to create an open circuit for dc analysis

opt2

3 mA

nonconductive foam

capacitive reactance

3

the maximum possible current with VGS held at -4 V

zero

10 V

substrate

connecting

polarization

for high voltages

As frequency increases input impedance is constant.

1 mS

JFET

0.25 IDSS

from the specification sheet

BJTs

to isolate the dc biasing arrangement from the applied signal and load

1 M

lower on-state resistance.

NOR gates

common-drain

Voltage controlled capacitor

VGS(th)

$R_G + R_{IN}(\text{gate})$.

of their threshold characteristic (VGS(th)).

using a dc meter

high-frequency

Germanium

Both MOSFET and BJT

analogue circuits

minimum voltage till which temperature is constant

more than that of FET and BJT.

barrier potential of p-n junction to control the channel current.

it is faster.

minority carriers in the drain

JEFT amplifier.

discrete circuits.

Silicon Nitride

Silicon dioxide

Drain, source and gate.

Depletion mode only (normally ON) only

the direction of electrons

converts digital data

VGS(th)

$R_G + R_{IN}(\text{gate})$.

of their threshold characteristic ($V_{GS(th)}$).
the maximum possible current with V_{GS} held at -4 V
zero
 10 V
substrate
connecting
polarization
discrete circuits.
Silicon Nitride
Silicon dioxide
 3 mA
nonconductive foam
capacitive reactance

3

the maximum possible current with V_{GS} held at -4 V
to isolate the dc biasing arrangement from the applied signal and load

opt3

0.75 mA

conductive foam

high input impedance

4

the maximum possible current with VGS held at 0 V

IDSS

24 V

gate charge

cutoff

for high currents

As frequency decreases input impedance increases.

1 k

D-MOSFET

0.5 IDSS

from the characteristics

MOSFETs

to create a short-circuit equivalent for ac analysis

10 M

a positive temperature coefficient.

NAND gates

common-source

Current controlled inductor

the switch's power handling

RG

of their high-frequency response capabilities.

applying a test ac signal

buffering

Silicon

BJT but not in MOSFET

high power circuits

minimum voltage to turn off the device

more than that of FET but less than BJT.

both (A) and (B).

it is TTL compatible.

majority carries in the substrate.

CE bipolar transistor.

disk drives.

Silicon dioxide

Silicon nitride

Drain, source and base.

Both Enhancement mode and Depletion mode

the direction of conventional current flow

project the data on screen

the switch's power handling

RG

of their high-frequency response capabilities.
the maximum possible current with VGS held at 0 V
IDSS
24 V

gate charge
cutoff
disk drives.
Silicon dioxide
Silicon nitride
0.75 mA
conductive foam
high input impedance

the maximum possible current with VGS held at 0 V
to create a short-circuit equivalent for ac analysis

opt4

0.5 mA

a wrist strap

inductive reactance

3 or 4

the maximum drain current with the source shorted

widening the channel

30 V

depletion

field effect

for high resistances

As frequency decreases input impedance is constant.

1 m Ω

E-MOSFET

IDSS

All of the above

any of the above

All of the above

1000 M Ω

all of the above

all of the above

all of the above

Voltage controlled inductor

VDS

RIN(gate).

of their power handling.

All of the above

All of the above

Zinc arsenide

None of these

all of the above

none of the above mentioned is true

less than that of FET and BJT.

none of these.

it has better drive capability.

majority carries in the source .

Common collector bipolar transistor

integrated circuit.

None of the mentioned

Poly silicon gate

Collector, emitter and base.

None of the above

that it is a P-channel MOSFET

Captures light

VDS

RIN(gate).

of their power handling.

the maximum drain current with the source shorted

widening the channel

30 V

depletion

field effect

integrated circuit.

None of the mentioned

Poly silicon gate

0.5 mA

a wrist strap

inductive reactance

3 or 4

the maximum drain current with the source shorted

All of the above

opt5

opt6

Answer

3 mA

conductive foam

high input impedance

3 or 4

the maximum possible current with VGS held at 0 V

zero

6 V

depletion

field effect

for high currents

As frequency decreases input impedance increases.

1 mS

E-MOSFET

0.25 IDSS

All of the above

MOSFETs

All of the above

1000 MΩ

all of the above

all of the above

common-source

Voltage controlled capacitor

VGS(th)

$R_G \parallel R_{IN}(\text{gate})$.

of their threshold characteristic (VGS(th)).

All of the above

All of the above

Gallium arsenide (GaAs)

BJT but not in MOSFET

Digital wrist watches

minimum voltage to induce a n-channel/p-channel for conduction

more than that of FET and BJT.

gate capacitance to control the channel current.

it is faster.

majority carries in the source .

MOSFET.

integrated circuit.

Silicon dioxide

Poly silicon gate

Drain, source and gate.

Both Enhancement mode and Depletion mode

the direction of electrons

captures light and converts it to digital data

VGS(th)

$R_G \parallel R_{IN}(\text{gate})$.

of their threshold characteristic ($V_{GS(th)}$).
the maximum possible current with V_{GS} held at 0 V
zero
6 V

depletion
field effect
integrated circuit.
Silicon dioxide
Poly silicon gate
3 mA
conductive foam
high input impedance
3 or 4
the maximum possible current with V_{GS} held at 0 V
All of the above

Questions

A differential amplifier
When a differential amplifier is operated single-ended,
In differential-mode
In the common-mode
The common-mode gain is
The differential gain is
If $A_{DM} = 3500$ and $A_{CM} = 0.35$, the CMRR is
With zero volts on both inputs, an OPamp ideally should have an output
Of the values listed, the most realistic value for open-loop voltage gain of an OP-amp is
A certain OP-amp has bias currents of $50\ \mu\text{A}$ and $49.3\ \mu\text{A}$. The input offset current is
The output of a particular OP-amp increases $8\ \text{V}$ in $12\ \mu\text{s}$. The slew rate is
A common-mode signal is applied to
The common-mode voltage gain is
The input stage of an OP-amp is usually a
Current cannot flow to ground through
Which of the following electrical characteristics is not exhibited by an ideal op-amp?
An ideal op-amp requires infinite bandwidth because
Ideal op-amp has infinite voltage gain because
Find the output voltage of an ideal op-amp. If V_1 and V_2 are the two input voltages
How will be the output voltage obtained for an ideal op-amp?
Which is not the ideal characteristic of an op-amp?
Find the input voltage of an ideal op-amp. It's one of the inputs and output voltages are 2v and 12v . (Gain=3)
Which factor determine the output voltage of an op-amp?
The opamp can amplify
In a nonlinear op-amp circuit, the
The input signal for an instrumentation amplifier usually comes from
In a differential amplifier, the CMRR is limited mostly by the
A common - mode signal is applied to
The common-mode voltage gain is
The input stage of an op amp is usually a
The common - mode rejection ratio is
A 741 C has
The typical input stage of an opamp has a
The input offset electric current is usually
With both bases grounded, the only offset that produces an error is the
The voltage gain of a loaded differential amp is
At the unity-gain frequency, the open-loop voltage gain is
The tail current in a differential amplifier equals
A common - mode signal is applied to
An instrumentation amplifier has a high
Of the values listed, the most realistic value for open-loop voltage gain of an OP-amp is
An ideal op-amp requires infinite bandwidth because
With zero volts on both inputs, an OPamp ideally should have an output
Of the values listed, the most realistic value for open-loop voltage gain of an OP-amp is
A certain OP-amp has bias currents of $50\ \mu\text{A}$ and $49.3\ \mu\text{A}$. The input offset current is

The output of a particular OP-amp increases 8 V in 12 μ s. The slew rate is
A common-mode signal is applied to
The common-mode voltage gain is
The input stage of an OP-amp is usually a
Current cannot flow to ground through
Which of the following electrical characteristics is not exhibited by an ideal op-amp?
An ideal op-amp requires infinite bandwidth because
The common-mode gain is
The differential gain is
If $A_{DM} = 3500$ and $A_{CM} = 0.35$, the CMRR is
With zero volts on both inputs, an OPamp ideally should have an output
The typical input stage of an opamp has a
The input offset electric current is usually
With both bases grounded, the only offset that produces an error is the
Current cannot flow to ground through

opt1

is a part of an OP-amp
the output is grounded
opposite polarity signals are applied to the inputs
both inputs are grounded
very high
very high
1225
equal to the positive supply voltage
1
700 nA
90 V/ μ s
the non-inverting in
smaller than differential voltage gain
differential amplifier
a mechanical ground
Infinite voltage gain
Signals can be amplified without attenuation
To control the output voltage
$V_O = V_1 - V_2$
Amplifies the difference between the two input voltages
Input Resistance $\rightarrow 0$
8v
Both positive and negative saturation voltage
AC signals only
opamp never saturates
an inverting amplifier.
CMRR of the opamp
the non - inverting input.
smaller than the voltage gain.
differential amp.
very low.
a voltage gain of 100,000.
single - ended input and single-ended output
less than the input bias current.
input offset current.
large than the unloaded voltage gain.
1
difference between two emitter currents
the non - inverting input.
output impedance
1
Signals can be amplified without attenuation
equal to the positive supply voltage
1
700 nA

90 V/ μ s
the non-inverting in
smaller than differential voltage gain
differential amplifier
a mechanical ground
Infinite voltage gain
Signals can be amplified without attenuation
very high
very high
1225
equal to the positive supply voltage
single - ended input and single-ended output
less than the input bias current.
input offset current.
a mechanical ground

opt2

has one input and one output
one input is grounded and signal is applied to the other
the gain is one
the outputs are connected together
very low
very low
10,000
equal to the negative supply voltage
2000
99.3 μA
0.67 V/ μs
the inverting input
equal to differential voltage gain
class B push-pull amplifier
an a.c. ground
Infinite bandwidth
Output common-mode noise voltage is zero
To obtain finite output voltage
$V_O = A \times (V_1 - V_2)$
Amplifies individual voltages input voltages
Output impedance $\rightarrow 0$
4v
Positive saturation
DC signals only.
feedback loop is never opened
resistor
gain - bandwidth product.
the inverting input.
equal to the voltage gain.
class B push-pull amplifier.
as high as possible.
an input impedance of 2 M Ω .
single - ended input and differential output.
equal to zero.
input bias current.
equal to R_C / r_e .
$A_{V(\text{mid})}$.
sum of two emitter currents
the inverting input.
power gain.
2000
Output common-mode noise voltage is zero
equal to the negative supply voltage
2000
99.3 μA

0.67 V/ μ s
the inverting input
equal to differential voltage gain
class B push-pull amplifier
an a.c. ground
Infinite bandwidth
Output common-mode noise voltage is zero
very low
very low
10,000
equal to the negative supply voltage
single - ended input and differential output.
equal to zero.
input bias current.
an a.c. ground

opt3

has two outputs
both inputs are connected together
the outputs are of different amplitudes
an identical signal appears on both inputs
always unity
dependent on input voltage
80 dB
equal to zero
80 dB
49.7 μ A
1.5 V/ μ s
both inputs
greater than differential voltage gain
CE amplifier
a virtual ground
Infinite output resistance
Output voltage occurs simultaneously with input voltage changes
To receive zero noise output voltage
$V_O = A \times (V_1 + V_2)$
Amplifies products of two input voltage
Bandwidth \rightarrow
-4v
Negative saturation
both AC and DC signals
output shape is the same as the input shape.
differential amplifier.
supply voltages
both inputs.
greater than the voltage gain.
CE amplifier.
equal to the voltage gain.
an output impedance of 75
differential input and single - ended output.
less than the input offset voltage.
input offset voltage.
smaller than the unloaded voltage gain.
zero.
collector current divided by current gain
both inputs.
CMMR.
80 dB
Output voltage occurs simultaneously with input voltage changes
equal to zero
80 dB
49.7 μ A

1.5 V/ μ s
both inputs
greater than differential voltage gain
CE amplifier
a virtual ground
Infinite output resistance
Output voltage occurs simultaneously with input voltage changes
always unity
dependent on input voltage
80 dB
equal to zero
differential input and single - ended output.
less than the input offset voltage.
input offset voltage.
a virtual ground

opt4

answers a and c
the output is not inverted
only one supply voltage is used
the output signals are in-phase
unpredictable
about 100
answers b and c
equal to the CMRR
100,000
none of these
none of these
top of the tail resistor
none of the above
swamped amplifier
an ordinary ground
Infinite slew rate.
Output can drive infinite number of device
None of the mentioned
$V_O = V_1 \times V_2$
None of the mentioned
Open loop voltage gain \rightarrow
-2v
Supply voltage
neither AC not DC signals.
opamp may saturate.
Wheatstone bridge.
tolerance of the resistors
he top of the tail resistor
none of the above.
swamped amplifier.
equal to the common-mode voltage gain.
all of the above.
differential input and differential output
unimportant when a base resistor is used.
.
impossible to determine.
very large
collector voltage divided by collector resistance
he top of the tail resistor
supply voltage.
100,000
Output can drive infinite number of device
equal to the CMRR
100,000
none of these

none of these
top of the tail resistor
none of the above
swamped amplifier
an ordinary ground
Infinite slew rate.
Output can drive infinite number of device
unpredictable
about 100
answers b and c
equal to the CMRR
differential input and differential output
unimportant when a base resistor is used.
.
an ordinary ground

[illegible]

[illegible]

opt6

[illegible]

[illegible]

Answer

a and c
one input is grounded and signal is applied to the other
opposite polarity signals are applied to the inputs
an identical signal appears on both inputs
very low
very low
answers b and c
equal to zero
100,000
700 nA
0.67 V/ μ s
both inputs
smaller than differential voltage gain
differential amplifier
a virtual ground
Infinite output resistance
Signals can be amplified without attenuation
To obtain finite output voltage
$V_O = A \times (V_1 - V_2)$
Amplifies the difference between the two input voltages
Input Resistance $\rightarrow 0$
-2v
Both positive and negative saturation voltage
both AC and DC signals
opamp may saturate.
Wheatstone bridge.
gain - bandwidth product.
both inputs.
greater than the voltage gain.
differential amp.
as high as possible.
all of the above.
differential input and single - ended output.
less than the input bias current.
input offset voltage.
equal to R_C / r_e.
1
sum of two emitter currents
both inputs.
CMMR.
100,000
Signals can be amplified without attenuation
equal to zero
100,000
700 nA

0.67 V/ μ s
both inputs
smaller than differential voltage gain
differential amplifier
a virtual ground
Infinite output resistance
Signals can be amplified without attenuation
very low
very low
answers b and c
equal to zero
differential input and single - ended output.
less than the input bias current.
input offset voltage.
a virtual ground

Questions

A summing amplifier can have
An averaging amplifier has five inputs. The ratio R_f/R_i must be
In a scaling adder, the input resistors are
In an integrator, the feed back element is a
For step - in put, the out put of an integrator is a
In a differentiator, the feed back element is a
The output of the differentiator is proportional to
The voltage follower has a:
The ratio between differential gain and common-mode gain is called:
In an analog multiplier, the reference Voltage V_{ref} is internally set to ____
In one quadrant multiplier, the polarity of the input voltage V_x is _____ and V_y is _____
If $V_s = V_s \sin(2\pi f_s t)$ and $V_o = V_o \sin((2\pi f_o t) + \phi)$ are applied to a switch type phase detector, then the output consists of a DC term and the other term is _____
Division can be accomplished by placing the multiplier circuit in the _____ of the operational amplifier.
The input stage of Phase Locked Loop is _____
The Voltage Controlled Oscillator is also called as _____
The Voltage Controlled Oscillator is designed such that at zero voltage, it is oscillating at some initial frequency called _____ frequency.
Analog Multiplier produces an output which is a
The function of phase detector is to compare the _____ of the incoming signal to that of the output V_o of Voltage Controlled Oscillator.
Phase detector is basically a _____.
The output of phase detector is _____.
The signal V_c shifts the frequency in a direction to reduce the difference between f_s and f_o . Now the signal is in _____ range.
The VCO continues to change the frequency till its output frequency is _____ the input signal frequency.
The range of frequencies over which the PLL can maintain the lock with the incoming signal is called _____ range.
The range of frequencies over which the PLL can acquire the lock with the incoming signal is called _____ range
The output frequency of Voltage Controlled Oscillator f_o is _____
Voltage Controlled Oscillator is otherwise called as _____.
In PLL, the high frequency component ($f_s + f_o$) is removed by _____
Which of the following are the stages of PLL? i) free running ii) capture iii) tracking iv) pull in
Which of the following are the problems associated with the switch type phase detector? i) since the output voltage V_e is directly proportional to V_s , the phase detector gain and loop gain becomes dependent on the input signal amplitude. ii) output is proportional to \cos which makes it non linear. iii) the circuit becomes unstable iv) full wave detector
In switch type phase detector, at the locked state ($f_s = f_o$) the phase shift should be _____ in order to get zero error signal.
In balanced modulator type phase detector, the transistors act as _____.
In balanced modulator type phase detector, the phase angle to voltage transfer co-efficient K is _____

The Voltage to Frequency conversion factor of VCO is _____.
The output from a Phase Locked Loop system is _____.
If a divide by N - network is inserted between VCO output and phase comparator input of PLL, then in the locked state f_0 is _____.
When PLL is used as AM demodulator, the AM signal is shifted in phase by _____ before being fed to the multiplier.
The other name for capture range is _____ range.
The other name for lock in range is _____ range.
The range of modulating input voltage applied to a VCO is _____.
Lock in range of a PLL is _____ the capture range.
Which of the following is the drawback of variable transconductance multiplier?
The time taken for a PLL to capture the incoming signal is called _____ time.
If the voltage at the modulation input of VCo is biased at $7/8 V_{cc}$ then the output frequency of VCO in PLL is given by $f_0 =$ _____.
The maximum operated range of PLL 565 is _____.
The Lock in range of Phase Locked Loop is _____.
If the offset frequency f_1 is applied to the phase detector of frequency translator circuit, then at the locked state f_0 is given by _____.
_____ filter controls the capture range and lock in range of PLL.
The operating voltage range of IC 565 is _____.
An external capacitor connected across IC 565 will act as _____.
If V_c shifts the VCO frequency from the free running frequency f_0 to a frequency f , then the new frequency shift from VCO in a PLL is _____.
A _____ is an electronic system which generates any range of frequencies from a single fixed time base or oscillator.
Phase detector is basically a _____.
In PLL, the output of the error amplifier is equal to the _____.
Select correct statement of PLL.
The Voltage to Frequency Converter of VCO is defined as _____
IC 566 functions as _____.
The total time taken by PLL to establish the lock is called _____.
If the frequency of the carrier wave is varied in accordance with the modulating signal, then the modulation refers to _____ modulation
The capture range of PLL is defined as _____.
The lock in range of PLL is defined as _____.

opt1	opt2
only one input	only two inputs
5	0.2
all of the same value	all of different values
resistor	capacitor
pulse	triangular wave form
resistor	capacitor
the RC time constant	the rate at which the input is changing
closed-loop voltage gain of unity	small open-loop voltage gain
Amplitude	differential-mode rejection
15V	5V
positive, negative.	positive, positive
f_o	$2 * f_o$
feedback loop	inverting input terminal
Low Pass Filter	Error Amplifier
relaxation oscillator	free running multivibrator
free running	cut off
product of two input signals divided by a reference voltage.	product of two input signals and reference voltage.
phase and frequency	phase
summer	subtractor
$f_s + f_o$	$f_s - f_o$
lock-in	capture
less than	exactly the same as
tracking	capture
tracking	capture
$(V_{cc} - v_c) / (R_T * C_T * V_{cc})$	$v_c / (R_T * C_T * V_{cc})$
voltage to frequency converter	voltage to time converter
high pass filter	low pass filter
only i and ii	only ii and iv
i and ii	i, ii and iii
0°	180°
switch	amplifier
$(I_Q * R_L) / \pi$	$V_o / (2 * \pi)$

f_0 / V_{CC}	$8*f_0 / V_{CC}$
voltage or frequency	only voltage
f_s / N	$N*f_s$
0°	180°
tracking	lock in
tracking	acquisition
$0.5 V_{CC}$ to V_{CC}	$0.75 V_{CC}$ to V_{CC}
greater than	equal to
inaccurate	costly
pull out	capture
$0.25 / (R_T * C_T)$	$(R_T * C_T) / 4$
0 to 500 kHz	0.001 to 500 kHz
$f_L = 7.8 f_0 / v$	$f_L = \pm (7.8 f_0 / v)$
f_s	$f_s * f_1$
high pass filter	low pass filter
$\pm 6V$ to $\pm 12V$	$\pm 10V$ to $\pm 12V$
passive device	low pass filter
$f_0 + k_v * V_c$	$f_0 - k_v * V_c$
frequency multiplier	frequency synthesizer
summer	subtractor
error voltage	applied voltage
capture range is smaller than lock in range	capture range is greater than lock in range
V_c / f_0	f_0
phase detector	low pass filter
pull in time	pull out time
frequency shift keying	frequency
$f_c = \pm \{ (f_L) / (2 * \pi * C * (3.6 * 10^3)) \}^{1/2}$	$f_c = \pm \{ (f_L) / (2 * \pi * C) \}^{1/2}$
$f_L = \pm (K_v * K)$	$f_L = \pm (K_v * K * A$

opt3

only three inputs
1
each proportional to the weight of its input
zener diode
spike
zener diode
the amplitude of the input
closed-loop bandwidth of zero
common-mode rejection
20V
negative, negative
$f_o/2$
output
Voltage Controlled Oscillator
monostable multivibrator
capture
product of three input signals.
frequency
multiplier
$f_s * f_0$
free running
greater than
free running
free running
$2*(V_{cc}-V_c)/(R_T*C_T*V_{cc})$
voltage to current converter
band pass filter
i, ii and iii
ii,iii
270°
oscillator
$(4*I_Q*R_L)/\pi$

opt4

any number of inputs
2
related by a factor of two
voltage divider
ramp
voltage divider
both a and b
large closed-loop output impedance
phase
10V
negative positive
$3* f_o$
non inverting terminal
Phase Detector
phase shift oscillator
free cycle
product of two input signals.
amplitude
divider
$f_s + f_0$
unlocked
twice that of
pull in
pull in
$1/(R_T*C_T)$
frequency to voltage converter
band reject filter
only iv
only i
90°
modulator
$(I_Q*R_L)/2*\pi$

$2*f_0 / V_{CC}$	$4*f_0 / V_{CC}$
only frequency	only phase.
$f_s + N$	$f_s - N$
270°	90°
free running	acquisition
free running	capture
0 V_{CC} to V_{CC}	0.25 V_{CC} to V_{CC}
lesser than	less than or equal to
difficult to integrate in IC	scale factor depends on temperature which affects the output
lock in	pull in
$4(R_T * C_T)$	$(R_T * C_T)/0.25$
100 to 400 kHz	10 to 400 kHz
$f_L = \pm (8.7 f_0/v)$	$f_L = 8.7 f_0/v$
$f_s + f_1$	$f_s - f_1$
band pass filter	band reject filter
$\pm 8V$ to $\pm 12V$	$\pm 12V$
charging device	discharging device
$k_v * V_c$	V_c
frequency doubler	frequency translator
multiplier	divider
control voltage	power supply voltage
capture range is equal to lock in range	capture range is not equal to lock in range
V_c	f_0 / V_c
VCO	PLL
rise time	hold time
amplitude	phase
$f_c = \pm \{ (f_L) / (2\pi * C * (3.6 * 10^3)) \}$	$f_c = \pm \{ (f_L) / (2\pi * C) \}$
$f_L = \pm (K_v * K) / (A * (\pi/2))$	$f_L = \pm (K_v * K * A * (\pi/2))$

opt5	opt6	Answer
		any number of inputs
		0.2
		each proportional to the weight of its input capacitor
		ramp
		resistor
		both a and b
		closed-loop voltage gain of unity
		common-mode rejection
		10V
		positive, positive
		$2 * f_o$
		feedback loop
		Phase Detector
		free running multivibrator
		free running
		product of two input signals divided by a reference voltage.
		phase and frequency
		multiplier
		$f_s + f_o$
		capture
		exactly the same as
		tracking
		capture
		$2 * (V_{cc} - V_c) / (R_T * C_T * V_{cc})$
		voltage to frequency converter
		low pass filter
		i, ii and iii
		i and ii
		90°
		switch
		$(4 * I_Q * R_L) / \pi$

	$8 \cdot f_0 / V_{CC}$
	voltage or frequency
	$N \cdot f_s$
	90°
	acquisition
	tracking
	$0.75 V_{CC}$ to V_{CC}
	greater than
	scale factor depends on temperature which affects the output
	capture
	$0.25 / (R_T \cdot C_T)$
	0.001 to 500 kHz
	$f_L = \pm (7.8 f_0 / v)$
	$f_s + f_1$
	low pass filter
	$\pm 6V$ to $\pm 12V$
	low pass filter
	$f_0 + k_v \cdot V_c$
	frequency synthesizer
	multiplier
	control voltage
	capture range is smaller than lock in range
	f_0 / V_c
	VCO
	pull in time
	frequency
	$f_c = \pm \{ (f_L) / (2 \cdot \pi \cdot C \cdot (3.6 \cdot 10^3)) \}^{1/2}$
	$f_L = \pm (K_v \cdot K \cdot A \cdot (\pi/2))$

